



Department of Electronic & Telecommunication Engineering  
University of Moratuwa

EN4431 - ANALOG IC DESIGN

FULLY DIFFERENTIAL 3GHZ LC-VCO SIMULATION TO ACHIEVE  
SPECIFICATIONS

Supervisors:

*Dr. Thayaparan Subramaniam*

Instructors:

*Mr. Kithmin Wickremasinghe*

*MANIMOHAN T.*

*200377M*

This report is submitted as Assignment - 02 of module EN4431  
30<sup>th</sup> March 2025

## **ABSTRACT**

This report presents the design, simulation, and analysis of a fully differential 3GHz LC voltage-controlled oscillator (VCO) using a 45nm CMOS technology. The project aims to achieve low power consumption, a wide tuning range, and low phase noise, which are essential for high-frequency clock generation and distribution in modern processing systems. The design begins with the creation of a basic cross-coupled NMOS LC oscillator and progresses to incorporate MOS varactors for continuous tuning and switched capacitors for discrete tuning. A significant improvement is made by adding a cross-coupled PMOS device stage, resulting in a fully differential VCO with increased output swing and better performance. Transient and parametric simulations are conducted to validate the design, showing a 3GHz oscillation frequency with a tuning range of over 20% (2.7 GHz to 3.3 GHz). The frequency of oscillation as a function of the control voltage is also analyzed. Additionally, the report discusses potential improvements for achieving a more stable and wider tuning range. Results from the simulation, including frequency spectrum analysis and phase noise, are provided, along with a discussion on how the design can be optimized further for better performance. The circuit netlist is included in the appendix for reference. This is based on the module EN4431 - Analog IC Design, Which is conducted by Dr. Thayaparan Subramaniam.

## CONTENTS

ABSTRACT .....	ii
CONTENTS .....	iii
LIST OF FIGURES.....	v
<b>1 INTRODUCTION .....</b>	<b>1</b>
<b>2 DESIGN METHODOLOGY AND DETAILS OF THE CALCULATION AND DEVICE SIZES OF A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTORS .....</b>	<b>2</b>
2.1 VCO Design Specifications.....	2
2.2 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	2
2.3 Pre-Calculations .....	3
2.3.1 Transistor Parameters from Cadence Simulation .....	3
2.3.2 Calculation of $\mu C_{ox}$ for NMOS and PMOS.....	3
2.4 Details of the Calculation and Device Sizes .....	4
2.4.1 LC Tank Design .....	4
2.4.2 Tuning Range 20%(2.7 GHz to 3.3 GHz).....	4
2.4.3 Varactor Size calculation( $M_{V1}$ , $M_{V2}$ ) .....	4
2.4.4 Calculation of Tank Loss $R_p$ .....	5
2.4.5 Calculation of Transistor Size ( $M_1$ , $M_2$ ) .....	5
2.5 Summary of Calculated Values .....	6
<b>3 SIMULATION RESULTS FOR A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTORS .....</b>	<b>7</b>
3.1 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	7
3.1.1 Transient simulation results (up to 10 ns after steady state) .....	7
3.1.2 Parametric simulation results of frequency of oscillation ( $f_0$ ) vs. control voltage ( $V_{cont}$ ) .....	8
3.1.3 Periodic steady-state (PSS) simulation .....	10
3.1.4 Phase noise (PS) simulation results. ....	11
3.2 Discussion on Type IV Fully Differential CC LC-VCO .....	11
3.2.1 Tuning Range.....	11
3.2.2 VCO Gain ( $K_{VCO}$ ) .....	11
3.2.3 Output Voltage Swing .....	12
3.2.4 Noise Performance (Phase & Amplitude) .....	12
<b>4 DESIGN METHODOLOGY AND DETAILS OF THE CALCULATION AND DEVICE SIZES OF A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR .....</b>	<b>13</b>
4.1 VCO Design Specifications.....	13
4.2 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	13
4.3 Pre-Calculations .....	14
4.3.1 Transistor Parameters from Cadence Simulation .....	14
4.3.2 Calculation of $\mu C_{ox}$ for NMOS and PMOS.....	14
4.4 Details of the Calculation and Device Sizes .....	15
4.4.1 LC Tank Design .....	15
4.4.2 Tuning Range 20%(2.7 GHz to 3.3 GHz).....	15

4.4.3	Varactor Size calculation ( $M_{V1}, M_{V2}$ ) .....	15
4.4.4	Calculation of Tank Loss $R_p$ .....	16
4.4.5	Calculation of Transistor Size ( $M_1, M_2$ ) .....	16
4.5	Summary of Calculated Values .....	17
5	SIMULATION RESULTS FOR A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR.....	18
5.1	A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	18
5.1.1	Transient simulation results (up to 10 ns after steady state) .....	18
5.1.2	Parametric simulation results of frequency of oscillation ( $f_0$ ) vs. control voltage ( $V_{cont}$ ) .....	19
5.1.3	Periodic steady-state (PSS) simulation .....	21
5.1.4	Phase noise (PS) simulation results. ....	22
5.2	Discussion on Type IV Fully Differential CC LC-VCO .....	22
5.2.1	Tuning Range.....	22
5.2.2	VCO Gain ( $K_{VCO}$ ) .....	22
5.2.3	Output Voltage Swing .....	23
5.2.4	Noise Performance (Phase & Amplitude) .....	23
6	COMPARISON BETWEEN SIMULATION RESULTS OF A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTOR AND A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR.....	24
6.1	Comparison .....	24
6.2	Key points on the Tuning Range .....	24
6.3	Enhancements and Improvements for a Wider and More Stable Tuning Range and Stability .....	24
6.3.1	Hybrid Capacitor Bank with Floating Switches .....	24
6.3.2	Optimized Symmetric Varactor Design .....	25
7	APPENDIX: NETLISTS .....	26
7.1	Netlist of A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	26
7.2	Netlist of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	34

## LIST OF FIGURES

1	LC-VCO.....	1
2	A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	2
3	Transistor Parameters from Cadence Simulation .....	3
4	Circuit diagram of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors.....	7
5	A transient simulation of $V_X - V_Y$ was performed with $V_{cont}$ set to 250mV, resulting in a peak-to-peak value of 446.1mV.a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	7
6	Transient simulation of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors.....	8
7	A transient simulation of $V_X - V_Y$ was conducted with $V_{cont}$ set to 500mV, and FFT analysis indicated an oscillation frequency of 3.048 GHz. ....	8
8	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	8
9	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	9
10	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	9
11	The relationship between the oscillation frequency ( $f_0$ ) and the control voltage ( $V_{cont}$ ) of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	10
12	A PSS simulation of $V_X - V_Y$ was performed at $V_{cont} = 500mV$ , revealing a first harmonic frequency of 3.06 GHz of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors .....	10
13	PSS simulation results: The green curve represents Phase Modulation (PM), while the purple curve corresponds to Amplitude Modulation (AM) of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors.....	11
14	Calculation of $K_{VCO}$ from the $V_{cont}$ vs. $f_0$ curve. ....	12
15	A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	13
16	Transistor Parameters from Cadence Simulation .....	14
17	A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor.....	18
18	Transient analysis of $V_X - V_Y$ with a control voltage ( $V_{cont}$ ) of 320 mv with $V_{pp}$ of 3.25V . of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor.....	18
19	Transient analysis of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor.....	19
20	Transient simulation of $V_X - V_Y$ with $V_{cont} = 320$ mV, and FFT analysis reveals an oscillation frequency of 3.023 GHz of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	19
21	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	19

22	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	20
23	Transient simulation of $V_X - V_Y$ and FFT analysis for $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$ of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	20
24	Oscillation frequency ( $f_0$ ) as a function of control voltage ( $V_{cont}$ ) of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	21
25	PSS simulation of $V_X - V_Y$ at $V_{cont} = 500$ mV, indicating a first harmonic frequency of 2.989 GHz of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	21
26	PSS simulation results: The green curve represents Phase Modulation (PM), while the purple curve corresponds to Amplitude Modulation (AM) of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor .....	22
27	Calculation of $K_{VCO}$ from the $V_{cont}$ vs. $f_0$ curve.....	23

## 1 INTRODUCTION


Voltage-Controlled Oscillators (VCOs) are essential components in modern communication systems, phase-locked loops (PLLs), and frequency synthesizers. They generate a periodic output signal whose frequency can be tuned by varying an external control voltage. Among the various VCO topologies, LC-based oscillators offer superior phase noise performance, making them ideal for high-frequency applications.

This report focuses on the analysis and design of two different LC-based VCO architectures:


- \* **Type I Cross-Coupled LC VCO** – A single-ended VCO with MOS varactors, which provides a compact and efficient design suitable for low-power applications.
- \* **Type IV Cross-Coupled Differential LC VCO** – A differential architecture incorporating a symmetric inductor and MOS varactors to achieve improved phase noise and higher tuning linearity.

The VCOs are designed in a 45nm CMOS process, operating with a 1V supply voltage and targeting an oscillation frequency of 3GHz. The design must achieve a tuning range of at least 20 (2.7GHz – 3.3GHz) while ensuring optimal performance metrics such as gain ( $K_{VCO}$ ), quality factor ( $Q$ ), and output swing.

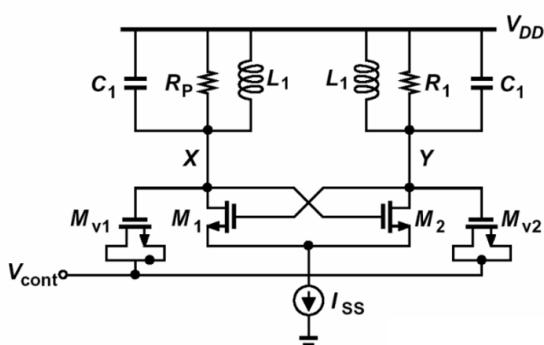This report provides a detailed step-by-step analysis of the key design parameters, including inductance, capacitance, and bias current selection. Furthermore, it presents calculations for both architectures to verify their compliance with the given specifications.



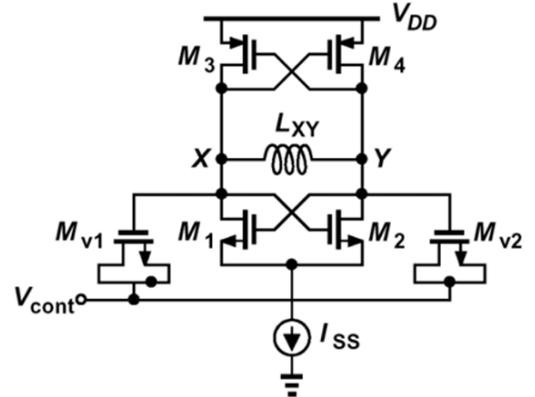(a) A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors



(b) A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

Figure 1 — LC-VCO

## 2 DESIGN METHODOLOGY AND DETAILS OF THE CALCULATION AND DEVICE SIZES OF A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTORS

### 2.1 VCO Design Specifications

#### VCO Design Specifications

Parameter	Specification
Technology Node	45 nm CMOS
Supply Voltage $V_{DD}$	1 V
Nominal Input Common-Mode Voltage $V_{DD}/2$	0.5 V
Bias Current $I_{bias}$	10 $\mu$ A (adjustable)
Oscillation Frequency $f_0$	3 GHz
Tuning Range	> 20% (2.7 GHz – 3.3 GHz)
VCO Gain $K_{VCO}$	To be determined (? GHz/V)
Varactor Type	MOS Varactor
Inductor Configuration	Symmetric Inductor (for Type IV VCO)

### 2.2 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

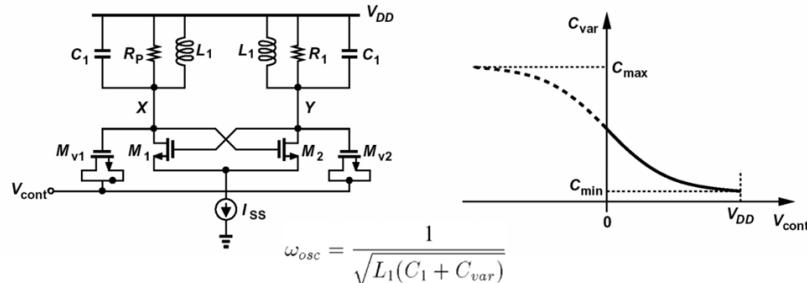


Figure 2 — A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

This voltage-controlled oscillator (VCO) works by generating a continuous oscillating signal with a frequency that can be adjusted using a control voltage ( $V_{cont}$ ). The **LC tank circuit**, made up of an inductor ( $L_1$ ) and capacitors ( $C_1 + C_{var}$ ), determines the oscillation frequency. The **cross-coupled transistors** ( $M_1$  and  $M_2$ ) provide **positive feedback**, which compensates for losses and keeps the oscillations going.

The **MOS varactors** ( $M_{v1}$  and  $M_{v2}$ ) act as voltage-controlled capacitors, where their capacitance ( $C_{var}$ ) changes based on  $V_{cont}$ . When  $V_{cont}$  increases,  $C_{var}$  decreases, making the frequency higher. When  $V_{cont}$  decreases,  $C_{var}$  increases, lowering the frequency.

The **current source** ( $I_{SS}$ ) provides a steady current to bias the transistors and control the oscillation amplitude. **Resistors** ( $R_1$  and  $R_p$ ) represent circuit losses, which can affect efficiency and phase noise. This VCO is commonly used in **wireless communication, radio systems, and phase-locked loops (PLLs)** because it provides a stable and tunable frequency signal.

## 2.3 Pre-Calculations

### 2.3.1 Transistor Parameters from Cadence Simulation

The following parameters are obtained from Cadence simulation for NMOS and PMOS design with channel length  $L = 1\mu\text{m}$  (to minimize the channel length modulation) and width  $W = 10\mu\text{m}$  for both NMOS and PMOS transistors. The supply voltage is  $V_{DD} = 1\text{V}$ , and the bias current is  $I_o = 10\mu\text{A}$ .

Referefnce : - [How to find process parameter of any technology node](#)

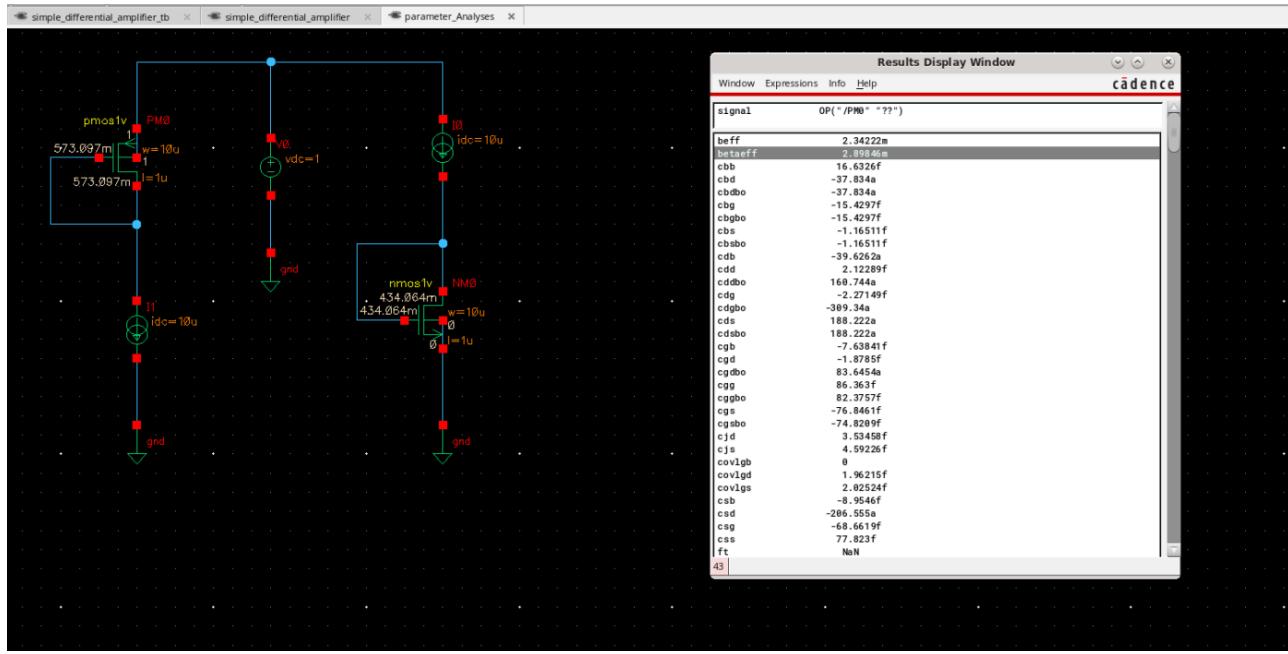


Figure 3 — Transistor Parameters from Cadence Simulation

### NMOS Parameters

- \* Effective Beta ( $\beta_{\text{eff, NMOS}}$ ): 2.89846 mA/V<sup>2</sup> (rounded to 3 mA/V<sup>2</sup>)
- \* Threshold Voltage ( $V_{\text{th, NMOS}}$ ): 397.975 mV (rounded to 0.4 V)

### PMOS Parameters

- \* Effective Beta ( $\beta_{\text{eff, PMOS}}$ ): 2.89846 mA/V<sup>2</sup> (rounded to 3 mA/V<sup>2</sup>)
- \* Threshold Voltage ( $V_{\text{th, PMOS}}$ ): -334.497 mV (rounded to -0.3 V)

### 2.3.2 Calculation of $\mu C_{ox}$ for NMOS and PMOS

The effective beta ( $\beta_{\text{eff}}$ ) is connected to the process transconductance parameter  $\mu C_{ox}$  through the equation:

$$\beta_{\text{eff}} = \mu C_{ox} \frac{W}{L}$$

where  $W = 10\mu\text{m}$ ,  $L = 1\mu\text{m}$ , and the aspect ratio  $\frac{W}{L} = 10$ . This relationship is based on the effective beta values obtained from the Cadence simulation results.

**NMOS  $\mu_n C_{ox}$  Calculation**

$$\beta_{\text{eff, NMOS}} \approx 3 \text{ mA/V}^2$$

$$\mu_n C_{ox} = \frac{\beta_{\text{eff, NMOS}}}{\frac{W}{L}}$$

$$\mu_n C_{ox} = \frac{3 \text{ mA/V}^2}{10}$$

$$\mu_n C_{ox} = 0.3 \text{ mA/V}^2$$

**PMOS  $\mu_p C_{ox}$  Calculation**

$$\beta_{\text{eff, PMOS}} \approx 3 \text{ mA/V}^2$$

$$\mu_p C_{ox} = \frac{\beta_{\text{eff, PMOS}}}{\frac{W}{L}}$$

$$\mu_p C_{ox} = \frac{3 \text{ mA/V}^2}{10}$$

$$\mu_p C_{ox} = 0.3 \text{ mA/V}^2$$

**2.4 Details of the Calculation and Device Sizes****2.4.1 LC Tank Design**

The oscillation frequency is determined by the LC tank:

$$\omega_0 = \frac{1}{\sqrt{L_{\text{tank}} C_{\text{tank}}}} \quad (1)$$

where  $L_{\text{tank}}$  is a non-ideal inductor with a quality factor ( $Q$ ) of 10, and  $C_{\text{tank}}$  includes the varactor capacitance ( $C_{\text{var}}$ ) and parasitic capacitances ( $C_{\text{par}}$ ) from transistors and the inductor. Rearranging for  $C_{\text{tank}}$ :

$$C_{\text{tank}} = \frac{1}{\omega_0^2 L_{\text{tank}}} \quad (2)$$

For  $f_0 = 3\text{GHz}$ :

$$\omega_0 = 2\pi \times 3 \times 10^9 \approx 1.885 \times 10^{10} \text{ rad/s} \quad (3)$$

Initially, I chose the  $L = 1\text{nH}$ , but in the later steps it will produce negative capacitance that's why I chose  $L = \text{nH}$ . Given  $L_{\text{tank}} = 2\text{nH}$ :

$$C_{\text{tank}} = \frac{1}{(1.885 \times 10^{10})^2 \times 2 \times 10^{-9}} \approx 1.407\text{pF} \quad (4)$$

**2.4.2 Tuning Range 20%(2.7 GHz to 3.3 GHz)**

$$C_{\text{tank,max}} = \frac{1}{(2\pi \times 2.7 \times 10^9)^2 \times 2 \times 10^{-9}} \approx 1.74\text{pF} \quad (5)$$

$$C_{\text{tank,min}} = \frac{1}{(2\pi \times 3.3 \times 10^9)^2 \times 2 \times 10^{-9}} \approx 1.16\text{pF} \quad (6)$$

Assuming parasitic capacitance  $C_{\text{par}} \approx 10\text{fF}$ : we are not using external capacitance to replace  $C_{1,2}$ . So we can use  $C_{1,2} = 500\text{fF}$

$$C_{\text{var}} = C_{\text{tank}} - C_{\text{par}} - 2 \times C_{1,2} \quad (7)$$

$$C_{\text{var,min}} = 1.74 - 0.01 - 2 \times 0.5 = 0.73\text{fF}, \quad \text{at } f_{\text{max}} = 3.3 \text{ GHz}, \quad (8)$$

$$C_{\text{var,max}} = 1.16 - 0.01 - 2 \times 0.5 = 0.15\text{fF}, \quad \text{at } f_{\text{min}} = 2.7 \text{ GHz}. \quad (9)$$

**2.4.3 Varactor Size calculation( $M_{V1}$ ,  $M_{V2}$ )**

Each varactor contributes  $C_{\text{var}}/2$  since they are in parallel:

$$C_{\text{var,per}} = \frac{C_{\text{var}}}{2} \quad (10)$$

$$C_{\text{var,per,max}} = \frac{0.73}{2} \approx 365fF \quad (11)$$

$$C_{\text{var,per,min}} = \frac{0.15}{2} \approx 75fF \quad (12)$$

Capacitance formula:

$$C_{\text{var}} = \varepsilon_{\text{ox}} \frac{W \cdot L}{t_{\text{ox}}} \quad (13)$$

Where :

\*  $\varepsilon_{\text{ox}} \approx 3.9 \times 8.85 \times 10^{-12} \text{ F/m}$  (for SiO<sub>2</sub>)

\*  $t_{\text{ox}} \approx 1\text{nm}$  (typical for 45nm process)

\*  $W \cdot L$  is the gate area

$$C_{\text{var}} = \frac{3.45 \times 10^{-11} \cdot W \cdot L}{1 \times 10^{-9}} = 3.45 \times 10^{-2} \cdot W \cdot L \quad (14)$$

Solving for  $W \cdot L$ :

$$C_{\text{var,per,min}} = 365fF \quad (15)$$

$$W \cdot L = \frac{365 \times 10^{-15}}{3.45 \times 10^{-2}} = 105.79 \times 10^{-13} \approx 10.6 \times 10^{-12} \text{ m}^2 \quad (16)$$

Setting  $L = 1\mu\text{m}$ :

$$W = \frac{10.6 \times 10^{-12} \text{ m}^2}{1\mu\text{m}^2} = 10\mu\text{m} \quad (17)$$

Thus, Varactor Dimensions:  $W = 10\mu\text{m}$ ,  $L = 1\mu\text{m}$ .

#### 2.4.4 Calculation of Tank Loss $R_p$

The tank loss resistance is modelled by  $R_p$  with a quality factor of inductor Q=10:

$$R_p = Q \cdot \omega_0 \cdot L_{\text{tank}} \quad (18)$$

$$R_p = 10 \times (1.885 \times 10^{10}) \times (2 \times 10^{-9}) \approx 377\Omega \quad (19)$$

#### 2.4.5 Calculation of Transistor Size ( $M_1, M_2$ )

The cross-coupled NMOS pair provides a negative resistance, which is essential for sustaining oscillation in a circuit such as an oscillator. This negative resistance is approximated as:

$$R_{\text{neg}} \approx \frac{-2}{g_m} \quad (20)$$

Ensuring oscillation:

$$g_m R_p \geq 1 \Rightarrow g_m \geq \frac{1}{R_p} = \frac{1}{377} \approx 2.65mS \quad (21)$$

For design purposes and to include a safety margin, we set the requirement as:

$$g_m \geq 2.65mS \quad (22)$$

$$g_m > 2mS \quad (23)$$

The drain current  $I_D$  for a MOSFET in saturation is given by:

$$I_D = \frac{1}{2} \mu C_{\text{ox}} \frac{W}{L} (V_{GS} - V_t)^2 \quad (24)$$

Transconductance relation:

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{GS} - V_t) \quad (25)$$

Solving for  $I_D$ :

$$g_m^2 = 2\mu C_{\text{ox}} \frac{W}{L} I_D \quad (26)$$

$$I_D = \frac{g_m^2}{2\mu C_{\text{ox}} \frac{W}{L}} \quad (27)$$

Given  $\mu C_{\text{ox}} \approx 0.3 \times 10^{-3}$  A/V<sup>2</sup> and  $g_m \approx 2mS$ :

$$I_D = \frac{(2 \times 10^{-3})^2}{2 \times 0.3 \times 10^{-3} \times 5} \approx 66.667 \mu A \quad (28)$$

$$I_{SS} = 2I_D \approx 133.33 \mu A \quad (29)$$

Setting  $W/L = 100$ :

$$M_1, M_2 : W = 5 \mu m, L = 50 nm \quad (30)$$

$$(31)$$

## 2.5 Summary of Calculated Values

**Summary of Calculated Values**

Parameter	Approximated	Chosen	Unit
Length of $M_{1,2}$	50	50	nm
Width of $M_{1,2}$	5	5	$\mu m$
Length of varactors $M_{v1,v2}$	1	2	$\mu m$
Width of varactors $M_{v1,v2}$	10	5	$\mu m$
Inductance $L_1$	1	3	nH
Capacitance $C_1$	500	720	fF
Resistance $R_p$	500	470	$\omega$
Bias current $I_{bias}$	133.33	800	$\mu A$
Control voltage $V_{cont}$	-	500	mV

**Summary of Calculated Values of Transistors**

Transistor	Length	Width	Unit
$M_1$	0.05	5	$\mu m$
$M_2$	0.05	5	$\mu m$
$M_{V1}$	1	10	$\mu m$
$M_{V2}$	1	10	$\mu m$

### 3 SIMULATION RESULTS FOR A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTORS

#### 3.1 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

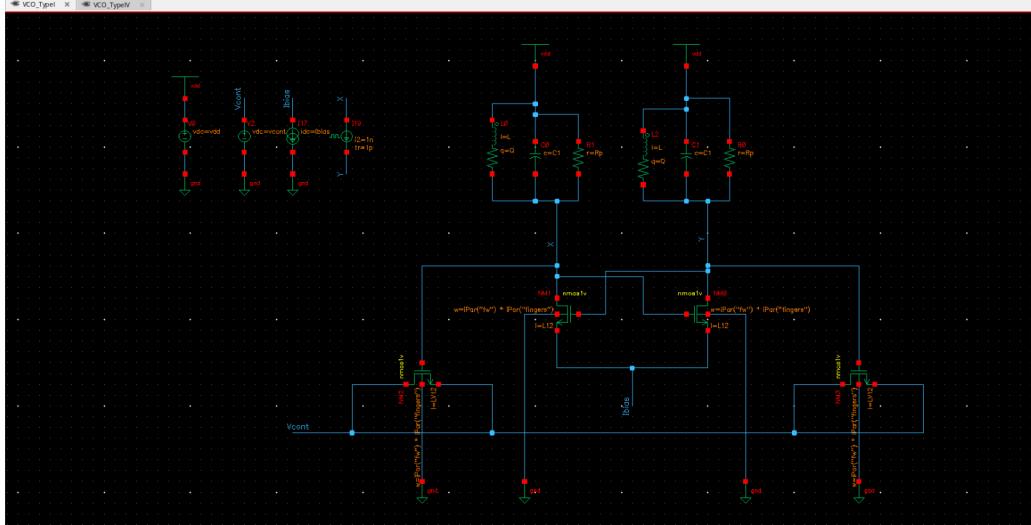


Figure 4 — Circuit diagram of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

To start the oscillation, a brief signal pulse was introduced with the following characteristics: Current 1 was set to 0 A, Current 2 to 1 mA, a rise time of 1 ps, a fall time of 1 ps, and a pulse width of 3 ps. All other parameters were configured based on the values specified in the table in the end of previous chapter.

##### 3.1.1 Transient simulation results (up to 10 ns after steady state)

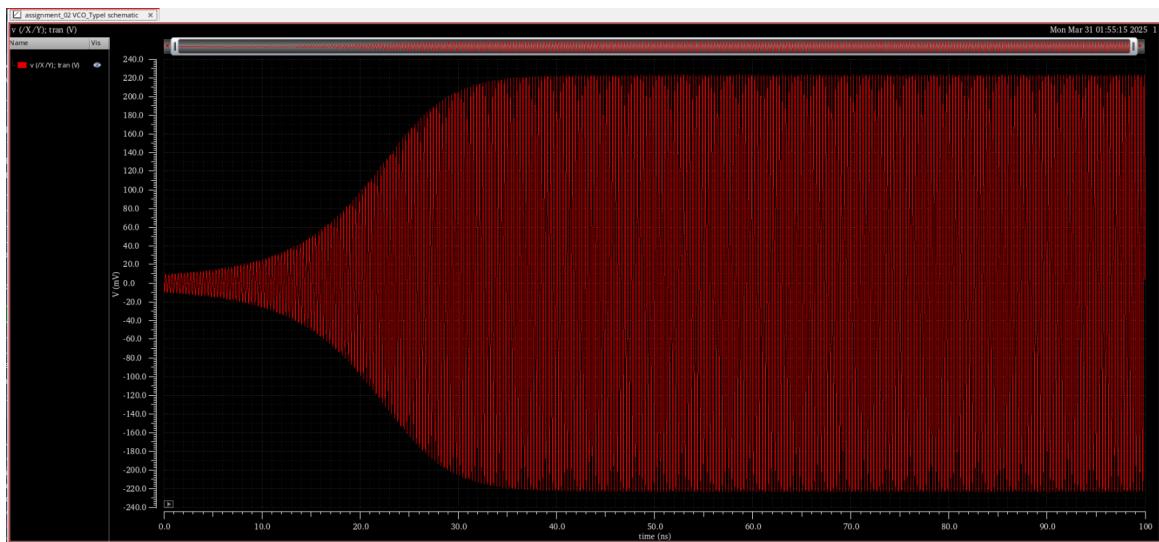


Figure 5 — A transient simulation of  $V_x - V_y$  was performed with  $V_{cont}$  set to 250mV, resulting in a peak-to-peak value of 446.1mV.a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

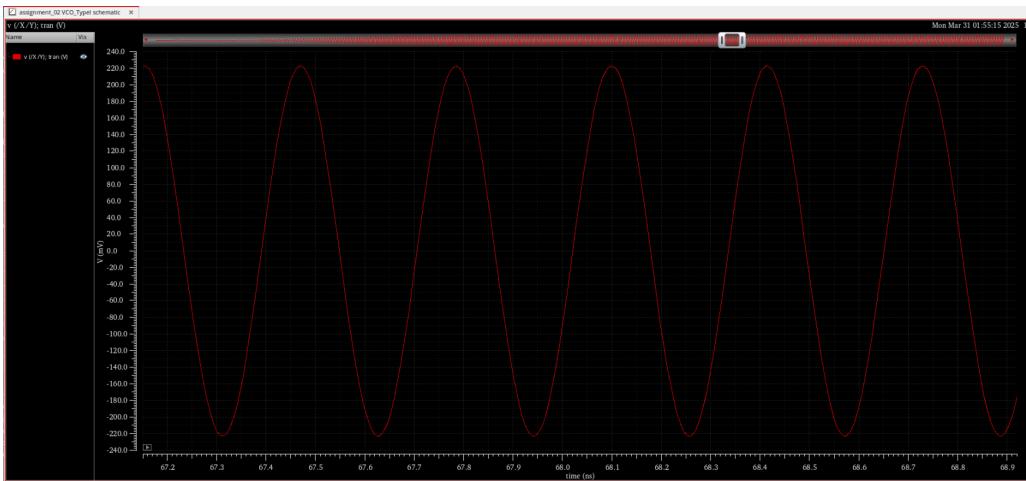


Figure 6 — Transient simulation of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

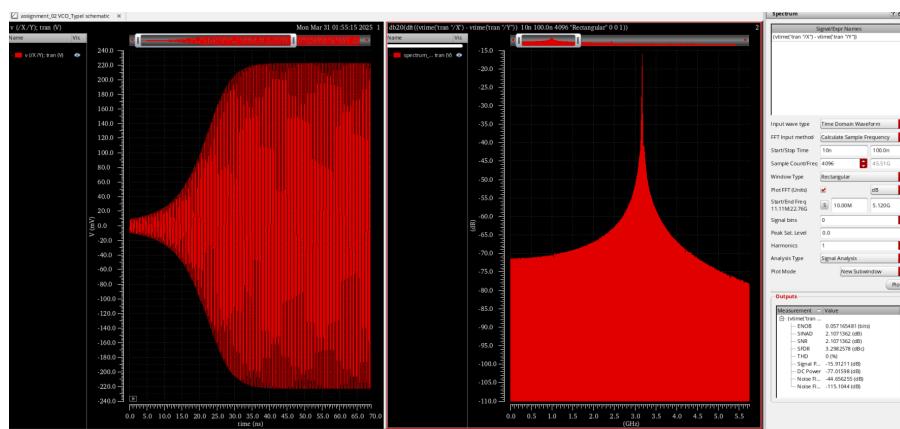


Figure 7 — A transient simulation of  $V_X - V_Y$  was conducted with  $V_{cont}$  set to 500mV, and FFT analysis indicated an oscillation frequency of 3.048 GHz.

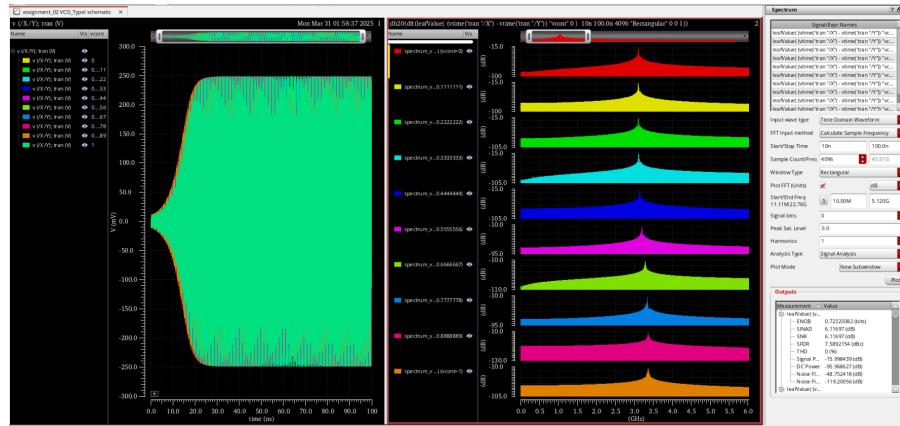


Figure 8 — Transient simulation of  $V_X - V_Y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$  of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

### 3.1.2 Parametric simulation results of frequency of oscillation ( $f_0$ ) vs. control voltage ( $V_{cont}$ )

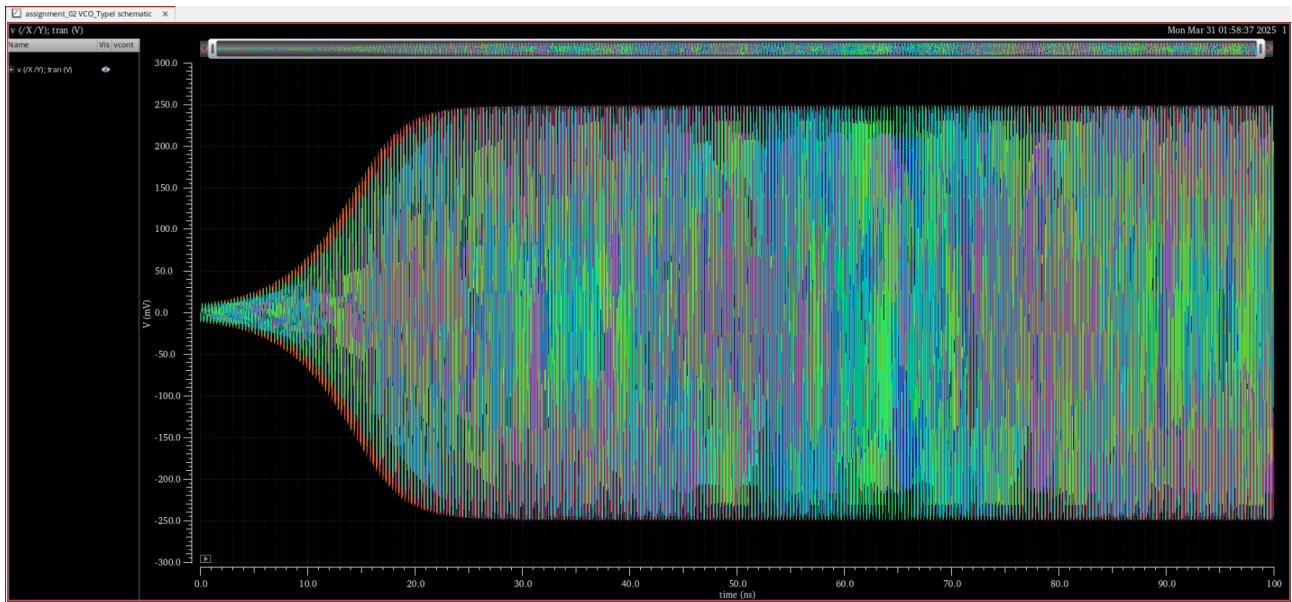


Figure 9 — Transient simulation of  $V_x - V_y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$  of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

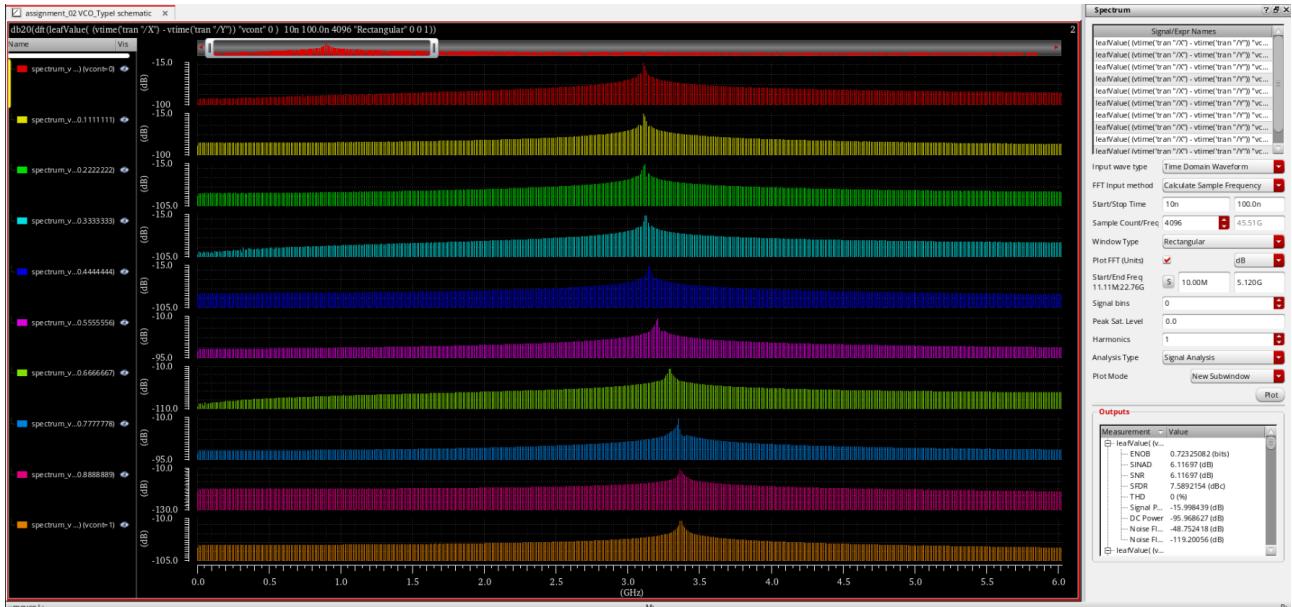


Figure 10 — Transient simulation of  $V_x - V_y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$  of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

The oscillation frequency  $f_{osc}$  increases with  $V_{cont}$  as a result of the VCO's positive gain.

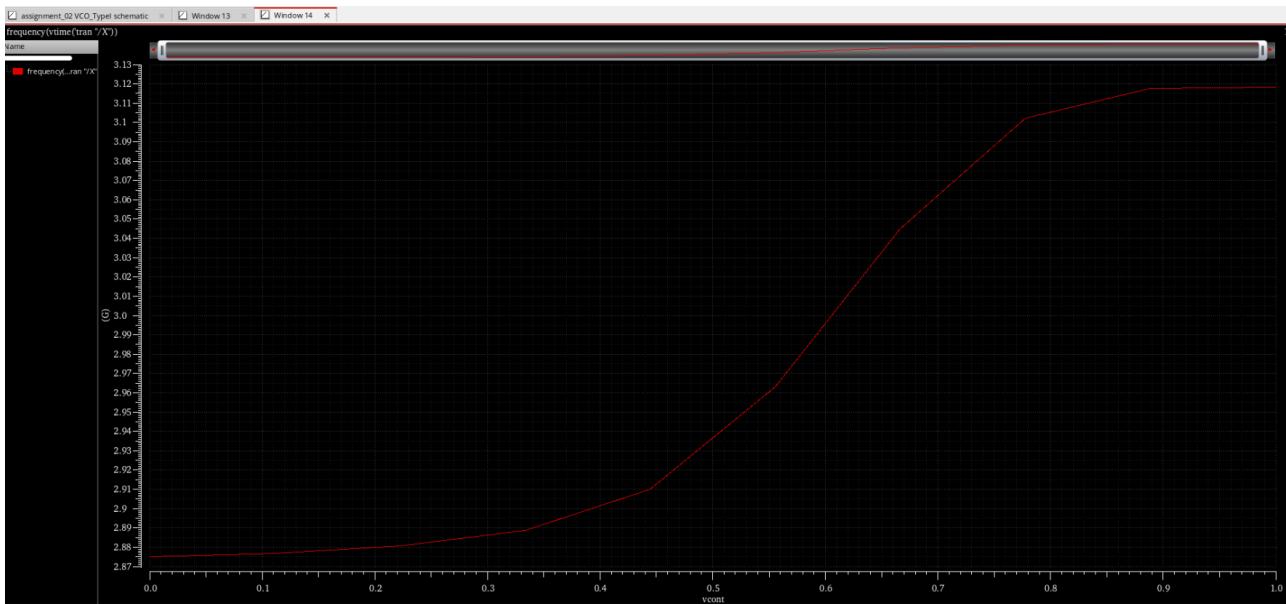


Figure 11 — The relationship between the oscillation frequency ( $f_0$ ) and the control voltage ( $V_{cont}$ ) of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

### 3.1.3 Periodic steady-state (PSS) simulation



Figure 12 — A PSS simulation of  $V_X - V_Y$  was performed at  $V_{cont} = 500\text{mV}$ , revealing a first harmonic frequency of 3.06 GHz of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

### 3.1.4 Phase noise (PS) simulation results.

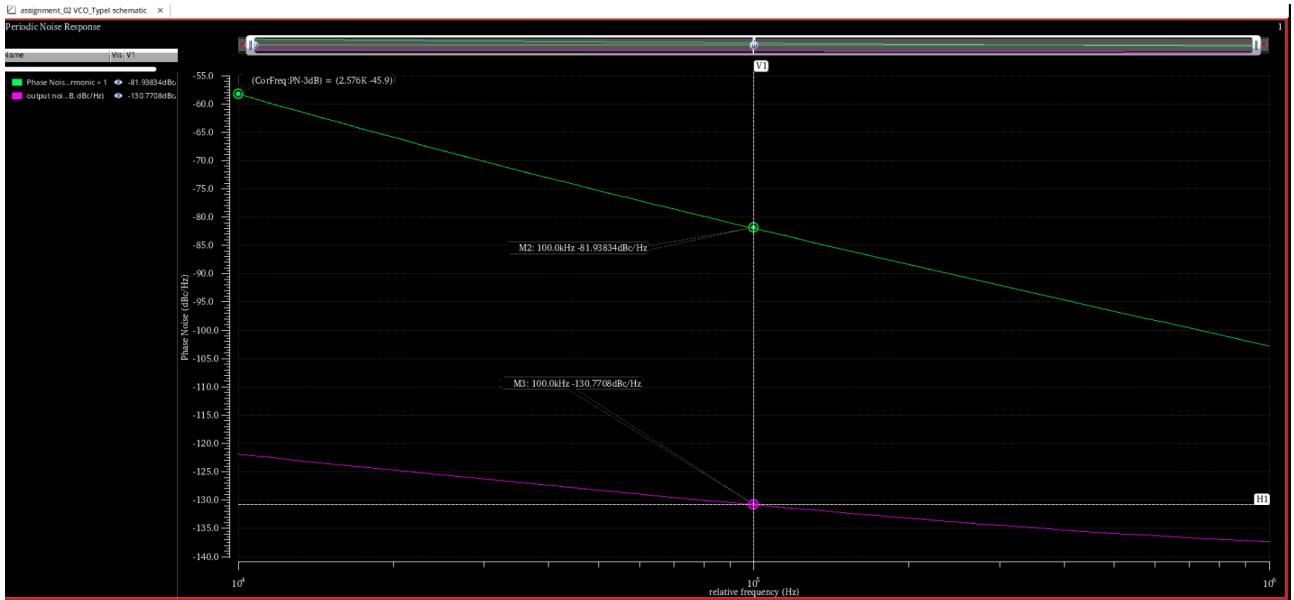


Figure 13 — PSS simulation results: The green curve represents Phase Modulation (PM), while the purple curve corresponds to Amplitude Modulation (AM) of a type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

## 3.2 Discussion on Type IV Fully Differential CC LC-VCO

### 3.2.1 Tuning Range

\* Center Frequency:

$$f_{\text{center}} = \frac{f_{\max} + f_{\min}}{2} = \frac{3.117 + 2.875}{2} = 2.996 \text{ GHz} \quad (32)$$

\* Total Tuning Range:

$$\frac{f_{\max} - f_{\min}}{f_{\text{center}}} \times 100\% = \frac{3.117 - 2.875}{2.996} \times 100\% = 8.077\% \quad (33)$$

\* Frequency Deviation:

$$\pm 4.03\%, \text{ so the frequency spans } 2.996 \pm (0.0403 \times 2.996) = 2.9775 \pm 0.121 \text{ GHz} \quad (34)$$

\* The wide tuning range is achieved through MOS varactors' capacitance swing and a symmetric inductor, ensuring balanced operation.

### 3.2.2 VCO Gain ( $K_{VCO}$ )

\* Defined as:

$$K_{VCO} = \frac{\Delta f}{\Delta V_{\text{cont}}}, \quad \text{where} \quad \Delta f \propto \frac{1}{L(C_{\text{var}}(V_{\text{cont}}))} \quad (35)$$

\* Using two selected points from the  $f_0$  vs.  $V_{\text{cont}}$  curve:

- At  $V_{\text{cont}} = 542.82$  mV,  $f = 3.1938$  GHz.
- At  $V_{\text{cont}} = 720.91$  mV,  $f = 3.3198$  GHz.

\* The gradient calculation:

$$K_{VCO} = \frac{f_2 - f_1}{V_{\text{cont}_2} - V_{\text{cont}_1}} = \frac{3.3198 - 3.1938}{0.72091 - 0.54282} = 0.7075 \text{ GHz/V} \quad (36)$$

\* Since  $K_{VCO} > 0$ , the VCO exhibits positive gain.

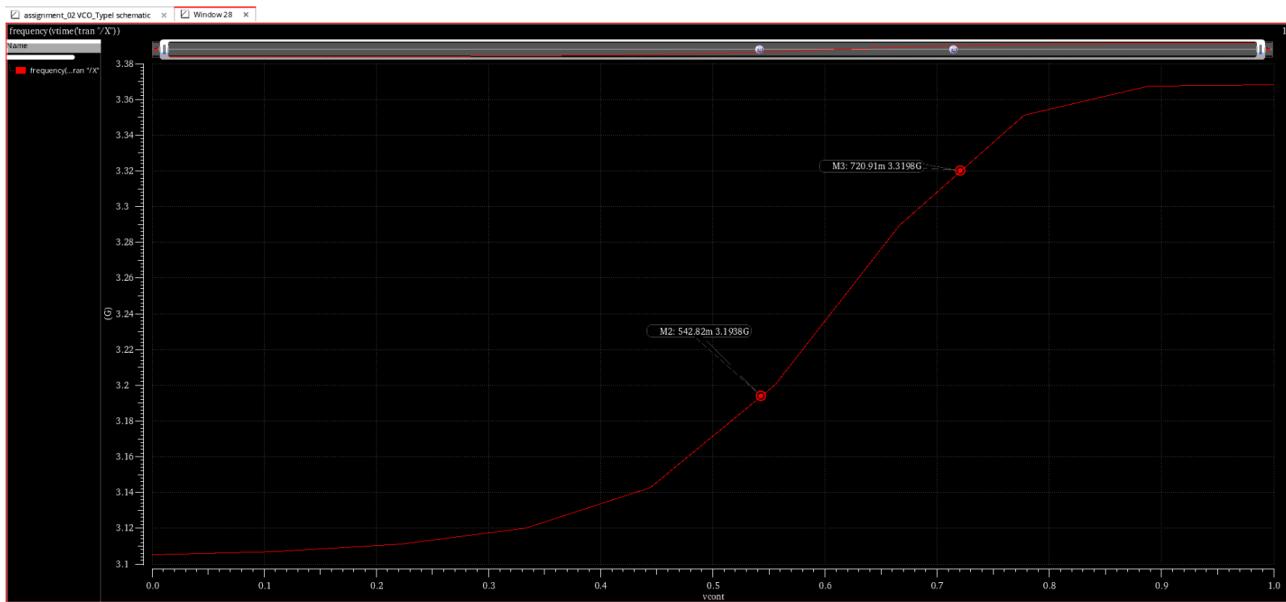


Figure 14 — Calculation of  $K_{VCO}$  from the  $V_{cont}$  vs.  $f_0$  curve.

### 3.2.3 Output Voltage Swing

- \* The maximum swing reaches approximately 446.1 mV, which is nearly half of VDD.

### 3.2.4 Noise Performance (Phase & Amplitude)

- \* At a **100 kHz** offset from the carrier:

- **Phase Modulation (PM) Noise:**  $-81.9383 \text{ dBc/Hz}$
- **Amplitude Modulation (AM) Noise:**  $-130.7708 \text{ dBc/Hz}$

- \* The phase noise analysis indicates that **amplitude modulation (AM) noise is significantly lower compared to phase modulation (PM) noise.**

## 4 DESIGN METHODOLOGY AND DETAILS OF THE CALCULATION AND DEVICE SIZES OF A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR

### 4.1 VCO Design Specifications

#### VCO Design Specifications

Parameter	Specification
Technology Node	45 nm CMOS
Supply Voltage $V_{DD}$	1 V
Nominal Input Common-Mode Voltage $V_{DD}/2$	0.5 V
Bias Current $I_{bias}$	10 $\mu$ A (adjustable)
Oscillation Frequency $f_0$	3 GHz
Tuning Range	> 20% (2.7 GHz – 3.3 GHz)
VCO Gain $K_{VCO}$	To be determined (? GHz/V)
Varactor Type	MOS Varactor
Inductor Configuration	Symmetric Inductor (for Type IV VCO)

### 4.2 A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

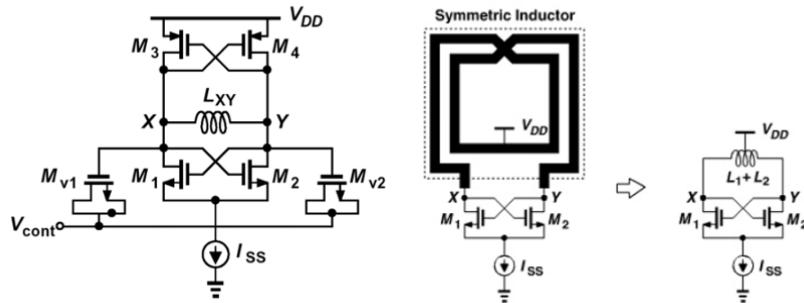


Figure 15 — A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

The Type IV Cross-Coupled Differential LC Voltage-Controlled Oscillator (VCO) is a widely used design in RF applications, incorporating MOS varactors and a symmetric inductor to achieve stable oscillations with low phase noise. It consists of a cross-coupled NMOS transistor pair ( $M_1, M_2$ ) that generates negative resistance, compensating for losses in the LC tank circuit formed by the inductor ( $L_{XY}$ ) and the MOS varactors ( $M_{v1}, M_{v2}$ ). A symmetric inductor is employed to ensure balanced operation, minimizing phase noise and improving oscillator performance. The circuit also includes a PMOS cross-coupled pair ( $M_3, M_4$ ) to enhance negative resistance, facilitating reliable startup. The oscillation frequency is determined by the LC tank and can be tuned by adjusting the control voltage ( $V_{cont}$ ), which modulates the capacitance of the varactors. The bias current source ( $I_{SS}$ ) sets the oscillation amplitude, ensuring stable operation. The equivalent circuit representation simplifies the design, showing how the symmetric inductor can be viewed as two coupled inductors ( $L_1 + L_2$ ), preserving differential operation. This VCO architecture is commonly used in RF

transceivers, phase-locked loops (PLLs), and high-frequency communication systems due to its efficient frequency tuning and low phase noise characteristics.

### 4.3 Pre-Calculations

#### 4.3.1 Transistor Parameters from Cadence Simulation

The following parameters are obtained from Cadence simulation for NMOS and PMOS design with channel length  $L = 1\mu\text{m}$  (to minimize the channel length modulation) and width  $W = 10\mu\text{m}$  for both NMOS and PMOS transistors. The supply voltage is  $V_{DD} = 1\text{V}$ , and the bias current is  $I_o = 10\mu\text{A}$ .

Referefnce : - How to find process parameter of any technology node

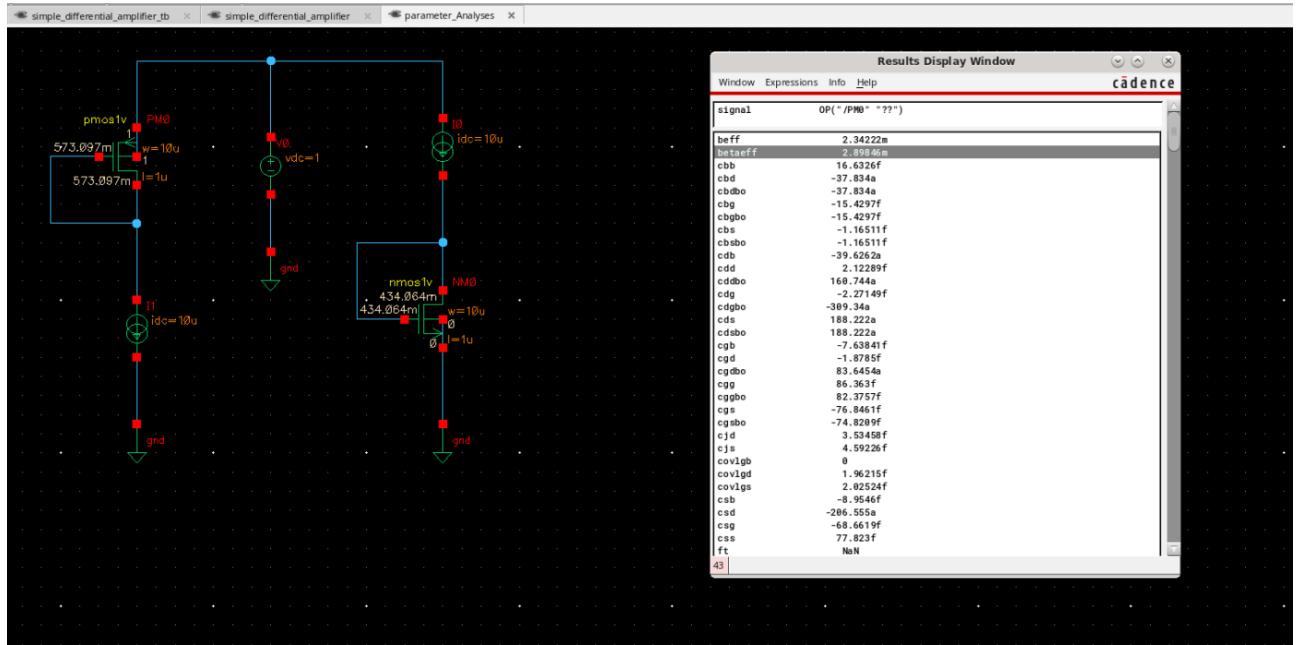


Figure 16 — Transistor Parameters from Cadence Simulation

#### NMOS Parameters

- \* Effective Beta ( $\beta_{\text{eff, NMOS}}$ ):  $2.89846 \text{ mA/V}^2$  (rounded to  $3 \text{ mA/V}^2$ )
- \* Threshold Voltage ( $V_{\text{th, NMOS}}$ ):  $397.975 \text{ mV}$  (rounded to  $0.4 \text{ V}$ )

#### PMOS Parameters

- \* Effective Beta ( $\beta_{\text{eff, PMOS}}$ ):  $2.89846 \text{ mA/V}^2$  (rounded to  $3 \text{ mA/V}^2$ )
- \* Threshold Voltage ( $V_{\text{th, PMOS}}$ ):  $-334.497 \text{ mV}$  (rounded to  $-0.3 \text{ V}$ )

#### 4.3.2 Calculation of $\mu C_{ox}$ for NMOS and PMOS

The effective beta ( $\beta_{\text{eff}}$ ) is related to the process transconductance parameter  $\mu C_{ox}$  by the following equation:

$$\beta_{\text{eff}} = \mu C_{ox} \frac{W}{L} \quad (37)$$

where  $W = 10 \mu\text{m}$ ,  $L = 1 \mu\text{m}$ , and  $\frac{W}{L} = 10$ .

Using the approximated effective beta values from the Cadence simulation:

**NMOS  $\mu_n C_{ox}$  Calculation**

$$\beta_{\text{eff, NMOS}} \approx 3 \text{ mA/V}^2$$

$$\mu_n C_{ox} = \frac{\beta_{\text{eff, NMOS}}}{\frac{W}{L}}$$

$$\mu_n C_{ox} = \frac{3 \text{ mA/V}^2}{10}$$

$$\mu_n C_{ox} = 0.3 \text{ mA/V}^2$$

**PMOS  $\mu_p C_{ox}$  Calculation**

$$\beta_{\text{eff, PMOS}} \approx 3 \text{ mA/V}^2$$

$$\mu_p C_{ox} = \frac{\beta_{\text{eff, PMOS}}}{\frac{W}{L}}$$

$$\mu_p C_{ox} = \frac{3 \text{ mA/V}^2}{10}$$

$$\mu_p C_{ox} = 0.3 \text{ mA/V}^2$$

**4.4 Details of the Calculation and Device Sizes****4.4.1 LC Tank Design**

The oscillation frequency is determined by the LC tank:

$$\omega_0 = \frac{1}{\sqrt{L_{\text{tank}} C_{\text{tank}}}} \quad (38)$$

where  $L_{\text{tank}}$  is a non-ideal inductor with a quality factor ( $Q$ ) of 10, and  $C_{\text{tank}}$  includes the varactor capacitance ( $C_{\text{var}}$ ) and parasitic capacitances ( $C_{\text{par}}$ ) from transistors and the inductor. Rearranging for  $C_{\text{tank}}$ :

$$C_{\text{tank}} = \frac{1}{\omega_0^2 L_{\text{tank}}} \quad (39)$$

For  $f_0 = 3\text{GHz}$ :

$$\omega_0 = 2\pi \times 3 \times 10^9 \approx 1.885 \times 10^{10} \text{ rad/s} \quad (40)$$

Given  $L_{\text{tank}} = 10nH$ :

$$C_{\text{tank}} = \frac{1}{(1.885 \times 10^{10})^2 \times 10 \times 10^{-9}} \approx 281.45fF \quad (41)$$

**4.4.2 Tuning Range 20%(2.7 GHz to 3.3 GHz)**

$$C_{\text{tank,max}} = \frac{1}{(2\pi \times 2.7 \times 10^9)^2 \times 10 \times 10^{-9}} \approx 347.47fF \quad (42)$$

$$C_{\text{tank,min}} = \frac{1}{(2\pi \times 3.3 \times 10^9)^2 \times 10 \times 10^{-9}} \approx 232.60fF \quad (43)$$

Assuming parasitic capacitance  $C_{\text{par}} \approx 10fF$ :

$$C_{\text{var}} = C_{\text{tank}} - C_{\text{par}} \quad (44)$$

$$(45)$$

$$C_{\text{var,min}} = 232.60 - 10 = 222.60fF, \quad \text{at } f_{\text{max}} = 3.3 \text{ GHz}, \quad (46)$$

$$C_{\text{var,max}} = 347.47 - 10 = 337.47fF, \quad \text{at } f_{\text{min}} = 2.7 \text{ GHz}. \quad (47)$$

**4.4.3 Varactor Size calculation ( $M_{V1}, M_{V2}$ )**

Each varactor contributes  $C_{\text{var}}/2$  since they are in parallel:

$$C_{\text{var,per}} = \frac{C_{\text{var}}}{2} \quad (48)$$

$$C_{\text{var,per,min}} = \frac{222.60}{2} \approx 111.30 fF \quad (49)$$

$$C_{\text{var,per,max}} = \frac{337.47}{2} \approx 168.735 fF \quad (50)$$

Capacitance formula:

$$C_{\text{var}} = \varepsilon_{\text{ox}} \frac{W \cdot L}{t_{\text{ox}}} \quad (51)$$

Where :

\*  $\varepsilon_{\text{ox}} \approx 3.9 \times 8.85 \times 10^{-12} \text{ F/m}$  (for SiO<sub>2</sub>)

\*  $t_{\text{ox}} \approx 1 \text{ nm}$  (typical for 45nm process)

\*  $W \cdot L$  is the gate area

$$C_{\text{var}} = \frac{3.45 \times 10^{-11} \cdot W \cdot L}{1 \times 10^{-9}} = 3.45 \times 10^{-2} \cdot W \cdot L \quad (52)$$

Solving for  $W \cdot L$ :

$$C_{\text{var,per,max}} = 168.735 fF \quad (53)$$

$$W \cdot L = \frac{168.735 \times 10^{-15}}{3.45 \times 10^{-2}} = 48.9 \times 10^{-13} \approx 5 \times 10^{-12} \text{ m}^2 \quad (54)$$

Setting  $L = 1 \mu\text{m}$ :

$$W = \frac{5 \times 10^{-12} \text{ m}^2}{1 \mu\text{m}} = 5 \mu\text{m} \quad (55)$$

Thus, Varactor Dimensions:  $W = 5 \mu\text{m}$ ,  $L = 1 \mu\text{m}$ .

#### 4.4.4 Calculation of Tank Loss $R_p$

The tank loss resistance is modelled by  $R_p$  with a quality factor of inductor  $Q=10$ :

$$R_p = Q \cdot \omega_0 \cdot L_{\text{tank}} \quad (56)$$

$$R_p = 10 \times (1.885 \times 10^{10}) \times (10 \times 10^{-9}) \approx 1.885 k\Omega \quad (57)$$

#### 4.4.5 Calculation of Transistor Size ( $M_1, M_2$ )

The cross-coupled NMOS pair provides a negative resistance, which is essential for sustaining oscillation in a circuit such as an oscillator. This negative resistance is approximated as:

$$R_{\text{neg}} \approx \frac{-2}{g_m} \quad (58)$$

Ensuring oscillation:

$$g_m R_p \geq 1 \Rightarrow g_m \geq \frac{1}{R_p} = \frac{1}{1885} \approx 0.53 mS \quad (59)$$

For design purposes and to include a safety margin, we set the requirement as:

$$g_m R_p \geq 0.53 mS \quad (60)$$

The drain current  $I_D$  for a MOSFET in saturation is given by:

$$I_D = \frac{1}{2} \mu C_{\text{ox}} \frac{W}{L} (V_{GS} - V_t)^2 \quad (61)$$

Transconductance relation:

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{GS} - V_t) \quad (62)$$

Solving for  $I_D$ :

$$g_m^2 = 2\mu C_{\text{ox}} \frac{W}{L} I_D \quad (63)$$

$$I_D = \frac{g_m^2}{2\mu C_{\text{ox}} \frac{W}{L}} \quad (64)$$

Given  $\mu C_{\text{ox}} \approx 0.3 \times 10^{-3}$  A/V<sup>2</sup> and  $g_m \approx 0.53mS$ :

$$I_D = \frac{(0.53 \times 10^{-3})^2}{2 \times 0.3 \times 10^{-3} \times 5} \approx 100\mu A \quad (65)$$

$$I_{SS} = 2I_D \approx 200\mu A \quad (66)$$

Setting  $W/L = 5$ :

$$M_1, M_2 : W = 5\mu m, L = 1\mu m \quad (67)$$

$$M_3, M_4 : W = 10\mu m, L = 1\mu m \quad (68)$$

#### 4.5 Summary of Calculated Values

**Summary of Calculated Values**

Parameter	Approximated	Chosen	Unit
Length of $M_{1,2}$	1	1	$\mu m$
Width of $M_{1,2}$	5	5	$\mu m$
Length of $M_{3,4}$	1	1	$\mu m$
Width of $M_{3,4}$	10	10	$\mu m$
Length of varactors $M_{v1,v2}$	1	10	$\mu m$
Width of varactors $M_{v1,v2}$	5	10	$\mu m$
Inductance $L_1$	10	5	nH
Bias current $I_{bias}$	200	800	$\mu A$
Control voltage $V_{cont}$	-	320	mV

**Summary of Calculated Values of Transistors**

Transistor	Length	Width	Unit
$M_1$	1	5	$\mu m$
$M_2$	1	5	$\mu m$
$M_3$	1	10	$\mu m$
$M_4$	1	10	$\mu m$
$M_{V1}$	1	5	$\mu m$
$M_{V2}$	1	5	$\mu m$

## 5 SIMULATION RESULTS FOR A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR

### 5.1 A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

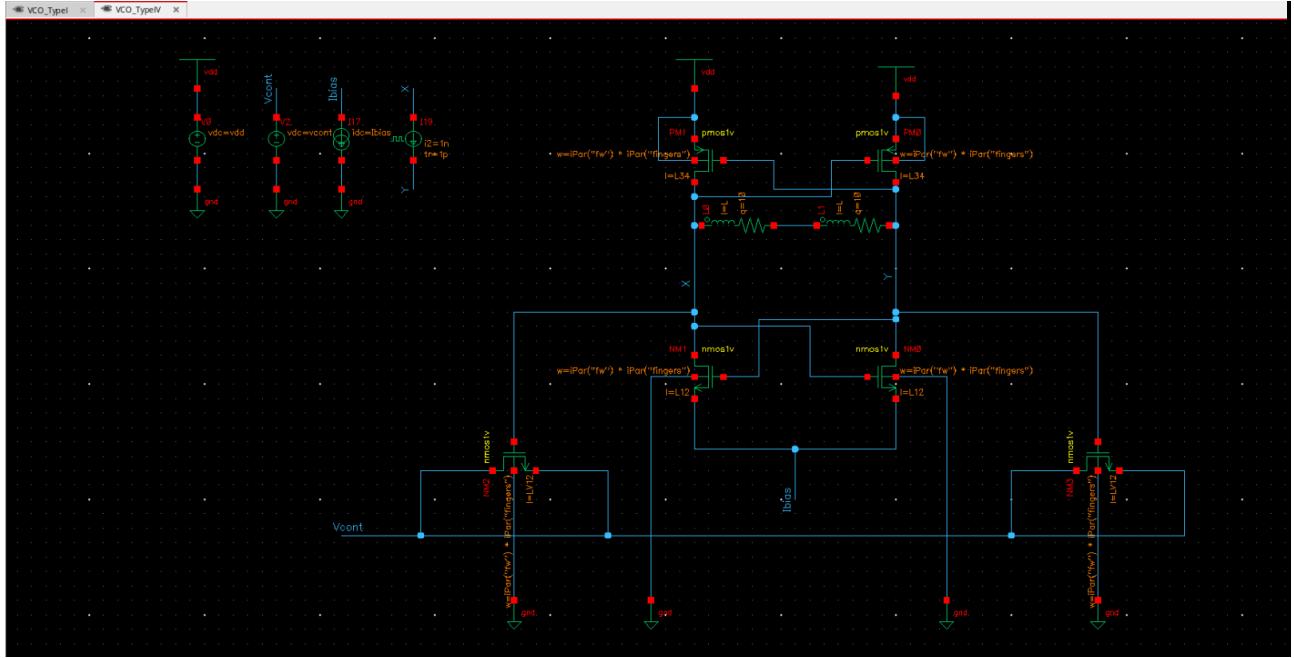


Figure 17 — A type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor  
a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

To start the oscillation, a short signal pulse was applied with the following characteristics: Current 1 set to 0 A, Current 2 set to 1 nA, a rise time of 1 ps, a fall time of 1 ps, and a pulse width of 3 ps. A symmetric 10 nH inductor was created by connecting two non-ideal inductors of 5 nH each in series. All other parameters were configured in the previous chapter.

#### 5.1.1 Transient simulation results (up to 10 ns after steady state)

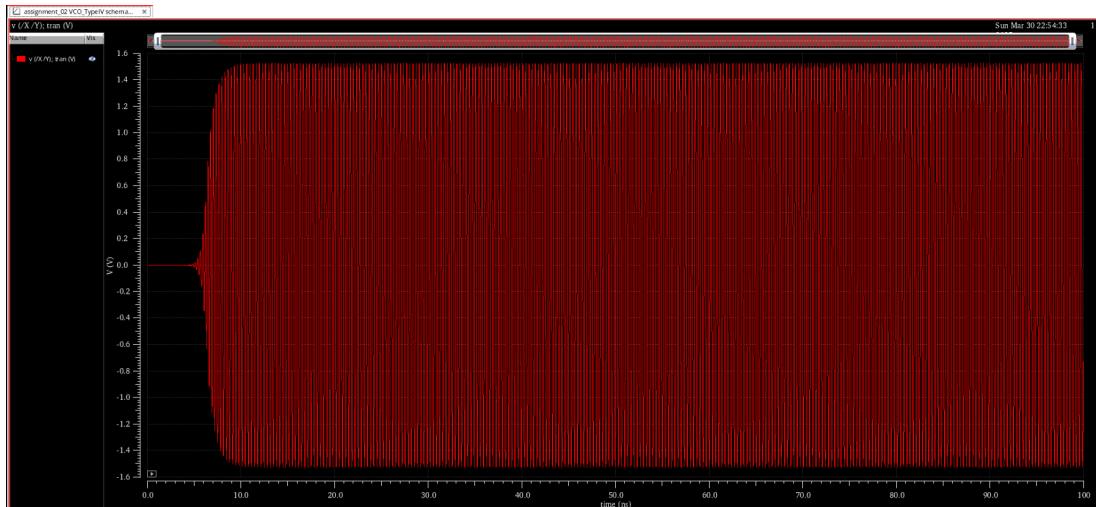


Figure 18 — Transient analysis of  $V_X - V_Y$  with a control voltage ( $V_{cont}$ ) of 320 mv with  $V_{pp}$  of 3.25V . of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

(Peak to peak is more than twice the value of VDD)

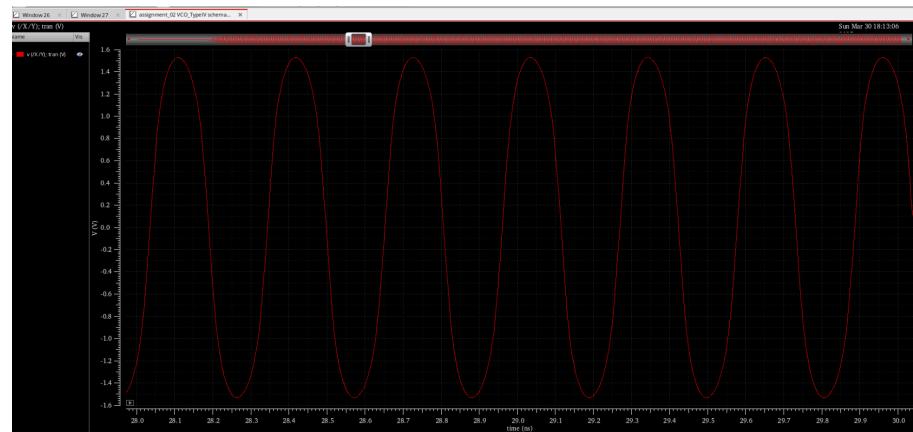


Figure 19 — Transient analysis of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

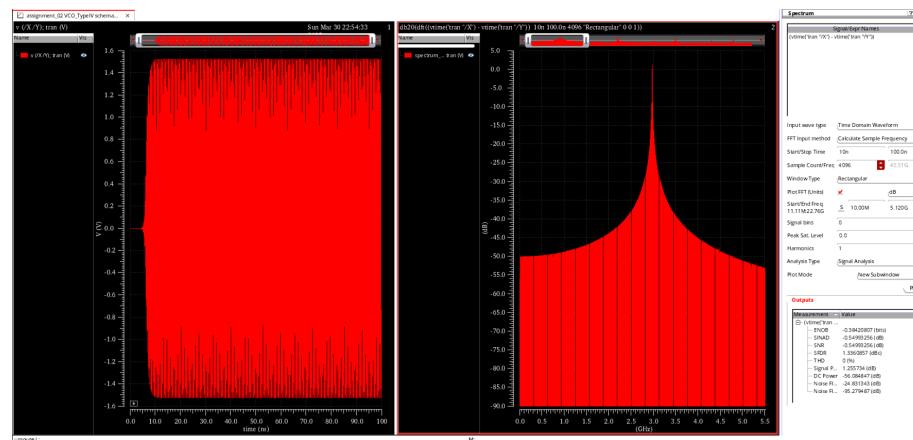


Figure 20 — Transient simulation of  $V_x - V_y$  with  $V_{cont} = 320, and FFT analysis reveals an oscillation frequency of 3.023 GHz of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor$

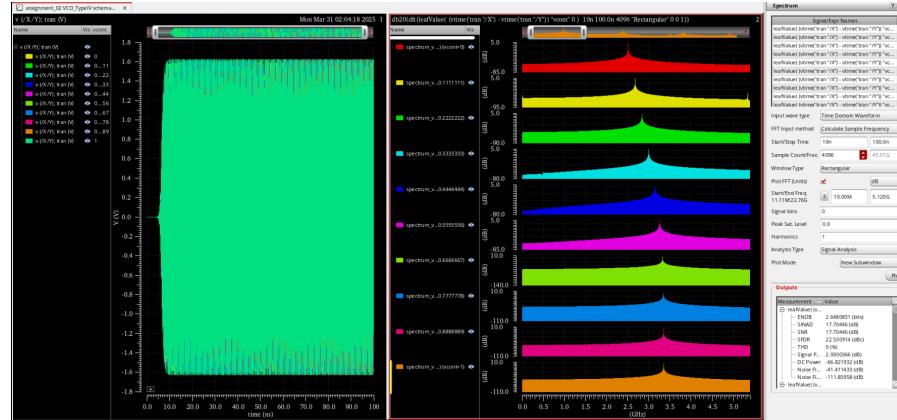


Figure 21 — Transient simulation of  $V_x - V_y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1\text{ V}$  of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

### 5.1.2 Parametric simulation results of frequency of oscillation ( $f_0$ ) vs. control voltage ( $V_{cont}$ )

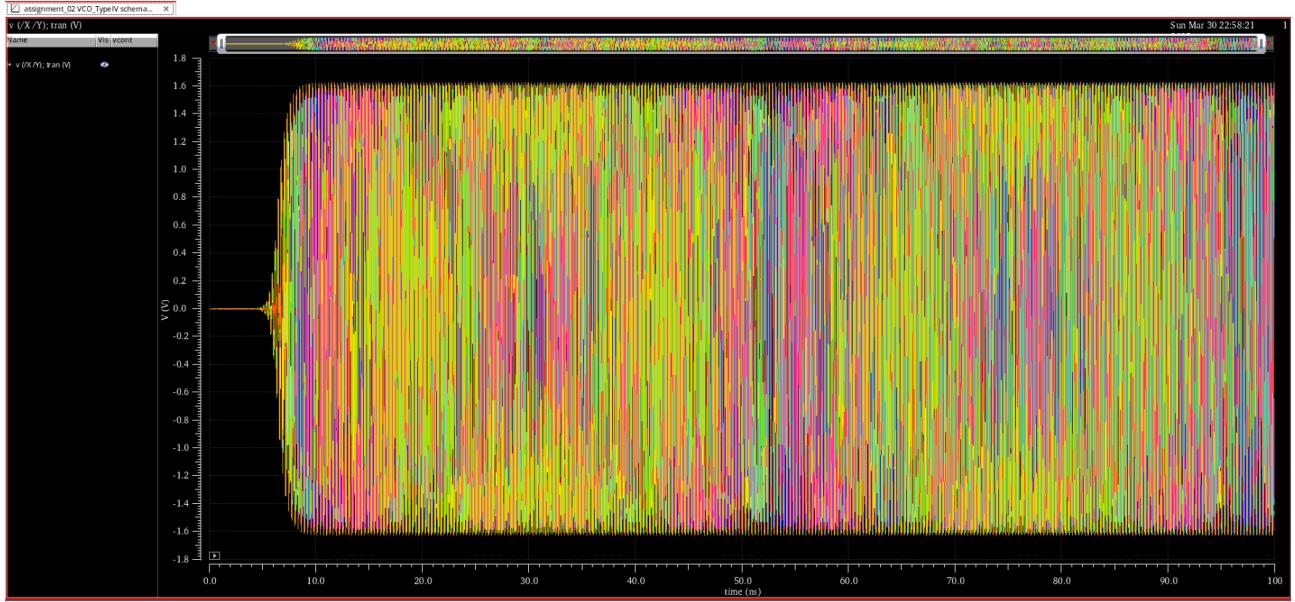


Figure 22 — Transient simulation of  $V_X - V_Y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$  of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

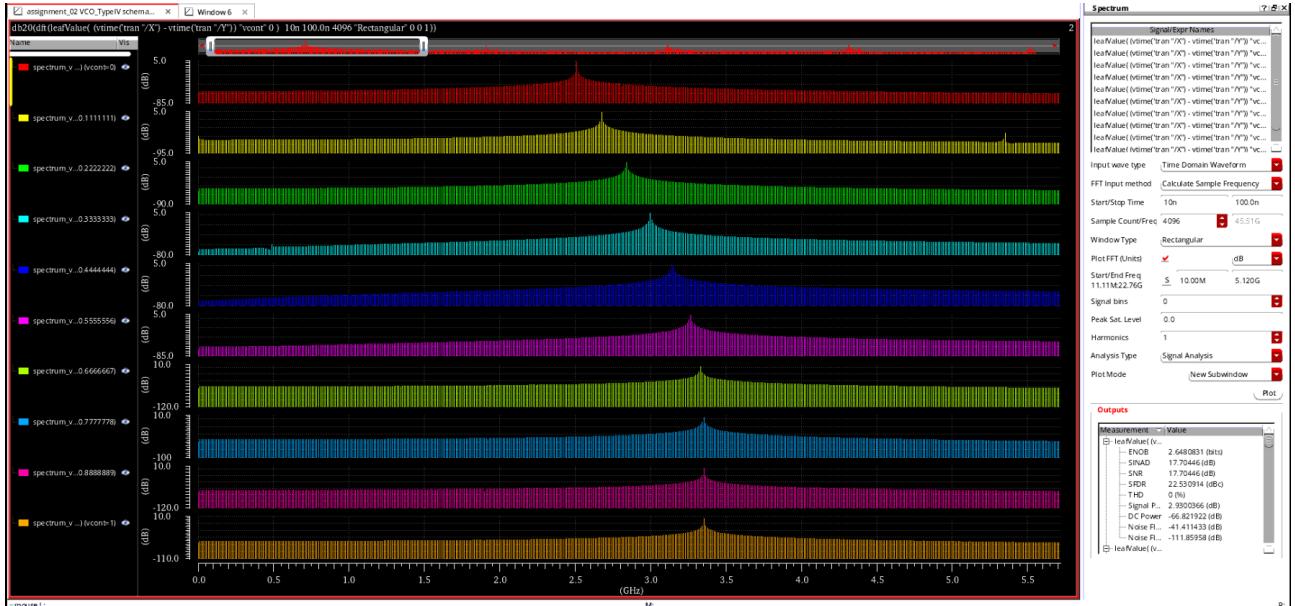


Figure 23 — Transient simulation of  $V_X - V_Y$  and FFT analysis for  $V_{cont} = 0, 0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1V$  of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

The oscillation frequency  $f_{osc}$  increases with  $V_{cont}$  as a result of the positive gain of the VCO.

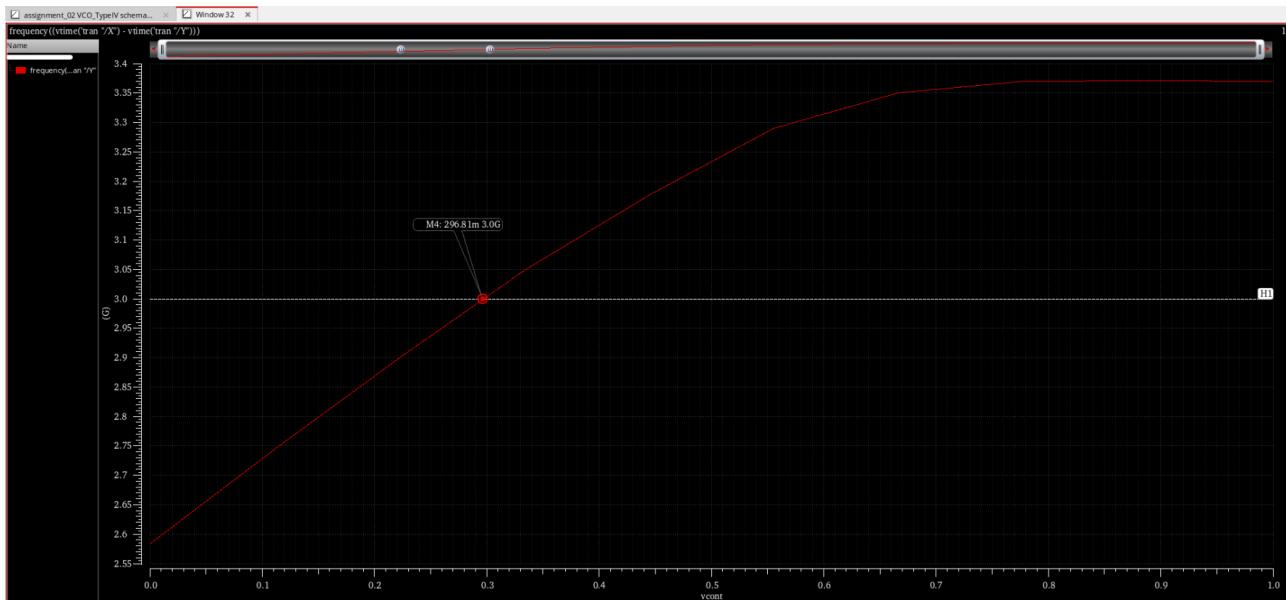


Figure 24 — Oscillation frequency ( $f_0$ ) as a function of control voltage ( $V_{cont}$ ) of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

### 5.1.3 Periodic steady-state (PSS) simulation



Figure 25 — PSS simulation of  $V_X - V_Y$  at  $V_{cont} = 500$  mV, indicating a first harmonic frequency of 2.989 GHz of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

### 5.1.4 Phase noise (PS) simulation results.

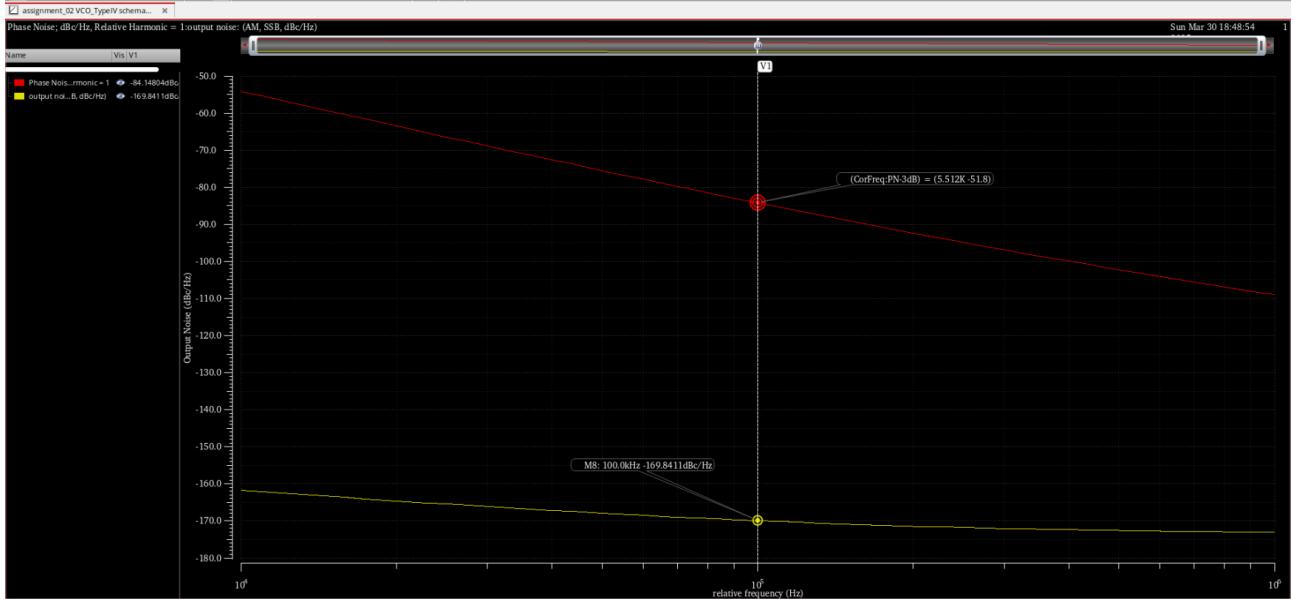


Figure 26 — PSS simulation results: The green curve represents Phase Modulation (PM), while the purple curve corresponds to Amplitude Modulation (AM) of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

## 5.2 Discussion on Type IV Fully Differential CC LC-VCO

### 5.2.1 Tuning Range

\* **Center Frequency:**

$$f_{\text{center}} = \frac{f_{\max} + f_{\min}}{2} = \frac{3.371 + 2.584}{2} = 2.9775 \text{ GHz} \quad (69)$$

\* **Total Tuning Range:**

$$\frac{f_{\max} - f_{\min}}{f_{\text{center}}} \times 100\% = \frac{3.371 - 2.584}{2.9775} \times 100\% = 26.43\% \quad (70)$$

\* **Frequency Deviation:**

$$\pm 13.2\%, \text{ so the frequency spans } 2.9775 \pm (0.132 \times 2.9775) = 2.9775 \pm 0.394 \text{ GHz} \quad (71)$$

\* The wide tuning range is achieved through MOS varactors' capacitance swing and a symmetric inductor, ensuring balanced operation.

### 5.2.2 VCO Gain ( $K_{VCO}$ )

\* Defined as:

$$K_{VCO} = \frac{\Delta f}{\Delta V_{\text{cont}}}, \quad \text{where} \quad \Delta f \propto \frac{1}{L(C_{\text{var}}(V_{\text{cont}}))} \quad (72)$$

\* Using two selected points from the  $f_0$  vs.  $V_{\text{cont}}$  curve:

- At  $V_{\text{cont}} = 50.9 \text{ mV}$ ,  $f = 2.658 \text{ GHz}$ .
- At  $V_{\text{cont}} = 555.56 \text{ mV}$ ,  $f = 3.2899 \text{ GHz}$ .

\* The gradient calculation:

$$K_{VCO} = \frac{f_2 - f_1}{V_{\text{cont}_2} - V_{\text{cont}_1}} = \frac{3.2899 - 2.658}{0.55556 - 0.0509} = 1.252 \text{ GHz/V} \quad (73)$$

\* Since  $K_{VCO} > 0$ , the VCO exhibits positive gain.

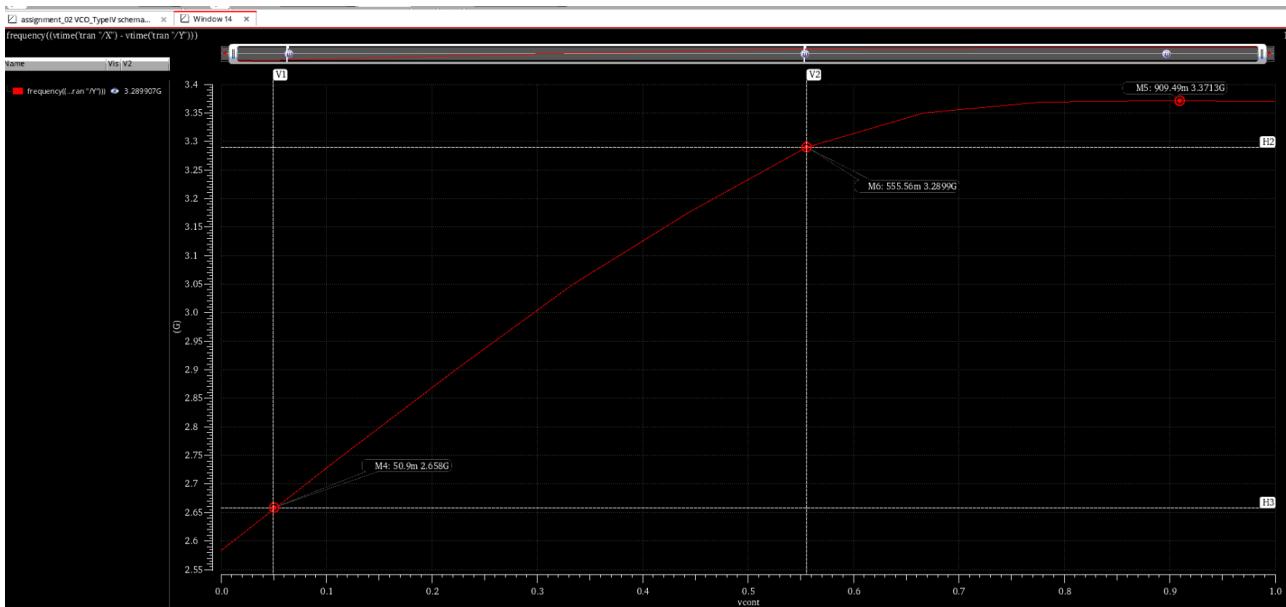


Figure 27 — Calculation of  $K_{VCO}$  from the  $V_{cont}$  vs.  $f_0$  curve.

### 5.2.3 Output Voltage Swing

- \* The peak-to-peak output voltage swing exceeds twice the supply voltage ( $V_{dd} = 1V$ ).
- \* Maximum peak-to-peak voltage:

$$3.25 \text{ V at } V_{cont} = 885.31 \text{ mV} \quad (74)$$

### 5.2.4 Noise Performance (Phase & Amplitude)

- \* At a **100 kHz** offset from the carrier:
  - **Phase Modulation (PM) Noise:**  $-84.1480 \text{ dBc/Hz}$
  - **Amplitude Modulation (AM) Noise:**  $-168.8411 \text{ dBc/Hz}$
- \* The phase noise analysis indicates that **amplitude modulation (AM) noise is significantly lower compared to phase modulation (PM) noise.**

## 6 COMPARISON BETWEEN SIMULATION RESULTS OF A TYPE I CC LC VOLTAGE-CONTROLLED OSCILLATOR (VCO) WITH MOS VARACTOR AND A TYPE IV CC DIFFERENTIAL LC-VCO WITH MOS VARACTORS AND A SYMMETRIC INDUCTOR

### 6.1 Comparison

**Comparison between Type I CC LC-VCO and Type IV CC LC-VCO**

Parameter	Type I CC LC-VCO	Type IV CC LC-VCO
Center Frequency	2.996 GHz	2.9775 GHz
Tuning Range	8.077% ( $\pm 121$ MHz)	26.43% ( $\pm 394$ MHz)
$K_{VCO}$	0.7075 GHz/V	1.252 GHz/V
Output Voltage Swing	446.1 mV	3.25 V
PM Noise (at 100 kHz offset)	-81.9383 dBc/Hz	-84.1480 dBc/Hz
AM Noise (at 100 kHz offset)	-130.7708 dBc/Hz	-168.8411 dBc/Hz

### 6.2 Key points on the Tuning Range

- \* **Better Tuning Range:** Type IV achieves a much wider tuning range (26.43%) compared to Type I (8.077%), allowing it to support multiple frequency bands for modern wireless systems.
- \* **Higher Output Swing:** Type IV provides a stronger output signal (3.25V) than Type I (446.1mV), leading to better signal quality and overall system performance.

### 6.3 Enhancements and Improvements for a Wider and More Stable Tuning Range and Stability

#### 6.3.1 Hybrid Capacitor Bank with Floating Switches

- \* Uses a mix of switchable capacitors and variable capacitors (varactors) for dual tuning.
- \* Allows both large frequency jumps (via the capacitor bank) and fine adjustments (via varactors).
- \* Improves stability by using floating switches, which reduce unwanted extra capacitance and maintain circuit efficiency.
- \* Separates coarse and fine tuning to keep the tuning sensitivity ( $K_{VCO}$ ) stable.

**Equation for frequency variation:**

$$\Delta f \propto \frac{b_n C_u}{L(C_{\text{var}} + b_n C_u)}$$

Where:

- \*  $b_n$  are binary control bits
- \*  $C_u$  is unit capacitance
- \*  $C_{\text{var}}$  is the capacitance of the varactor

### 6.3.2 Optimized Symmetric Varactor Design

- \* Uses back-to-back varactors with adjustable bias for better tuning control.
- \* Expands the tuning range by adjusting bias levels to get the most capacitance variation.
- \* Enhances stability by keeping the capacitance change balanced, reducing noise and distortion.
- \* Maintains a steady  $K_{VCO}$ , minimizing phase noise fluctuations for better performance.

**Equation for symmetric capacitance modulation:**

$$C_{\text{diff}} = \frac{C_{\text{var1}}(V) \cdot C_{\text{var2}}(V)}{C_{\text{var1}}(V) + C_{\text{var2}}(V)}$$

Where:

- \*  $C_{\text{var1}}(V)$  and  $C_{\text{var2}}(V)$  are the capacitances of the two varactors, which are symmetrically tuned.

## 7 APPENDIX: NETLISTS

### 7.1 Netlist of A type I CC LC voltage-controlled oscillator (VCO) with MOS varactors

```

1 // Generated for: spectre
2 // Generated on: Mar 30 03:52:57 2025
3 // Design library name: assignment_02
4 // Design cell name: VCO_TypeI
5 // Design view name: schematic
6 simulator lang=spectre
7 global 0 vdd!
8 parameters C1=700f Ibias=800u L=3n L12=50n LV12=2u Q=10 Rp=400 vcont=500m \
9     vdd=1 W1=5u W2=5u W3=5u W4=5u F0=3G delF=10k
10 include "/home/aed/cadence/dicd_source/cadence_pdk/gpdk045_v_6_0/gpdk045/.../
    models/spectre/gpdk045.scs" section=mc
11
12 // Library name: assignment_02
13 // Cell name: VCO_TypeI
14 // View name: schematic
15 NM3 (Vcont Y Vcont 0) g45n1svt w=((W4) * (1)) l=LV12 nf=1 as=((W4) < 119.5n) ?
  (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
  50n)) + (floor(((1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W4) * 100
  n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
  n : (((60n) - 0) + 60n)) * 120n) + ((W4) * 50n)) : 0)) / 1 : (((100n > (((60n)
  ) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) + (floor((1) / 2.0) *
  ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W4))) + (((1)
  / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n)
  ) - 0) + 80n)) * (W4)) : 0)) / 1 \
  ad=((W4) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
  + ((W4) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
  (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
  50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
  60n : (((60n) - 0) + 50n)) * (W4))) + (((1) / 2) - floor((1) / 2)
  != 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
  (W4)) : 0)) / 1 \
  ps=((W4) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
  ) - 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
  + 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
  ) > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
  1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
  ) + (2 * (W4))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
  0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W4)))) + (((1) / 2)
  - floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
  (((60n) - 0) + 80n)) + (2 * (W4))) : 0)) / 1 \
  pd=((W4) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
  440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
  0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
  ((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
  + 50n)) + (2 * (W4)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
  (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 *
  (W4))) : 0)) / 1 \
  nrd=((W4) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
  + ((W4) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
  (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
  50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
  60n : (((60n) - 0) + 50n)) * (W4))) + (((1) / 2) - floor((1) / 2)
  != 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
  (W4)) : 0)) / 1 / ((W4) * (1) * (W4) * (1)) \

```

```

20      nrs=((W4) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W4) * 50n)) + (floor(((1) - 1) / 2.0) *
((((60n) - 0) + 60n) * 120n) + ((W4) * 100n)) + (((((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W4) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W4))) + (((((1) / 2) - floor((1) / 2) == 0) ? (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) : 0)) / 1 / ((W4) *
(1) * (W4) * (1)) \
21      sa=((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
22      sb=((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
23      sd=((W4) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
24      sca=(( (W4) * ( (((1u) * (1u) / (((W4) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W4) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+
60n)+(45n))) + ((1u) * (1u) / (((W4) < 119.5n) ? (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W4) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+
60n)+(45n)))) + ( (45n) * ( (((1u) * (1u) / (60n)) - ((1u) * (1u) /
(60n)+(W4)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W4)))
)))) / ((W4) * (45n)) \
25      scb=((((W4) * (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u))
) - (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+(45n))/10 + (1u)/100)*exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n)
) / (1u)) + (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n)
) / (1u)) + ((45n) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u))
) - (((60n)+(W4))/10 + (1u)/100)*exp(-10 * ((60n)+(W4)) / (1u)) +
(60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W4))/10 +
(1u)/100)*exp(-10 * ((60n)+(W4)) / (1u)))) / ((W4) * (45n)) \
26      scc=((((W4) * (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u))
) - (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W4) < 119.5n)

```

```

? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u)) + (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u)))) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u
))) - (((60n)+(W4))/20 + (1u)/400)*exp(-20 * ((60n)+(W4)) / (1u)) +
((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W4))/20 +
(1u)/400)*exp(-20 * ((60n)+(W4)) / (1u)))) / ((W4) * (45n)) \
m=(1)

27 NM2 (Vcont X Vcont 0) g45n1svt w=((W3) * (1)) l=LV12 nf=1 as=((W3) < 119.5n) ?
((((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W3) *
50n)) + (floor(((1) - 1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W3) * 100
n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
n : (((60n) - 0) + 60n)) * 120n) + ((W3) * 50n)) : 0)) / 1 : (((100n > (((60n
) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W3)) + (floor((1) - 1) / 2.0)
* ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W3))) + (((1)
/ 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) * (W3)) : 0)) / 1 \
ad=((W3) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
+ ((W3) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W3) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W3))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W3)) : 0)) / 1 \
ps=((W3) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n
) - 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
) + (2 * (W3)) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W3)))) + (((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + (2 * (W3))) : 0)) / 1 \
pd=((W3) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n)) + (2 * (W3)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
W3))) : 0)) / 1 \
nrnd=((W3) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n
) + ((W3) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W3) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W3))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W3)) : 0)) / 1 / ((W3) * (1) * (W3) * (1)) \
nrs=((W3) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W3) * 50n)) + (floor(((1) - 1) / 2.0) *
(((60n) - 0) + 60n) * 120n) + ((W3) * 100n)) + (((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) * 120n) + ((W3) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W3)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W3))) : 0)) / 1

```



```

        )) - (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
        - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
        - 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W3) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
        ) / (1u)))) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u
        )) - (((60n)+(W3))/20 + (1u)/400)*exp(-20 * ((60n)+(W3)) / (1u)) +
        ((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W3))/20 +
        (1u)/400)*exp(-20 * ((60n)+(W3)) / (1u)))) / ((W3) * (45n)) \
40      m=(1)

41 NM1 (X Y Ibias 0) g45n1svt w=((W1) * (1)) l=L12 nf=1 as=((W1) < 119.5n) ? (((50
        n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) * 50n))
        + (floor(((1) - 1) / 2.0) * (((((60n) - 0) + 60n) * 120n) + ((W1) * 100n))) +
        (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n :
        (((60n) - 0) + 60n)) * 120n) + ((W1) * 50n)) : 0)) / 1 : (((100n > (((60n) -
        0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) + (floor((1) - 1) / 2.0) *
        ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W1))) + (((1) /
        2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
        0) + 80n)) * (W1)) : 0)) / 1 \
42      ad=((W1) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n)
        + ((W1) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
        (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) *
        50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
        60n : (((60n) - 0) + 50n)) * (W1))) + (((1) / 2) - floor((1) / 2)
        != 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
        (W1)) : 0)) / 1 \
43      ps=((W1) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
        - 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
        + 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
        > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
        1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)))
        ) + (2 * (W1)) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
        0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W1)))) + (((1) / 2)
        - floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
        (((60n) - 0) + 80n)) + (2 * (W1))) : 0)) / 1 \
44      pd=((W1) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
        440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
        0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
        ((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
        + 50n)) + (2 * (W1)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
        W1))) : 0)) / 1 \
45      nrd=((W1) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n
        ) + ((W1) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
        (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) *
        50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
        60n : (((60n) - 0) + 50n)) * (W1))) + (((1) / 2) - floor((1) / 2)
        != 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
        (W1)) : 0)) / 1 / ((W1) * (1) * (W1) * (1)) \
46      nrs=((W1) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
        0) + 60n)) * 120n) + ((W1) * 50n)) + (floor(((1) - 1) / 2.0) *
        (((((60n) - 0) + 60n) * 120n) + ((W1) * 100n))) + (((1) / 2) -
        floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
        0) + 60n)) * 120n) + ((W1) * 50n)) : 0)) / 1 : (((100n > (((60n) -
        0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) + (floor(((1) - 1)
        / 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
        (W1))) + (((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
        + 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) : 0)) / 1 / ((W1) * (1)
        * (W1) * (1)) \
47      sa=((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
        60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
        80n)) \

```

```

48      sb=((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
        60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
        80n)) \
49      sd=((W1) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
        0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
50      sca=(( (W1) * ( (((1u) * (1u) / (((W1) < 119.5n) ? (50n > (((60n) - 0)
        + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
        80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W1) <
        119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
        5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n))) + ((1u) * (1u) / (((W1) < 119.5n) ? (50n > (((60n) -
        0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
        80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W1) <
        119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
        5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n)))) + ((45n) * ( (((1u) * (1u) / (60n)) - ((1u) * (1u) /
        ((60n)+(W1)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W1)))))) / ((W1) * (45n)) \
51      scb=(((W1) * (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
        (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
        (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u))
        ) - (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
        0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
        0) + 80n))+60n)+45n)/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n) /
        (1u)) + (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
        (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
        (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n) /
        (1u)) + ((45n) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)))
        - (((60n)+(W1))/10 + (1u)/100)*exp(-10 * ((60n)+(W1)) / (1u)) +
        ((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W1))/10 +
        (1u)/100)*exp(-10 * ((60n)+(W1)) / (1u)))))) / ((W1) * (45n)) \
52      scc=(((W1) * (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
        (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
        (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u))
        ) - (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
        0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
        0) + 80n))+60n)+45n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n) /
        (1u)) + (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
        (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
        (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
        ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
        (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n) /
        (1u)) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)))
        - (((60n)+(W1))/20 + (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)) +
        ((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W1))/20 +
        (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)))))) + ((45n) * (((60n)/20 +
        (1u)/400)*exp(-20 * (60n) / (1u)))

```

```

    )) - (((60n)+(W1))/20 + (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)) +
    ((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W1))/20 +
    (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)))) / ((W1) * (45n)) \
53   m=(1)
54 NMO (Y X Ibias 0) g45n1svt w=((W2) * (1)) l=L12 nf=1 as=((W2) < 119.5n) ? (((50
n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) * 50n)) +
(floor(((1) - 1) / 2.0) * (((((60n) - 0) + 60n) * 120n) + ((W2) * 100n))) +
(((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) * 120n) + ((W2) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) + (floor(((1) - 1) / 2.0) *
((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W2))) + (((1) /
2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n)) * (W2)) : 0)) / 1 \
55   ad=((W2) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n)
+ ((W2) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
(((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W2))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W2)) : 0)) / 1 \
56   ps=((W2) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
) + (2 * (W2))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W2)))) + (((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + (2 * (W2))) : 0)) / 1 \
57   pd=((W2) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n)) + (2 * (W2)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
W2))) : 0)) / 1 \
58   nrd=((W2) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n)
+ ((W2) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
(((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W2))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W2)) : 0)) / 1 / ((W2) * (1) * (W2) * (1)) \
59   nrs=((W2) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W2) * 50n)) + (floor(((1) - 1) / 2.0) *
((((60n) - 0) + 60n) * 120n) + ((W2) * 100n)) + (((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W2) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W2))) + (((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) : 0)) / 1 / ((W2) * (1)
* (W2) * (1)) \
60   sa=((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
61   sb=((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
62   sd=((W2) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
63   sca=(( (W2) * ( ((1u) * (1u) / (((W2) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n)) \

```

```

80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W2) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) +
+60n)+(45n)))) + ((1u) * (1u) / (((W2) < 119.5n) ? (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u)/ (((W2)
) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)
) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)
)+60n)+(45n)))) + ( (45n) * ( (((1u) * (1u) / (60n)) - ((1u) * (1u)
/ ((60n)+(W2)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u)/ ((60n)+(W2)
)))) ) / ((W2) * (45n)) \
64 scb=(((W2) * (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) + (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u)) + ((45n) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u
)) - (((60n)+(W2))/10 + (1u)/100)*exp(-10 * ((60n)+(W2)) / (1u)) +
((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W2))/10 +
(1u)/100)*exp(-10 * ((60n)+(W2)) / (1u)))) ) / ((W2) * (45n)) \
65 scc=(((W2) * (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u)) + (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u))) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u
)) - (((60n)+(W2))/20 + (1u)/400)*exp(-20 * ((60n)+(W2)) / (1u)) +
((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W2))/20 +
(1u)/400)*exp(-20 * ((60n)+(W2)) / (1u)))) ) / ((W2) * (45n)) \
66 m=(1)
67 C1 (vdd! Y) capacitor c=C1
68 C0 (vdd! X) capacitor c=C1
69 R1 (vdd! X) resistor r=Rp

```

```

70 R0 (vdd! Y) resistor r=Rp
71 V2 (Vcont 0) vsource dc=vcont type=dc
72 V0 (vdd! 0) vsource dc=vdd type=dc
73 I17 (Ibias 0) isource dc=Ibias type=dc
74 I19 (X Y) isource type=pulse val0=0 val1=1m rise=1p fall=1p width=3p
75 L2 (vdd! Y) inductor l=L q=Q fq=100M mode=1
76 L0 (vdd! X) inductor l=L q=Q fq=100M mode=1
77 simulatorOptions options reltol=1e-3 vabstol=1e-6 iabstol=1e-12 temp=27 \
    tnom=27 scalem=1.0 scale=1.0 gmin=1e-12 rforce=1 maxnotes=5 maxwarns=5 \
    digits=5 cols=80 pivrel=1e-3 sensfile="..../psf/sens.output" \
    checklimitdest=psf
78 tran tran stop=100n errpreset=conservative write="spectre.ic" \
    writefinal="spectre.fc" annotate=status maxiters=5
79 finalTimeOP info what=oppoint where=rawfile
80 pss ( X Y ) pss fund=F0 harms=20 errpreset=conservative
81 + autosteady=yes oscic=lin annotate=status
82 pnoise ( X Y ) pnoise sweeptype=relative relharmnum=1
83 + start=10k stop=1M noisetype=timeaverage noiseout=[am pm usb
84 + lsb] annotate=status
85 modelParameter info what=models where=rawfile
86 element info what=inst where=rawfile
87 outputParameter info what=output where=rawfile
88 designParamVals info what=parameters where=rawfile
89 primitives info what=primitives where=rawfile
90 subckts info what=subckts where=rawfile
91 save NM1:d NM0:d
92 saveOptions options save=allpub

```

Listing 7.1 — Example Circuit Netlist

## 7.2 Netlist of a type IV CC Differential LC-VCO with MOS varactors and a symmetric inductor

```

1 // Generated for: spectre
2 // Generated on: Mar 30 18:07:33 2025
3 // Design library name: assignment_02
4 // Design cell name: VCO_TypeIV
5 // Design view name: schematic
6 simulator lang=spectre
7 global 0 vdd!
8 parameters Ibias=100u L=5n L12=1u L34=1u LV12=1u vcont=0.5 vdd=1 W1=5u \
    W2=5u W3=5u W4=5u W5=10u W6=10u F0=10k delF=10k
9 include "/home/aed/cadence/dicd_source/cadence_pdk/gpdk045_v_6_0/gpdk045/../
10 models/spectre/gpdk045.scs" section=mc
11
12 // Library name: assignment_02
13 // Cell name: VCO_TypeIV
14 // View name: schematic
15 NM3 (Vcont Y Vcont 0) g45n1svt w=((W4) * (1)) l=LV12 nf=1 as=((W4) < 119.5n) ?
    (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
    50n)) + (floor(((1) - 1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W4) * 100
    n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
    n : (((60n) - 0) + 60n)) * 120n) + ((W4) * 50n)) : 0)) / 1 : (((100n > (((60n
    ) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) + (floor(((1) - 1) / 2.0)
    * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W4))) + (((1)
    / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n
    ) - 0) + 80n)) * (W4)) : 0)) / 1 \
    ad=((W4) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n) +
    ((W4) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
    (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
    50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
    60n : (((60n) - 0) + 50n)) * (W4))) + (((1) / 2) - floor((1) / 2)
    * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W4))) :
    0)) / 1
16

```

```

17 ! = 0) ? (((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W4)) : 0)) / 1 \
ps=((W4) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n))) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n))) + 340n) : 0)) / 1 :
(((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
) + (2 * (W4))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)))) + (2 * (W4)))) + (((((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))) + (2 * (W4))) : 0)) / 1 \
pd=((W4) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n))) + 340n) : 0)) / 1 : ((floor
((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n)))) + (2 * (W4)))) + (((((1) / 2) - floor((1) / 2) != 0) ? ((2 *
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))) + (2 * (W4)))
: 0)) / 1 \
nrld=((W4) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n
) + ((W4) * 100n))) + (((((1) / 2) - floor((1) / 2) != 0) ? ((50n >
(((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W4) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W4))) + (((((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W4)) : 0)) / 1 / ((W4) * (1) * (W4) * (1)) \
nrs=((W4) < 119.5n) ? (((((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W4) * 50n)) + (floor(((1) - 1) / 2.0) *
((((60n) - 0) + 60n) * 120n) + ((W4) * 100n))) + (((((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W4) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W4))) + (((((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W4)) : 0)) / 1 / ((W4) * (1)
* (W4) * (1)) \
sa=((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
sb=((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
sd=((W4) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
sca=(( (W4) * ( (((1u) * (1u) / (((W4) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W4) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) +
60n)+LV12))) + ((1u) * (1u) / (((W4) < 119.5n) ? (50n > (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) /
(((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) +
60n)+LV12))) + ( LV12 * ( (((1u) * (1u) / (60n)) - ((1u) * (1u) /
((60n)+(W4)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W4)))
))) / ((W4) * LV12) \
scb=(( (W4) * (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
) - (((((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) +
80n))+60n)) / (1u)) )
```

26

```

- 0) + 80n)) + 60n) + LV12) / 10 + (1u) / 100) * exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) + LV12)
/ (1u) + (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + 60n) / 10 + (1u) / 100) * exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) / (1u))
- (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) + 60n) / 10 + (1u) / 100) * exp(-10 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) / (1u)))
+ (LV12 * (((60n) / 10 + (1u) / 100) * exp(-10 * (60n) / (1u)))
- (((60n) + (W4)) / 10 + (1u) / 100) * exp(-10 * ((60n) + (W4)) / (1u)) +
((60n) / 10 + (1u) / 100) * exp(-10 * (60n) / (1u)) - (((60n) + (W4)) / 10 +
(1u) / 100) * exp(-10 * ((60n) + (W4)) / (1u)))) / ((W4) * LV12) \
scc=(((W4) * (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + 60n) / 20 + (1u) / 400) * exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) / (1u))
- (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) + 60n) / 20 + (1u) / 400) * exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) / (1u)))
+ (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + 60n) / 20 + (1u) / 400) * exp(-20 * (((W4) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + 60n) / (1u))
- (((W4) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) + 60n) / 20 + (1u) / 400) * exp(-20 * ((60n) + (W4)) / (1u)) +
((60n) / 20 + (1u) / 400) * exp(-20 * (60n) / (1u)) - (((60n) + (W4)) / 20 +
(1u) / 400) * exp(-20 * ((60n) + (W4)) / (1u)))) / ((W4) * LV12) \
m=(1)

```

27

```

28 NM2 (Vcont X Vcont 0) g45n1svt w=((W3) * (1)) l=LV12 nf=1 as=((W3) < 119.5n) ?
((((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W3) *
50n)) + (floor(((1) - 1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W3) * 100
n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
n : (((60n) - 0) + 60n)) * 120n) + ((W3) * 50n)) : 0)) / 1 : (((100n > (((60n)
- 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W3)) + (floor(((1) - 1) / 2.0)
* ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W3))) + (((1)
/ 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) * (W3)) : 0)) / 1 \
ad=((W3) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
+ ((W3) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W3) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W3))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W3)) : 0)) / 1 \
ps=((W3) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n))) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))) +

```

30



```

(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+LV12)/10 + (1u)/100)*exp(-10 * (((W3) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+LV12)
/ (1u)))) + (LV12 * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u))
- (((60n)+(W3))/10 + (1u)/100)*exp(-10 * ((60n)+(W3)) / (1u)) + ((60
n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W3))/10 + (1u)
/100)*exp(-10 * ((60n)+(W3)) / (1u)))) / ((W3) * LV12) \
39 scc=(((W3) * (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W3) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
))) - (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+LV12)/20 + (1u)/400)*exp(-20 * (((W3) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+LV12)
/ (1u)) + (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W3) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
))) - (((((W3) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+LV12)/20 + (1u)/400)*exp(-20 * (((W3) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
))) + (LV12 * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u))
- (((60n)+(W3))/20 + (1u)/400)*exp(-20 * ((60n)+(W3)) / (1u)) + ((60
n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W3))/20 + (1u)
/400)*exp(-20 * ((60n)+(W3)) / (1u)))) / ((W3) * LV12) \
40 m=(1)
41 NM1 (X Y Ibias 0) g45n1svt w=((W1) * (1)) l=L12 nf=1 as=((W1) < 119.5n) ? (((50
n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) * 50n))
+ (floor(((1) - 1) / 2.0) * (((((60n) - 0) + 60n) * 120n) + ((W1) * 100n))) +
(((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) * 120n) + ((W1) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) + (floor(((1) - 1) / 2.0) *
((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W1))) + (((1) /
2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n)) * (W1)) : 0)) / 1 \
42 ad=((W1) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n)
+ ((W1) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
(((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W1))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W1)) : 0)) / 1 \
43 ps=((W1) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)))
+ (2 * (W1))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W1)))) + (((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + (2 * (W1))) : 0)) / 1 \
44 pd=((W1) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor

```

```

((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n))) + (2 * (W1)))) + (((((1) / 2) - floor((1) / 2) != 0) ? ((2 *
100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))) + (2 * (W1))) : 0)) / 1 \
45 nrd=((W1) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n
) + ((W1) * 100n))) + (((((1) / 2) - floor((1) / 2) != 0) ? (((50n >
(((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W1) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W1))) + (((((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W1)) : 0)) / 1 / ((W1) * (1) * (W1) * (1)) \
46 nrs=((W1) < 119.5n) ? (((((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W1) * 50n)) + (floor(((1) - 1) / 2.0) *
((((((60n) - 0) + 60n) * 120n) + ((W1) * 100n))) + (((((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W1) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W1))) + (((((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W1)) : 0)) / 1 / ((W1) * (1)
* (W1) * (1)) \
47 sa=((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
48 sb=((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
49 sd=((W1) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
50 sca=(( (W1) * ( (((1u) * (1u) / (((W1) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n) ? 100n : (((60n) - 0) + 80n))+60n) - ((1u) * (1u) / (((W1) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) +
60n)+(45n)))) + ((1u) * (1u) / (((W1) < 119.5n) ? (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) - ((1u) * (1u) / (((W1) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) +
60n)+(45n)))) + ( (45n) * ( (((1u) * (1u) / (60n)) - ((1u) * (1u) /
(60n)+(W1)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W1)))
)) / ((W1) * (45n)) \
51 scb=(( (W1) * (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
) - (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+(45n))/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n)
) / (1u)) + (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n) / (1u) ) - (((((W1) < 119.5n) ? (50n > (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+(45n))/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
) - (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+(45n))/10 + (1u)/100)*exp(-10 * (((W1) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n)
) / (1u)))) + ((45n) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)
) + ((1u) / (60n)+(W1)))) + ((1u) / (60n)+(W1)) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)
) + ((1u) / (60n)+(W1))) \

```

```

    )) - (((60n)+(W1))/10 + (1u)/100)*exp(-10 * ((60n)+(W1)) / (1u)) +
    ((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W1))/10 +
    (1u)/100)*exp(-10 * ((60n)+(W1)) / (1u)))) / ((W1) * (45n)) \
52 scc=(((W1) * (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
    (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
    (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
    ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
    (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
    )) - (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
    - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
    - 0) + 80n))+60n)+(45n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
    ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
    (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
    )) / (1u)) + (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
    (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
    (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
    ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
    (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
    )) / (1u)) + (((((W1) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
    (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
    (((60n) - 0) + 80n))+60n)+(45n)/20 + (1u)/400)*exp(-20 * (((W1) < 119.5n)
    ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
    (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
    )) / (1u))) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u))
    )) - (((60n)+(W1))/20 + (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)) +
    ((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W1))/20 +
    (1u)/400)*exp(-20 * ((60n)+(W1)) / (1u)))) / ((W1) * (45n)) \
53 m=(1)

54 NMO (Y X Ibias 0) g45n1svt w=((W2) * (1)) l=L12 nf=1 as=((W2) < 119.5n) ? (((50
    n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) * 50n))
    + (floor(((1) - 1) / 2.0) * (((((60n) - 0) + 60n) * 120n) + ((W2) * 100n))) +
    (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n :
    (((60n) - 0) + 60n)) * 120n) + ((W2) * 50n)) : 0)) / 1 : (((100n > (((60n) -
    0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) + (floor(((1) - 1) / 2.0) *
    ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W2))) + (((1) /
    2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
    0) + 80n)) * (W2)) : 0)) / 1 \
55 ad=((W2) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n)
    + ((W2) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
    (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) *
    50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
    60n : (((60n) - 0) + 50n)) * (W2))) + (((1) / 2) - floor((1) / 2)
    != 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
    (W2)) : 0)) / 1 \
56 ps=((W2) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
    - 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
    + 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
    > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
    1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)))
    + (2 * (W2))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
    0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W2)))) + (((1) / 2)
    - floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
    (((60n) - 0) + 80n)) + (2 * (W2))) : 0)) / 1 \
57 pd=((W2) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
    440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
    0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
    ((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
    + 50n)) + (2 * (W2)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
    (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
    W2))) : 0)) / 1 \
58 nrd=((W2) < 119.5n) ? ((floor((1) / 2.0) * (((((60n) - 0) + 60n) * 120n
    ) + ((W2) * 100n))) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
    (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W2) *
    50n)) : 0)) / 1

```

```

50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W2))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W2)) : 0)) / 1 / ((W2) * (1) * (W2) * (1)) \
59 nrs=((W2) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W2) * 50n)) + (floor(((1) - 1) / 2.0) *
((((60n) - 0) + 60n) * 120n) + ((W2) * 100n))) + (((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W2) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W2))) + (((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W2)) : 0)) / 1 / ((W2) * (1)
* (W2) * (1)) \
60 sa=((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
61 sb=((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
62 sd=((W2) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
63 sca=(( (W2) * ( (((1u) * (1u) / (((W2) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W2) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n))) + ((1u) * (1u) / (((W2) < 119.5n) ? (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W2) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n))) + ((45n) * ( (((1u) * (1u) / (60n)) - ((1u) * (1u)
/ ((60n)+(W2)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W2)))))) / (((W2) * (45n)) \
64 scb=(((W2) * (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u))
- (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) -
0) + 80n))+60n)+45n)/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n)) /
(1u)) + (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+45n)) /
(1u)) + ((45n) * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)))
- (((60n)+(W2))/10 + (1u)/100)*exp(-10 * ((60n)+(W2)) / (1u)) +
(60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W2))/10 +
(1u)/100)*exp(-10 * ((60n)+(W2)) / (1u)))))) / (((W2) * (45n)) \
65 scc=(((W2) * (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)) / (((W2) * (45n)) \

```

```

(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+(45n
)) / (1u)) + (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
)) - (((((W2) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+(45n))/20 + (1u)/400)*exp(-20 * (((W2) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u
))) + ((45n) * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u
)) - (((60n)+(W2))/20 + (1u)/400)*exp(-20 * ((60n)+(W2)) / (1u)) +
(60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W2))/20 +
(1u)/400)*exp(-20 * ((60n)+(W2)) / (1u)))) / ((W2) * (45n)) \
m=(1)

66 PM1 (X Y vdd! vdd!) g45p1svt w=((W6) * (1)) l=L34 nf=1 as=((W6) < 119.5n) ?
67 (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W6) *
50n)) + (floor(((1) - 1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W6) * 100
n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
n : (((60n) - 0) + 60n)) * 120n) + ((W6) * 50n)) : 0)) / 1 : (((100n > (((60n
) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W6)) + (floor(((1) - 1) / 2.0)
* ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W6))) + (((1)
/ 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n
) - 0) + 80n)) * (W6)) : 0)) / 1 \
68 ad=((W6) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
+ ((W6) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W6) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W6))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W6)) : 0)) / 1 \
69 ps=((W6) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n
) - 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
) + (2 * (W6))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W6)))) + (((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + (2 * (W6))) : 0)) / 1 \
70 pd=((W6) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n)) + (2 * (W6)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
W6))) : 0)) / 1 \
71 nrd=((W6) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n
) + ((W6) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W6) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W6))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W6)) : 0)) / 1 / ((W6) * (1) * (W6) * (1)) \
72 nrs=((W6) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W6) * 50n)) + (floor(((1) - 1) / 2.0) *
(((60n) - 0) + 60n) * 120n) + ((W6) * 100n)) + (((1) / 2) -

```

```

    floor((1) / 2) == 0 ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) * 120n) + ((W6) * 50n) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W6)) + (floor(((1) / 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W6))) + (((((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W6)) : 0)) / 1 / ((W6) * (1)
* (W6) * (1)) \
73   sa=((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
74   sb=((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
80n)) \
75   sd=((W6) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
76   sca=(( (W6) * ( (((1u) * (1u) / (((W6) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W6) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n+
L34))) + ((1u) * (1u) / (((W6) < 119.5n) ? (50n > (((60n) - 0)
+ 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W6) <
119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n+
L34))) + ( L34 * ( (((1u) * (1u) / (60n)) - ((1u) * (1u) /
(60n)+(W6)))) + ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W6)))
))) / ((W6) * L34) \
77   scb=(((W6) * (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) - (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+L34)/10 + (1u)/100)*exp(-10 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) + (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) - (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 80n))+60n)+L34)/10 + (1u)/100)*exp(-10 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) + (L34 * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) -
((60n)+(W6))/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W6))/10 +
(1u)/100)*exp(-10 * ((60n)+(W6)) / (1u)))) / ((W6) * L34) \
78   scc=(((W6) * (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) - (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+L34)/20 + (1u)/400)*exp(-20 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) + (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)+L34)) / ((W6) * L34) \

```

```

(((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W6) < 119.5n)
? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) / (1u)
)) - (((((W6) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n))+60n)+L34)/20 + (1u)/400)*exp(-20 * (((W6) < 119.5n) ?
(50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+L34)
/ (1u)))) + (L34 * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) -
(((60n)+(W6))/20 + (1u)/400)*exp(-20 * ((60n)+(W6)) / (1u)) + ((60n)
/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W6))/20 + (1u)
/400)*exp(-20 * ((60n)+(W6)) / (1u)))) / ((W6) * L34) \
m=(1)

79 PMO (Y X vdd! vdd!) g45p1svt w=((W5) * (1)) l=L34 nf=1 as=((W5) < 119.5n) ?
(((50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W5) *
50n)) + (floor(((1) - 1) / 2.0) * (((60n) - 0) + 60n) * 120n) + ((W5) * 100
n)) + (((1) / 2) - floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50
n : (((60n) - 0) + 60n)) * 120n) + ((W5) * 50n)) : 0)) / 1 : (((100n > (((60n)
- 0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W5)) + (floor(((1) - 1) / 2.0)
* ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) * (W5))) + (((1)
/ 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n)
- 0) + 80n)) * (W5)) : 0)) / 1 \
80 ad=((W5) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n)
+ ((W5) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W5) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W5))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W5)) : 0)) / 1 \
81 ps=((W5) < 119.5n) ? (((2 * (50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) + 340n) + (floor(((1) - 1) / 2.0) * ((2 * (((60n) - 0)
+ 60n)) + 440n)) + (((1) / 2) - floor((1) / 2) == 0) ? ((2 * (50n
> (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) /
1 : (((2 * (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))
) + (2 * (W5))) + (floor(((1) - 1) / 2.0) * ((2 * (60n > (((60n) -
0) + 50n) ? 60n : (((60n) - 0) + 50n)) + (2 * (W5)))) + (((1) / 2)
- floor((1) / 2) == 0) ? ((2 * (100n > (((60n) - 0) + 80n) ? 100n :
(((60n) - 0) + 80n)) + (2 * (W5))) : 0)) / 1 \
82 pd=((W5) < 119.5n) ? ((floor((1) / 2.0) * ((2 * (((60n) - 0) + 60n)) +
440n)) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 * (50n > (((60n) -
0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 340n) : 0)) / 1 : ((floor
((1) / 2.0) * ((2 * (60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0)
+ 50n)) + (2 * (W5)))) + (((1) / 2) - floor((1) / 2) != 0) ? ((2 *
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) + (2 * (
W5))) : 0)) / 1 \
83 nrd=((W5) < 119.5n) ? ((floor((1) / 2.0) * (((60n) - 0) + 60n) * 120n
) + ((W5) * 100n)) + (((1) / 2) - floor((1) / 2) != 0) ? (((50n >
((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) * 120n) + ((W5) *
50n)) : 0)) / 1 : ((floor((1) / 2.0) * ((60n > (((60n) - 0) + 50n) ?
60n : (((60n) - 0) + 50n)) * (W5))) + (((1) / 2) - floor((1) / 2)
!= 0) ? ((100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n)) *
(W5)) : 0)) / 1 / ((W5) * (1) * (W5) * (1)) \
84 nrs=((W5) < 119.5n) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n) -
0) + 60n)) * 120n) + ((W5) * 50n)) + (floor(((1) - 1) / 2.0) *
(((60n) - 0) + 60n) * 120n) + ((W5) * 100n)) + (((1) / 2) -
floor((1) / 2) == 0) ? (((50n > (((60n) - 0) + 60n) ? 50n : (((60n)
- 0) + 60n)) * 120n) + ((W5) * 50n)) : 0)) / 1 : (((100n > (((60n) -
0) + 80n) ? 100n : (((60n) - 0) + 80n)) * (W5)) + (floor(((1) - 1)
/ 2.0) * ((60n > (((60n) - 0) + 50n) ? 60n : (((60n) - 0) + 50n)) *
(W5))) + (((1) / 2) - floor((1) / 2) == 0) ? ((100n > (((60n) - 0)
+ 80n) ? 100n : (((60n) - 0) + 80n)) * (W5)) : 0)) / 1 / ((W5) * (1)
* (W5) * (1)) \
85

```

```

86      sa=((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
87          60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
88          80n)) \
89      sb=((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) +
90          60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) +
91          80n)) \
92      sd=((W5) < 119.5n) ? (((60n) - 0) + 60n) + (2*5e-08) : (60n > (((60n) -
93          0) + 50n) ? 60n : (((60n) - 0) + 50n)) \
94      sca=(( (W5) * ( ((1u) * (1u) / (((W5) < 119.5n) ? (50n > (((60n) - 0)
95          + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) +
96          80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W5) <
97          119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
98          5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n+
99          L34))) + ((1u) * (1u) / (((W5) < 119.5n) ? (50n > (((60n) - 0)
100         + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0)
101         + 80n) ? 100n : (((60n) - 0) + 80n))+60n)) - ((1u) * (1u) / (((W5) <
102         119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) +
103         5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n+
104         L34))) + ( L34 * ( ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W5)))) +
105         ((1u) * (1u) / (60n)) - ((1u) * (1u) / ((60n)+(W5)))) ) / ((W5) * L34) \
106         ) / ((W5) * L34) \
107         scb=(((W5) * (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
108             (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
109                 (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W5) < 119.5n)
110                 ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
111                     (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
112                     (1u)) - (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
113                         (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
114                             (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W5) < 119.5n)
115                             ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
116                               (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
117                               (1u)) - (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
118                                   (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
119                                       (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W5) < 119.5n)
120                                       ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
121                                         (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
122                                         (1u)) - (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
123                                             (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
124                                                 (((60n) - 0) + 80n))+60n)/10 + (1u)/100)*exp(-10 * (((W5) < 119.5n)
125                                                 ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
126                                                   (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
127                                                   (1u)) + (L34 * (((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) -
128                                                       (((60n)+(W5))/10 + (1u)/100)*exp(-10 * ((60n)+(W5)) / (1u)) +
129                                                       ((60n)/10 + (1u)/100)*exp(-10 * (60n) / (1u)) - (((60n)+(W5))/10 + (1u) /
130                                                       100)*exp(-10 * ((60n)+(W5)) / (1u)))) ) / ((W5) * L34) \
131         scc=(((W5) * (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
132             (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
133                 (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W5) < 119.5n)
134                 ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
135                     (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
136                     (1u)) - (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
137                         (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
138                             (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W5) < 119.5n)
139                             ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
140                               (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
141                               (1u)) + (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
142                                   (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
143                                       (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W5) < 119.5n)
144                                       ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
145                                         (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
146                                         (1u)) - (((((W5) < 119.5n) ? (50n > (((60n) - 0) + 60n) ? 50n :
147                                             (((60n) - 0) + 60n)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n :
148                                                 (((60n) - 0) + 80n))+60n)/20 + (1u)/400)*exp(-20 * (((W5) < 119.5n)
149                                                 ? (50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
150                                                   (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
151                                                   (1u)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
152                                                   (1u)) + 5e-08 : (100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n) /
153                                                   (1u)) ) / ((W5) * L34) \

```

```

(50n > (((60n) - 0) + 60n) ? 50n : (((60n) - 0) + 60n)) + 5e-08 :
(100n > (((60n) - 0) + 80n) ? 100n : (((60n) - 0) + 80n))+60n)+L34)
/ (1u)))) + (L34 * (((60n)/20 + (1u)/400)*exp(-20 * (60n) / (1u)) -
(((60n)+(W5))/20 + (1u)/400)*exp(-20 * ((60n)+(W5)) / (1u)) + ((60n)
/20 + (1u)/400)*exp(-20 * (60n) / (1u)) - (((60n)+(W5))/20 + (1u)
/400)*exp(-20 * ((60n)+(W5)) / (1u)))))) / ((W5) * L34) \
m=(1)
92 L1 (net20 Y) inductor l=L q=10 fq=100M mode=1
93 L0 (X net20) inductor l=L q=10 fq=100M mode=1
94 V2 (Vcont 0) vsource dc=vcont type=dc
95 V0 (vdd! 0) vsource dc=vdd type=dc
96 I17 (Ibias 0) isource dc=Ibias type=dc
97 I19 (X Y) isource type=pulse val0=0 val1=1n rise=1p fall=1p width=3p
98 simulatorOptions options reltol=1e-3 vabstol=1e-6 iabstol=1e-12 temp=27 \
100 tnom=27 scalem=1.0 scale=1.0 gmin=1e-12 rforce=1 maxnotes=5 maxwarns=5 \
101 digits=5 cols=80 pivrel=1e-3 sensfile="..../psf/sens.output" \
102 checklimitdest=psf
103 tran tran stop=100m errpreset=conservative write="spectre.ic" \
104 writefinal="spectre.fc" annotate=status maxiters=5
105 finalTimeOP info what=oppont where=rawfile
106 hb ( X Y ) hb autotstab=yes oversample=[1] fundfreqs=[(F0)]
107 + maxharms=[20] errpreset=conservative oscic=lin oscmethod=onetier
108 + annotate=status
109 pss ( X Y ) pss fund=F0 harms=20 autosteady=yes oscic=lin
110 + annotate=status
111 pnoise ( X Y ) pnoise sweeptype=relative relharmnum=1
112 + start=100k stop=1M noisetype=timeaverage noiseout=[am pm usb
113 + lsb] annotate=status
114 modelParameter info what=models where=rawfile
115 element info what=inst where=rawfile
116 outputParameter info what=output where=rawfile
117 designParamVals info what=parameters where=rawfile
118 primitives info what=primitives where=rawfile
119 subckts info what=subckts where=rawfile
120 saveOptions options save=allpub

```

Listing 7.2 — Example Circuit Netlist