

High-Speed Serial Interface Circuits and Systems

Design Exercise3 – LC VCO

LC VCO Structure

✓LC Tank

- Spiral inductor (symmetric type)
- Ideal capacitor

✓Varactor

- Accumulation varactor


✓Cross coupled circuit

- Negative resistance
- To compensate for the loss of the tank

✓Source MOSFET

✓OSC frequency

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$


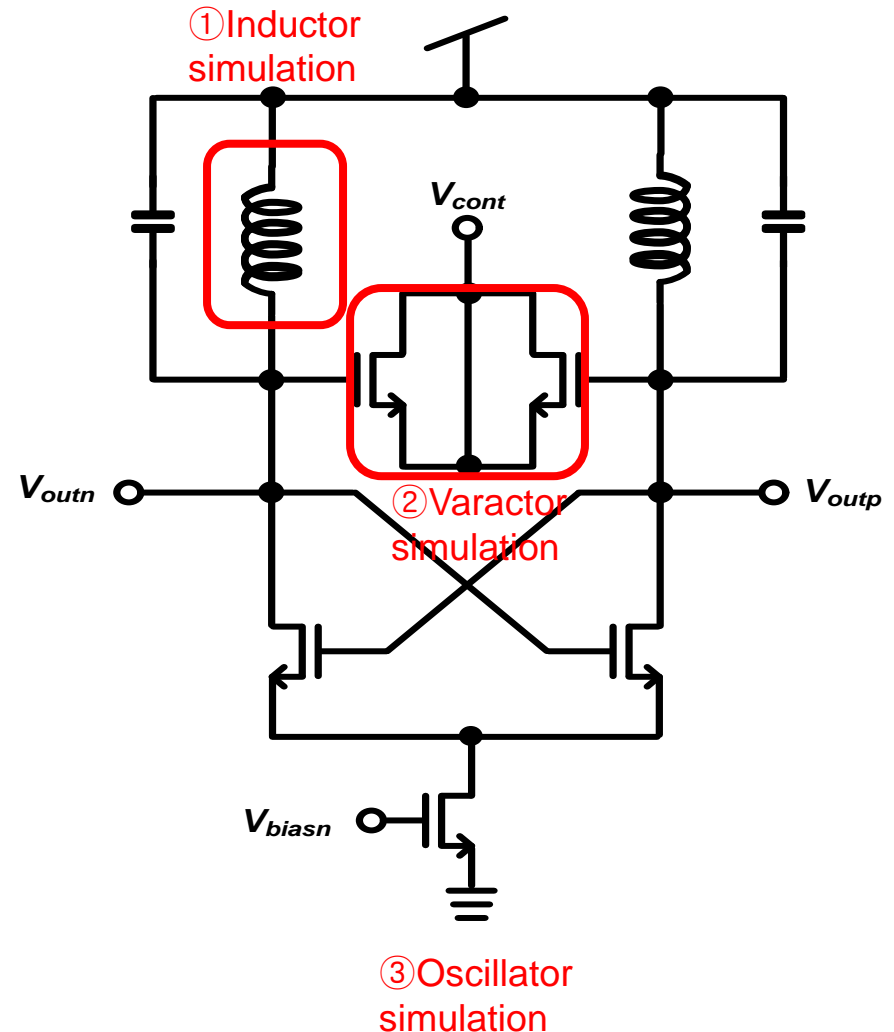


Design Example

- ✓ LC voltage controlled oscillator (VCO)
 - Supply voltage: 1.8V
 - Frequency tuning range: > 30-MHz
 - Oscillation frequency : 1.5-GHz
 - Phase noise @ 1-MHz offset with 1.5-GHz: < -125dBc

Inductor Model

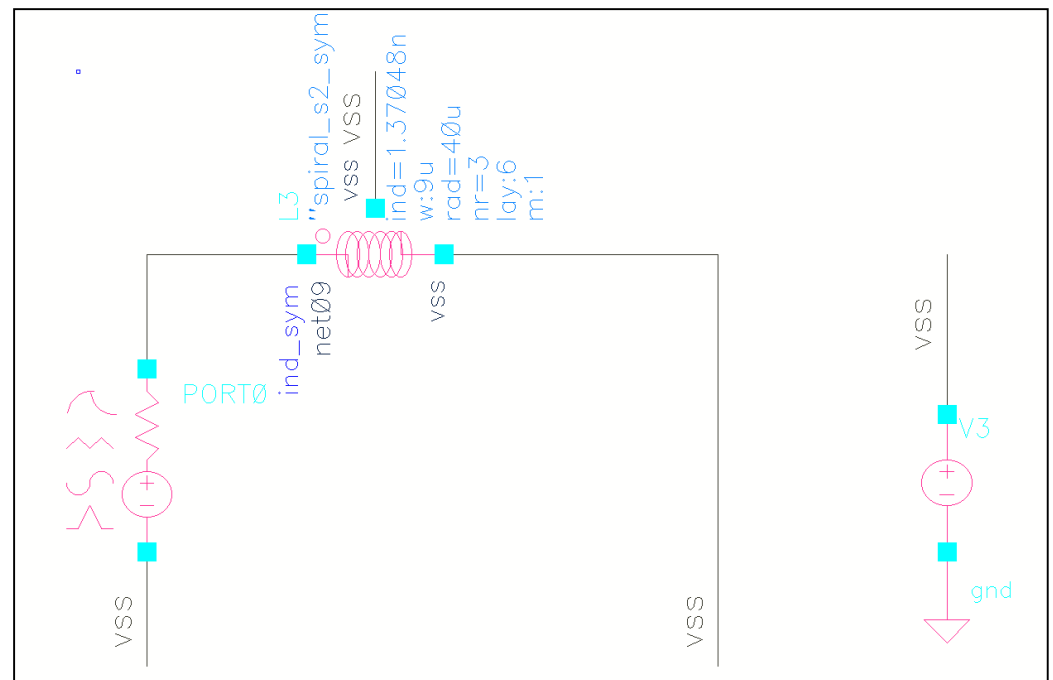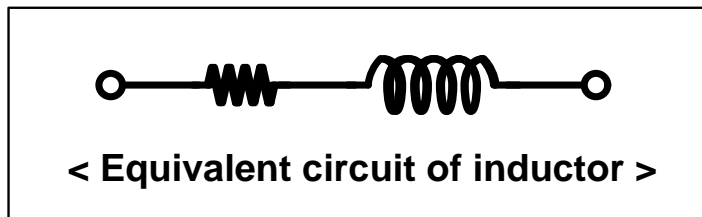
- An equivalent circuit model of inductor
 - Series connection of resistance and inductance
 - Analyze inductance into using Z-parameter



< Simulation schematic >

Inductor

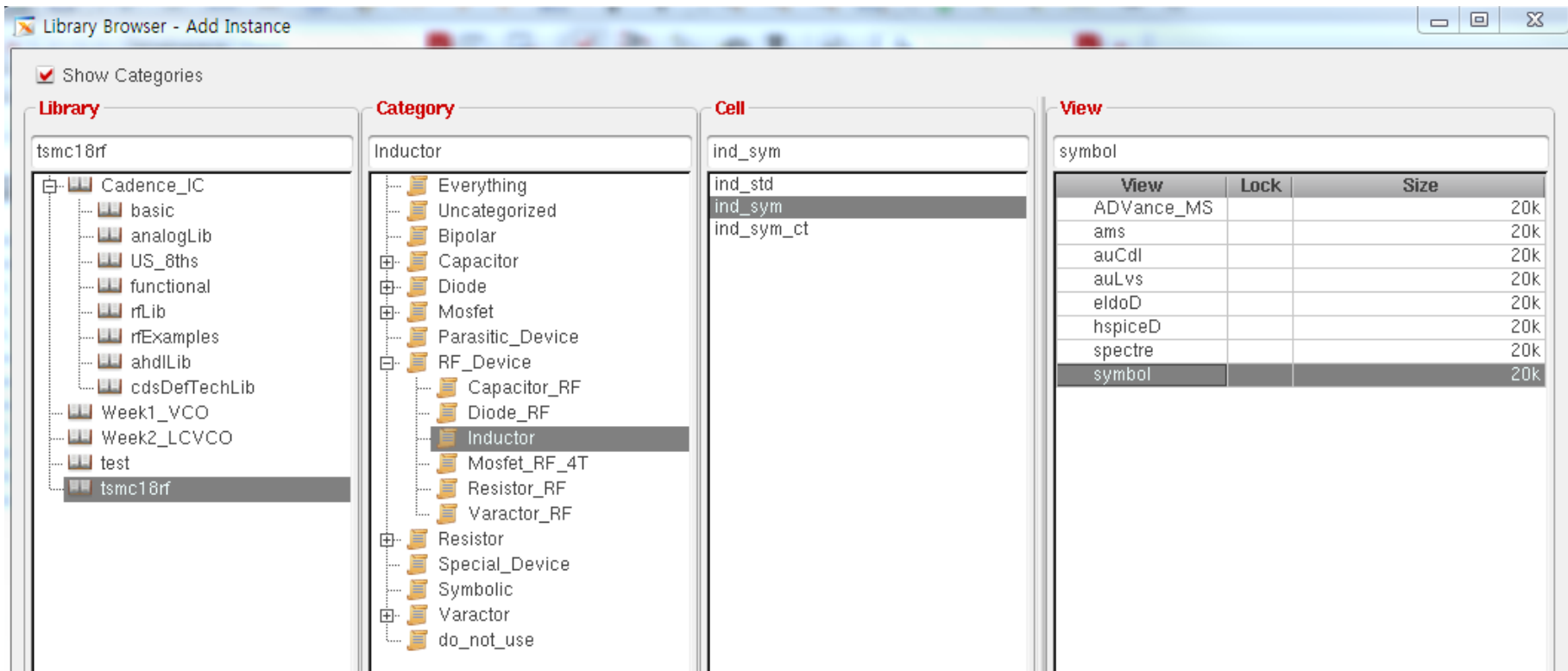- Inductor selection
 - Tsmc18rf → RF_Device → Inductor → ind_sym → symbol
 - Symmetric inductor selection



Inductor Parameters

- Setting of frequency, inductor width, inner radius and number of turns.

Property	Value	Display
Library Name	tsmc18rf	off
Cell Name	ind_sym	value
View Name	symbol	off
Instance Name	L2	off


CDF Parameter	Value	Display
Model name	spiral_s3_sym	off
L_value_single_ended(H)	5.54128n H	off
Q_factor_single_ended	8.88728	off
L_value_differential(H)	5.31668n H	off
Q_factor_differential	10.0172	off
temp(C)	27 c	off
freq(Hz)	1.56 Hz	off
Inductor_Width_(M)	30u	off
Inductor_Space_(M)	3u M	off
Inner_Radius(M)	90u M	off
Number_Of_Turns	4	off
multiplier	1	off
Hard_constrain	<input checked="" type="checkbox"/>	off

- Freq(Hz) : 1.5G
- Inductor_Width (M) : 30u
- Inner_Radius (M) : 90u
- Number_Of_Turns : 4

→ Inductance : 5.54nH
→ Q_factor : 8.88



Port for S-parameter Simulation

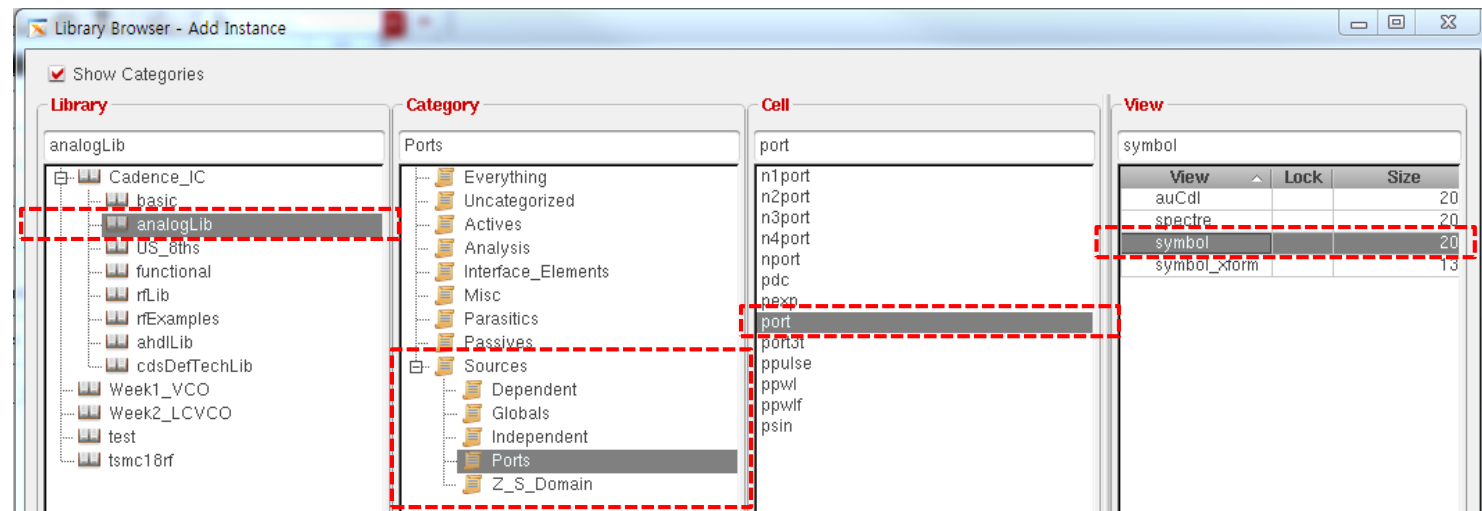- Port
 - Show Categories check
 - analogLib → Sources → Ports → port → symbol





S-parameter Simulation Setup

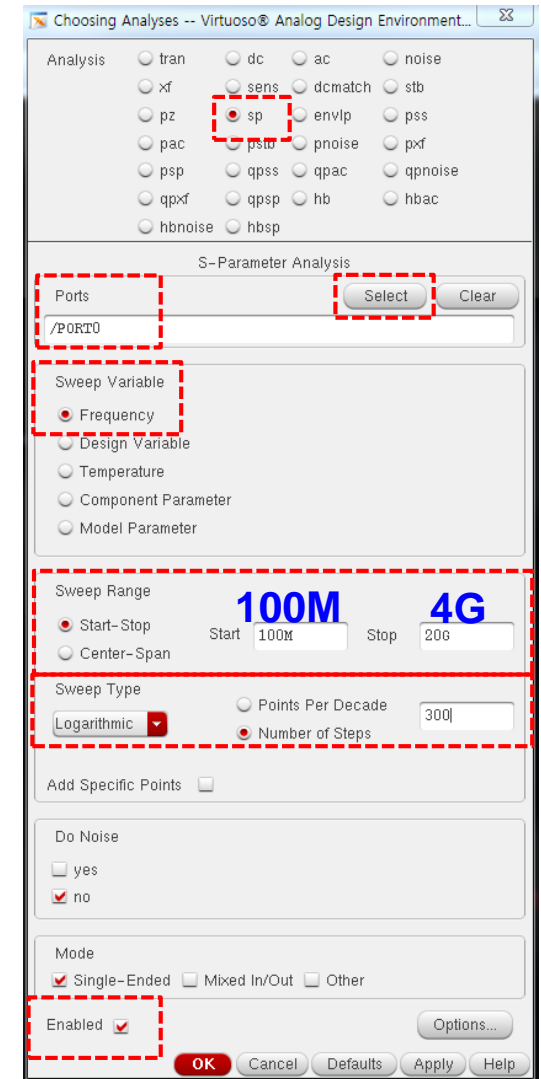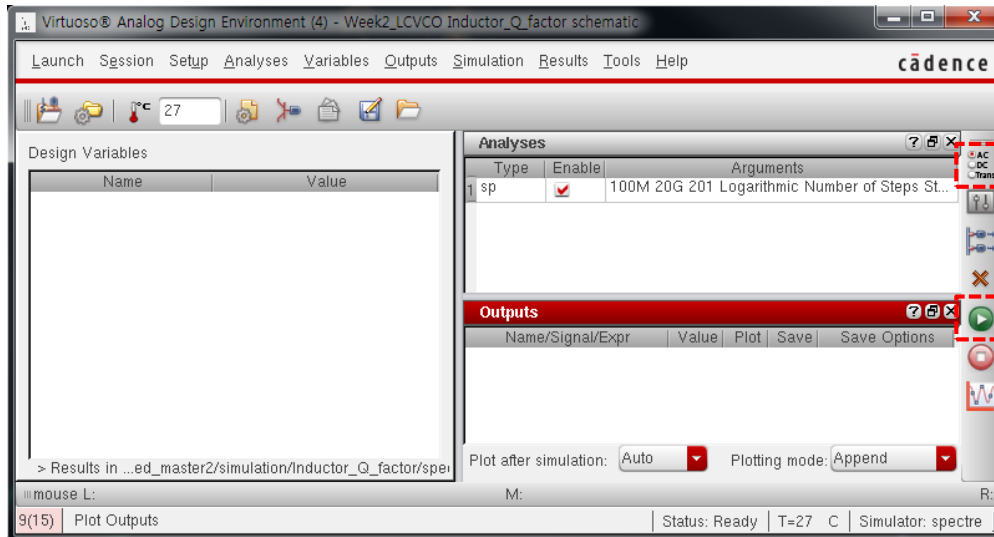- Simulation condition setting
 - Analysis : sp (S-Parameter Analysis)
 - Ports : Port0 (schematic node choice)
 - Sweep Variable : Frequency
 - Sweep Range : 100M ~ 5G
 - Sweep Type : Logarithmic
 - Number of Steps : 301
 - Enabled check → OK → Netlist and Run



Plotting Z-parameter

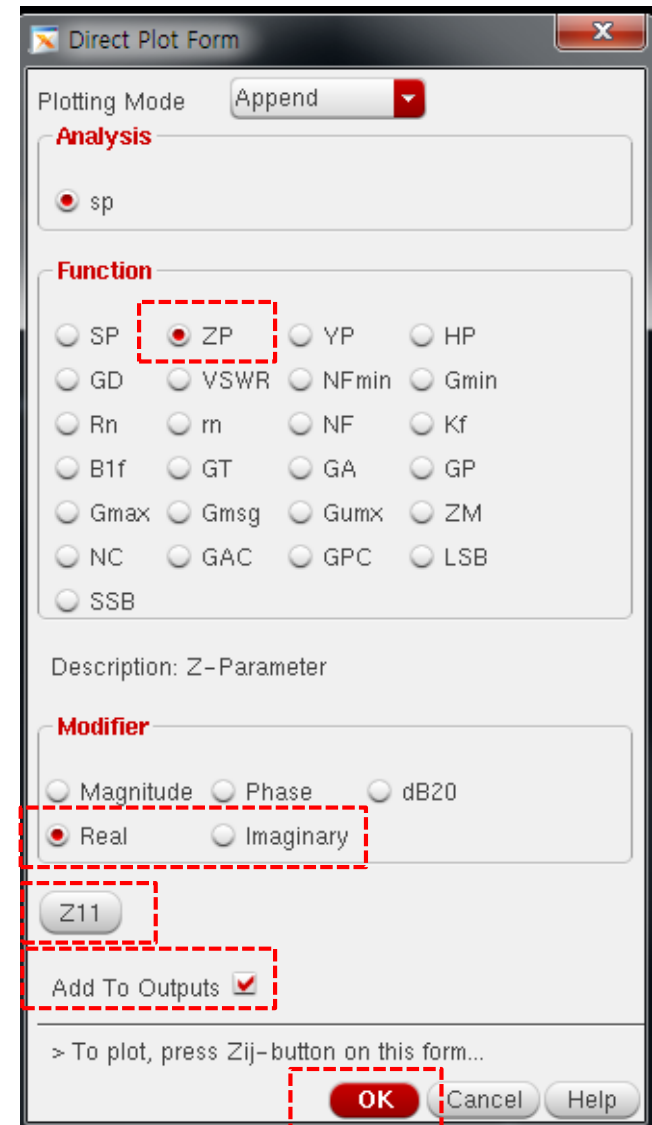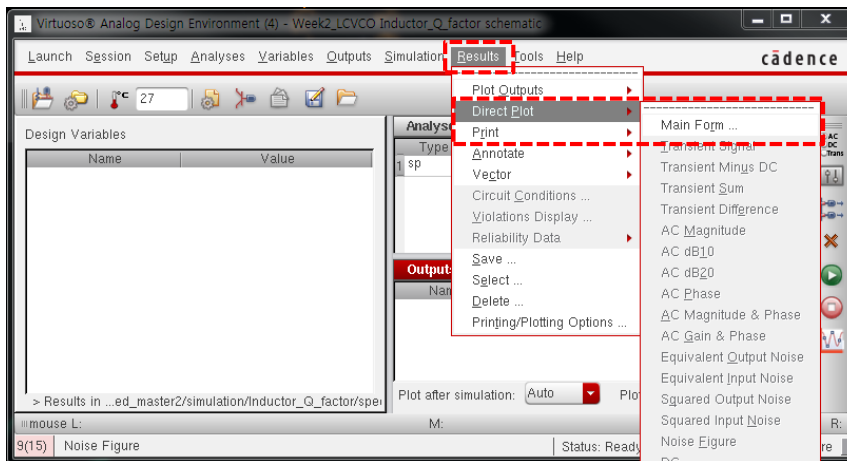- Simulation condition setting
 - Results → Direct Plot → Main Form
 - Function : ZP
 - Add To Outputs choice
 - Modifier : Real → Z11 and Imaginary → Z11
 - OK




Z-parameter Results

- $Z = R + j\omega L$
 - Resistance = Real [Z11]
 - Inductance = Imaginary [Z11] / ω
 - Check the SRF(self resonance frequency)




< Equivalent circuit of inductor >

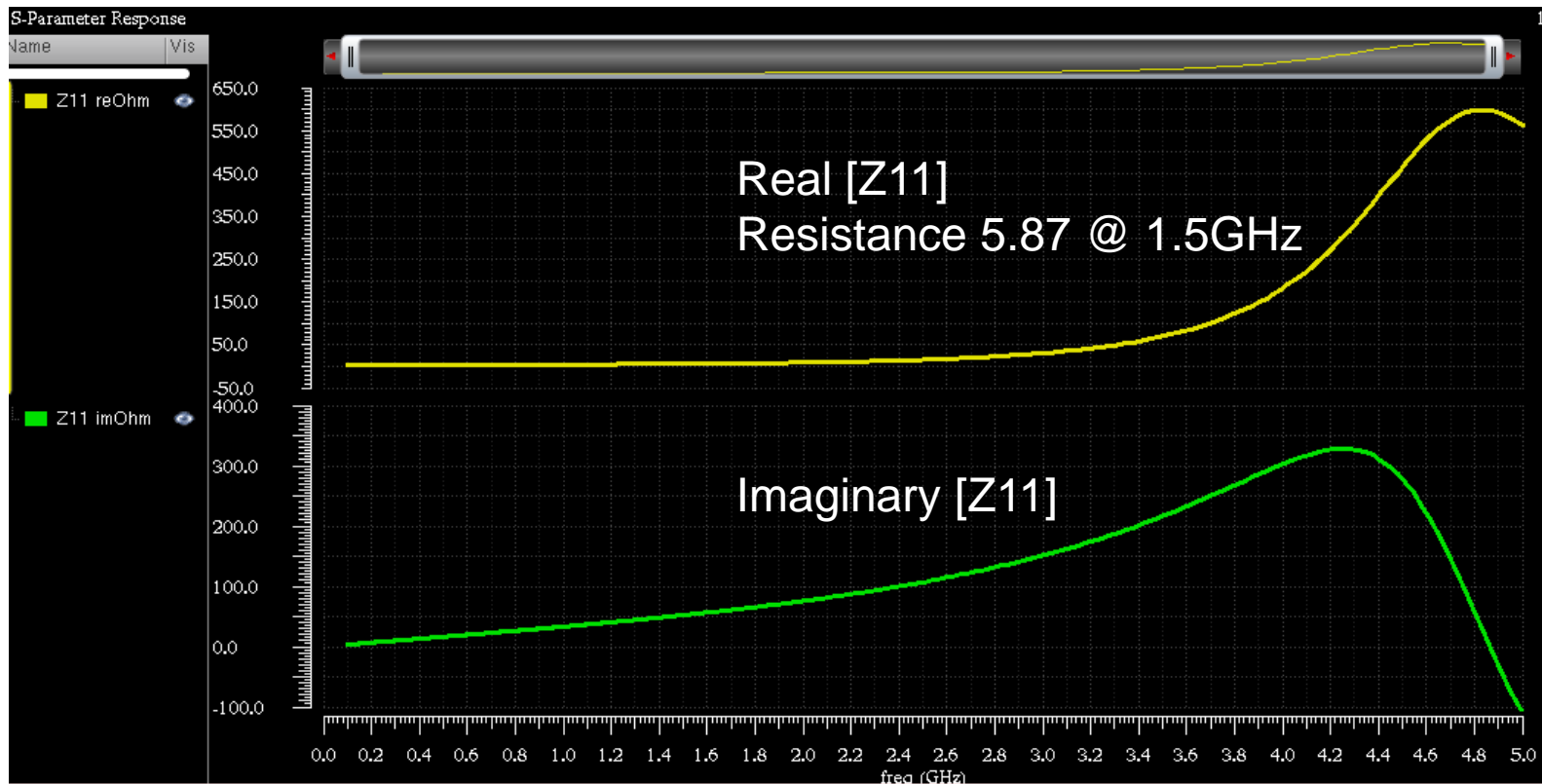


Inductance

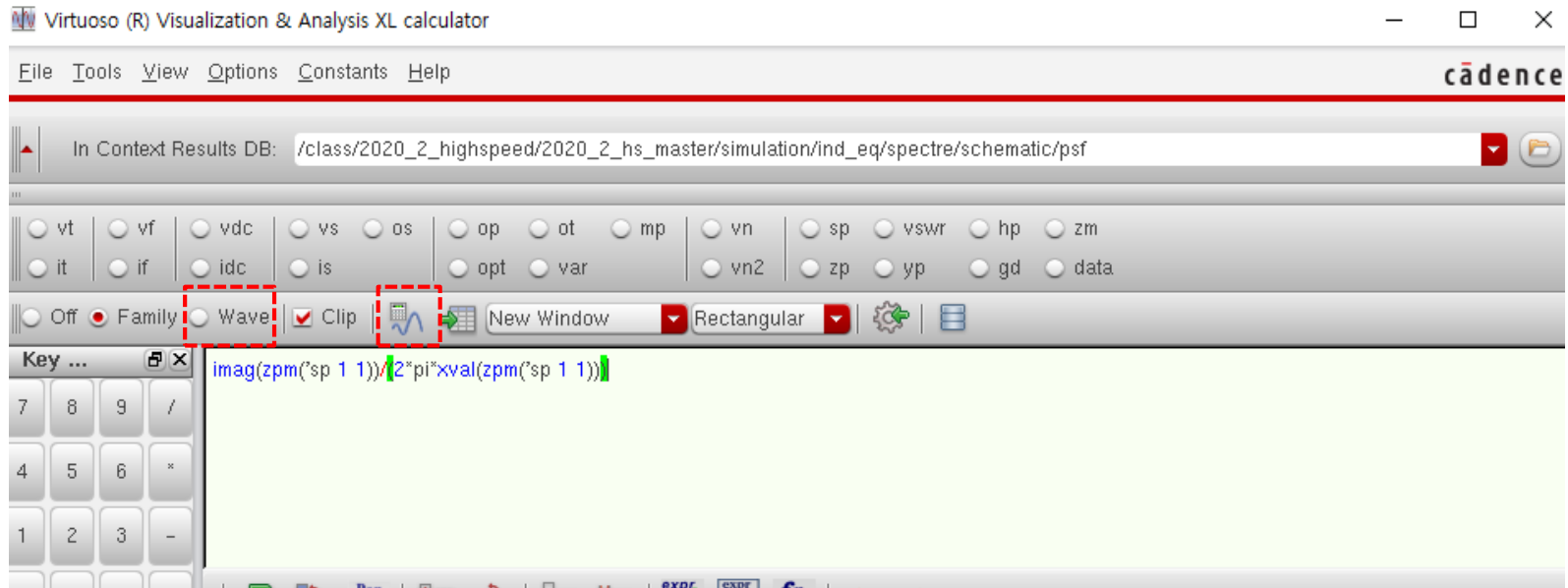- Simulation condition setting
 - $L = \frac{\omega L}{\omega} = \frac{\text{Imag}[Z_{11}]}{\omega}$
 - Calculator (Visualization & Analysis XL)
 - Wave choice → `imag(zpm('sp 1 1'))/(2*pi*xval(zpm('sp 1 1')))`



Inductance

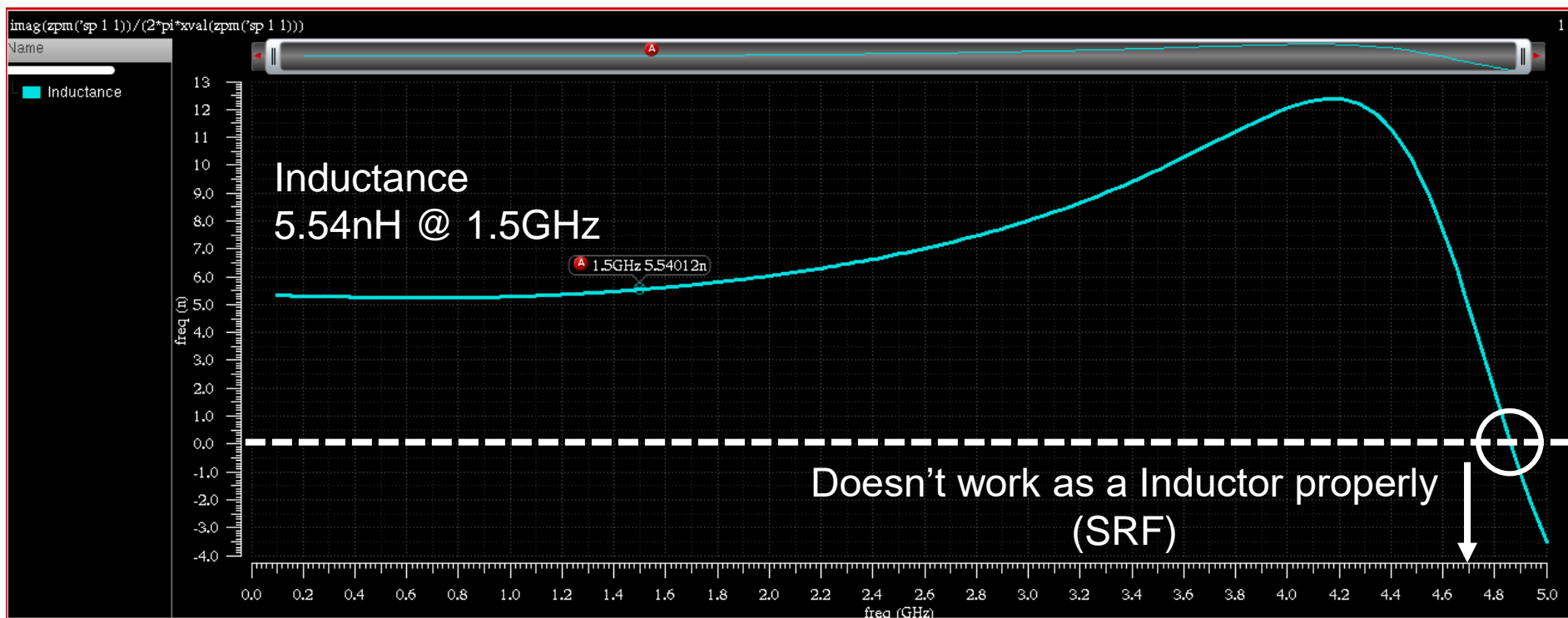- Inductance simulation
 - Inductance : 5.54nH @ 1.50GHz




Q-factor

- In an series RL circuit


$$Q = \omega \frac{\text{energy stored}}{\text{energy loss}} = \frac{\omega L}{R} = \frac{\text{imag}(Z_{11})}{\text{real}(Z_{11})}$$

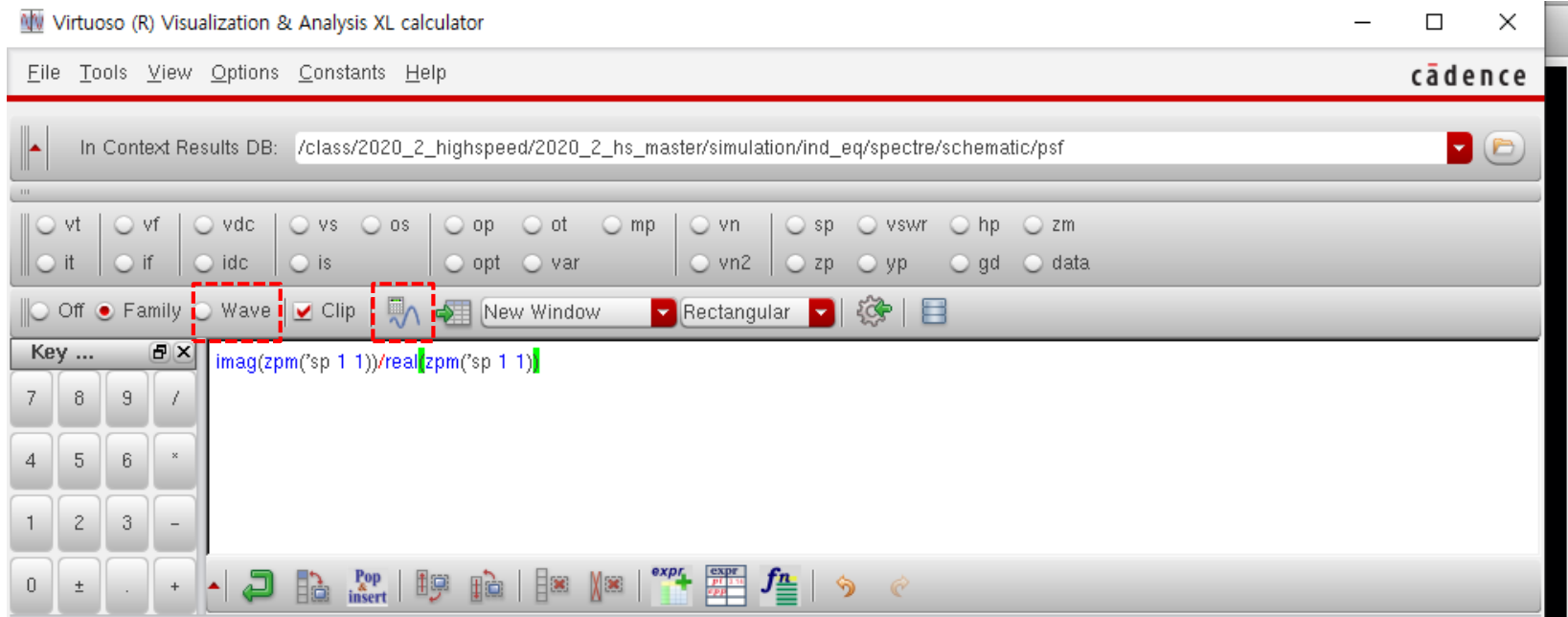- Calculator (Visualization & Analysis XL)
- Wave choice → `imag(zpm('sp 1 1))/real(zpm('sp 1 1))`



Q-factor Results

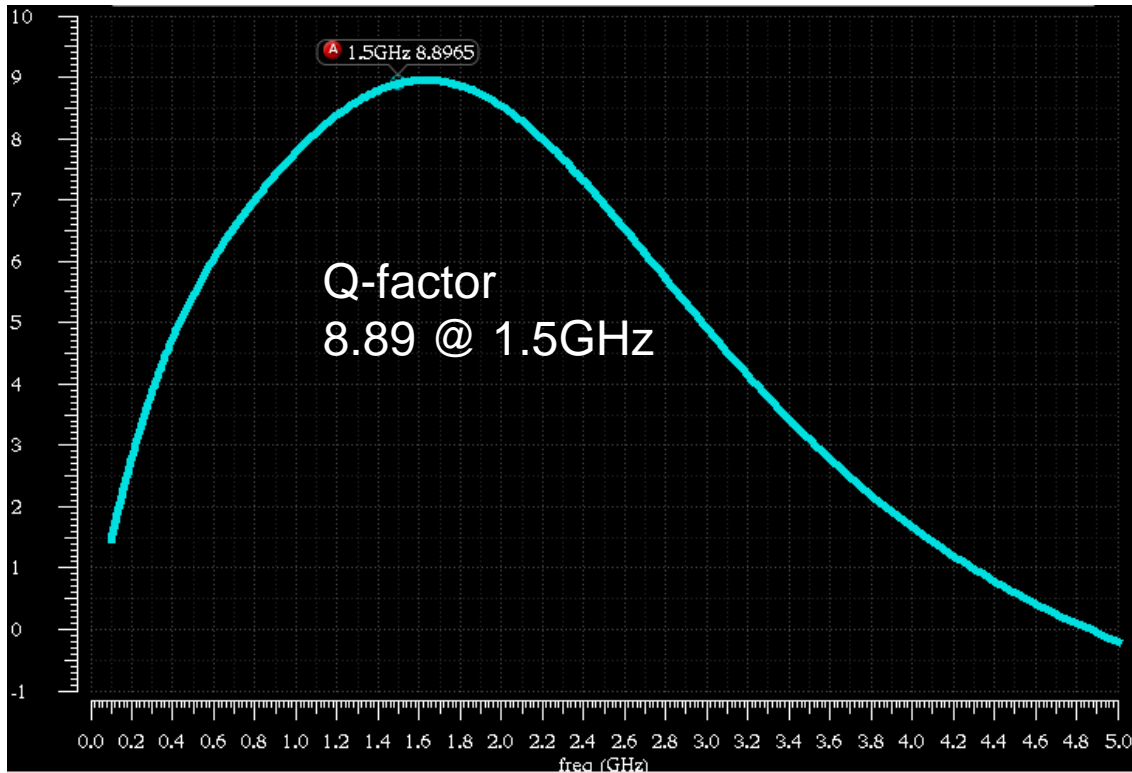- Inductor Q-factor simulation
 - Inductor Q-factor : 8.89 @ 1.50GHz



Edit Object Properties

Apply To:


Show: ☐ system ☒ user ☒ CDF

Property	Value	Display
Library Name	tsmc18rf	<input type="button" value="off"/>
Cell Name	ind_sym	<input type="button" value="value"/>
View Name	symbol	<input type="button" value="off"/>
Instance Name	L3	<input type="button" value="off"/>



CDF Parameter	Value	Display
Model name	spiral_s3_sym	<input type="button" value="off"/>
L_value_single_ended(H)	5.54128e-11	<input type="button" value="off"/>
Q_factor_single_ended	8.88728	<input type="button" value="off"/>
L_value_differential(H)	5.31668e-11	<input type="button" value="off"/>
Q_factor_differential	10.0172	<input type="button" value="off"/>
temp(C)	27 C	<input type="button" value="off"/>
freq(Hz)	1.5G Hz	<input type="button" value="off"/>
Inductor_Width(M)	30u	<input type="button" value="off"/>
Inductor_Space(M)	3u M	<input type="button" value="off"/>
Inner_Radius(M)	90u M	<input type="button" value="off"/>
Number_Of_Turns	4	<input type="button" value="off"/>
multiplier	1	<input type="button" value="off"/>
Hard_constraint	<input checked="" type="checkbox"/>	<input type="button" value="off"/>

Accumulation Mode Varactor


- On (Accumulated channel)

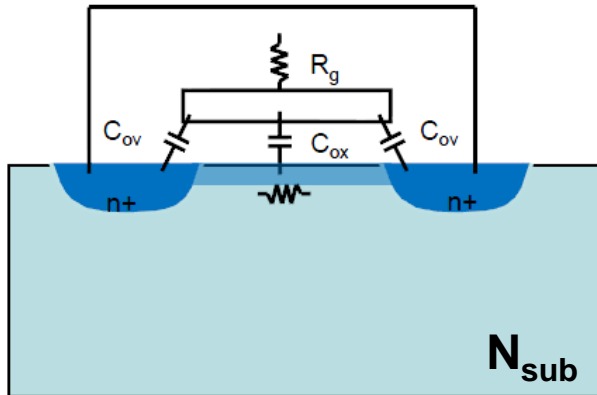

- OFF (Depleted)

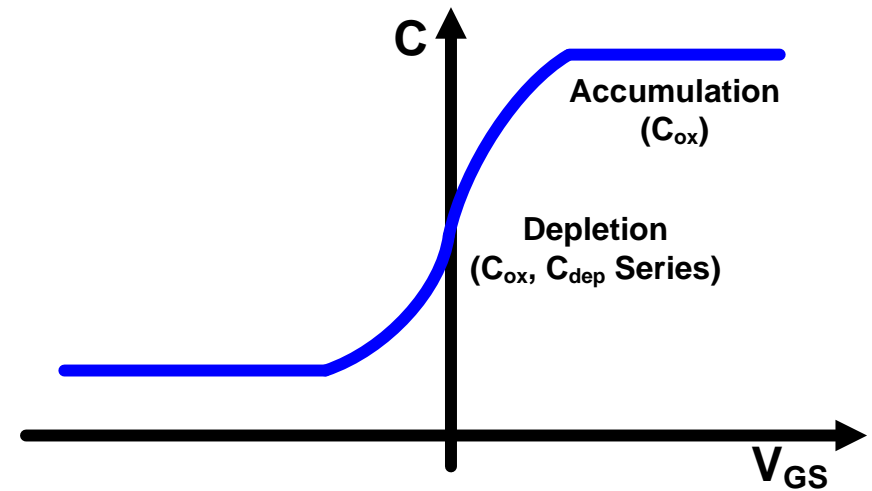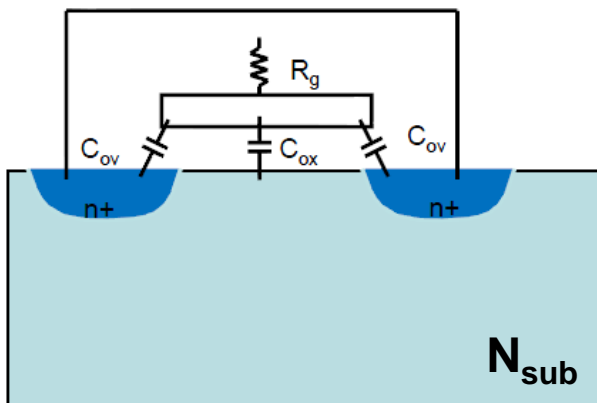


Oscillator with Varactor

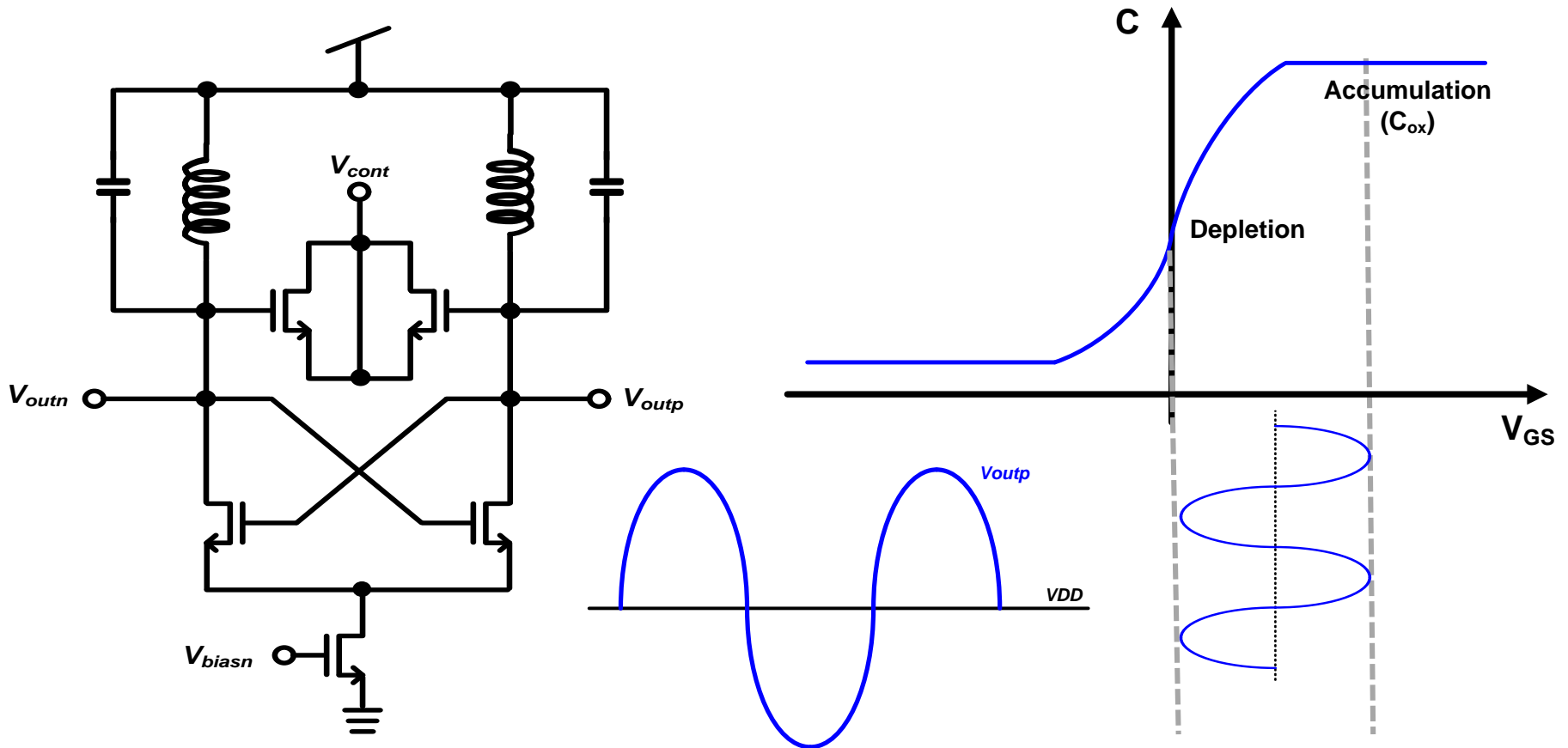

- Change average capacitance from control voltage.


Varactor

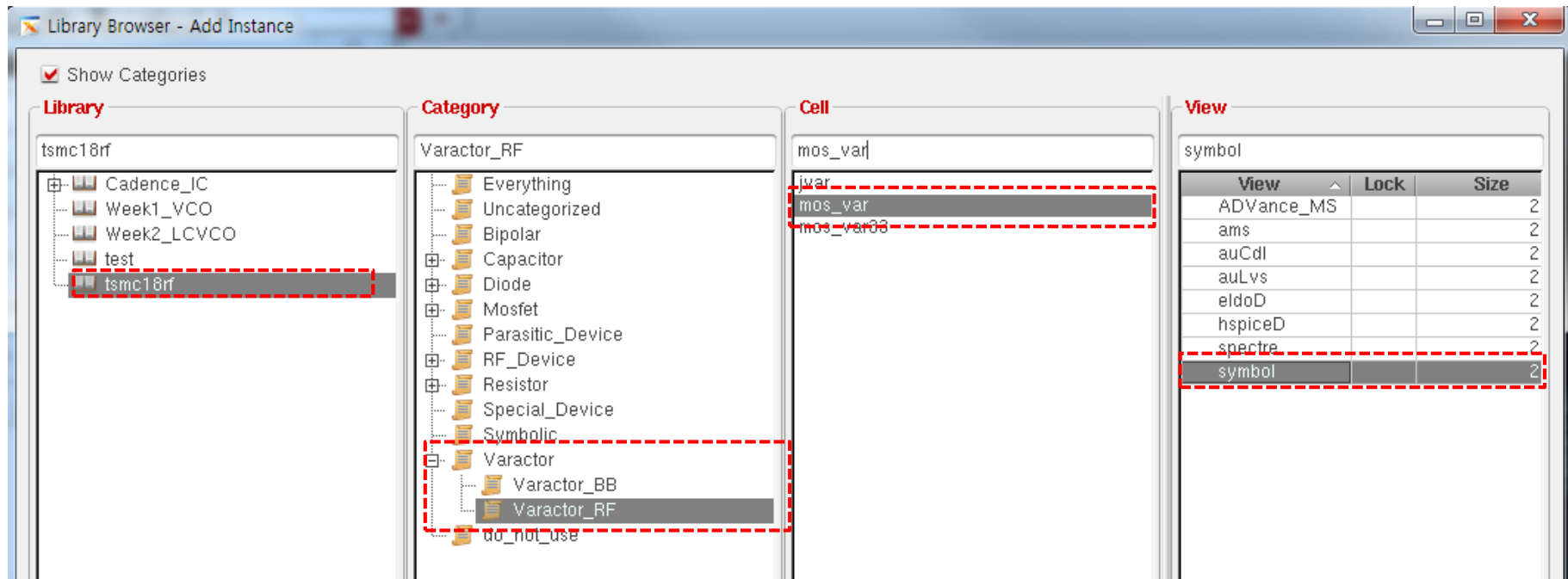- Varactor selection
 - Tsmc18rf → Varactor → Varactor_RF → mos_var → symbol




Varactor Modeling

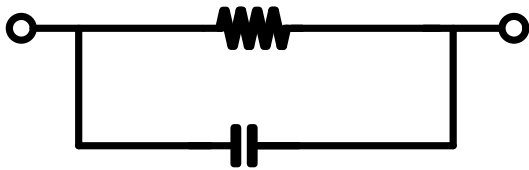
- An equivalent circuit model of varactor
 - Parallel connection of resistance and capacitance
 - Analyze capacitance into using Y-parameter



< Equivalent circuit of varactor >

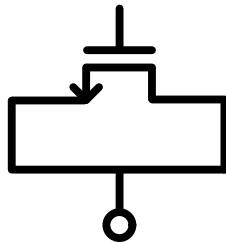



Vcontrol
< Varactor structure >

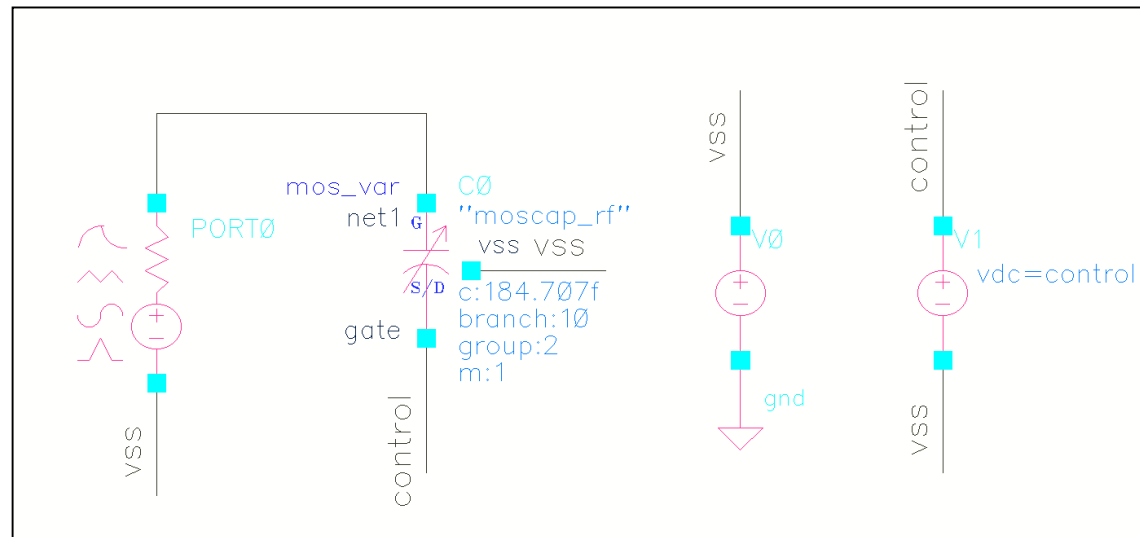

< Test schematic >



S - Parameter

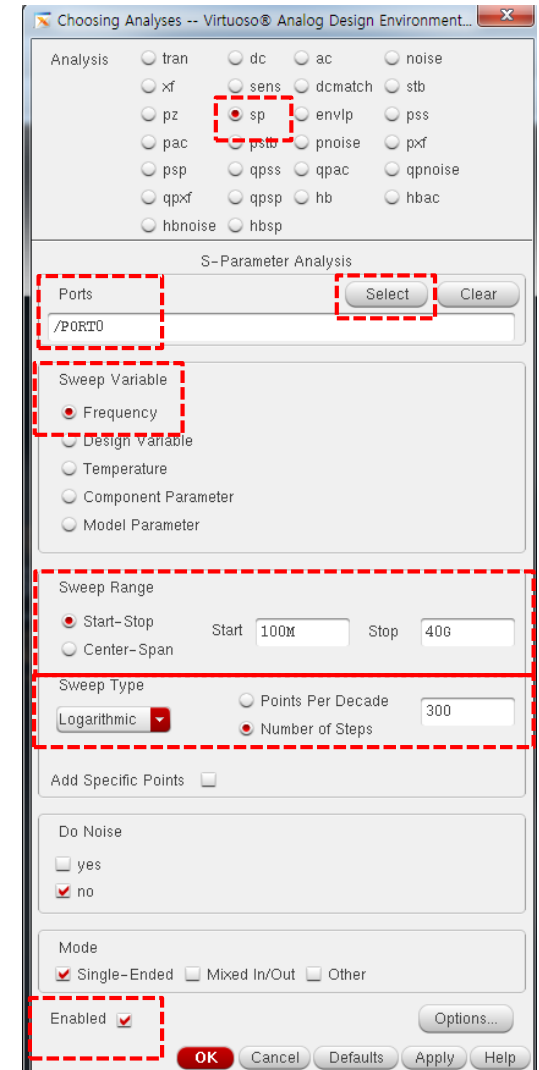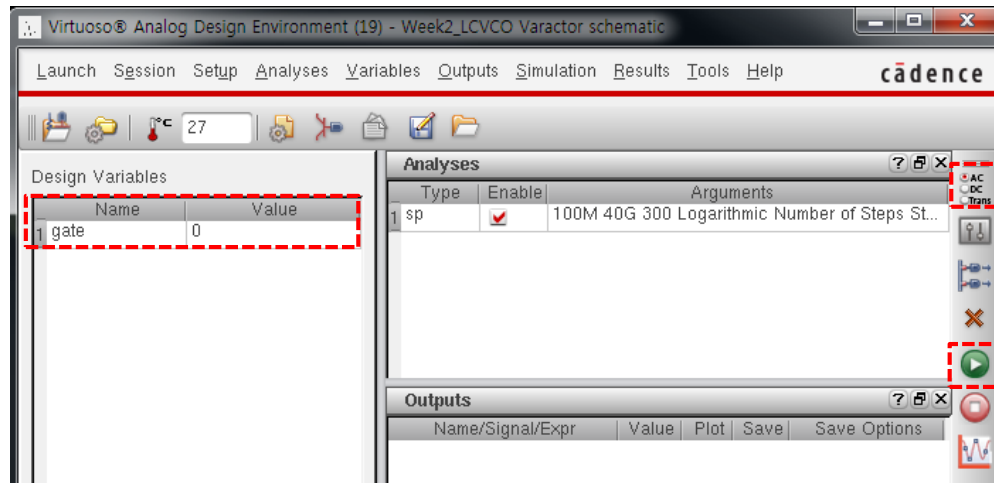- Simulation condition setting
 - Analysis : sp (S-Parameter Analysis)
 - Ports : Port0 (schematic node choice)
 - Sweep Variable : Frequency
 - Sweep Range : 100M ~ 40G
 - Sweep Type : Logarithmic
 - Number of Steps : 301
 - Enabled check → OK → Netlist and Run





Plotting Y-Parameter

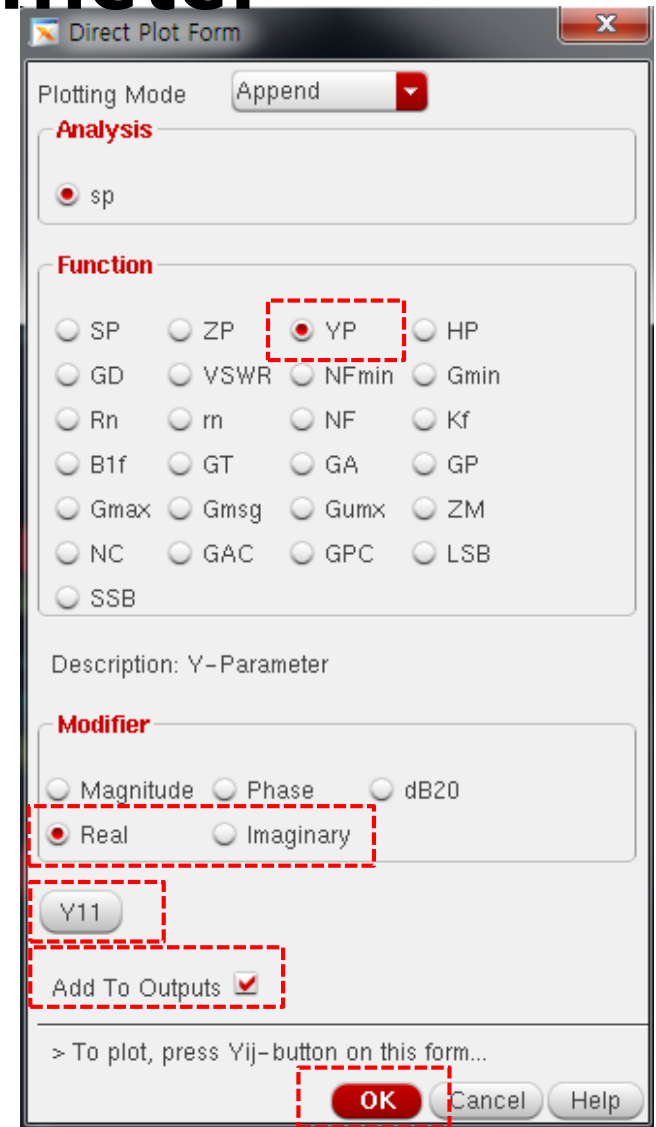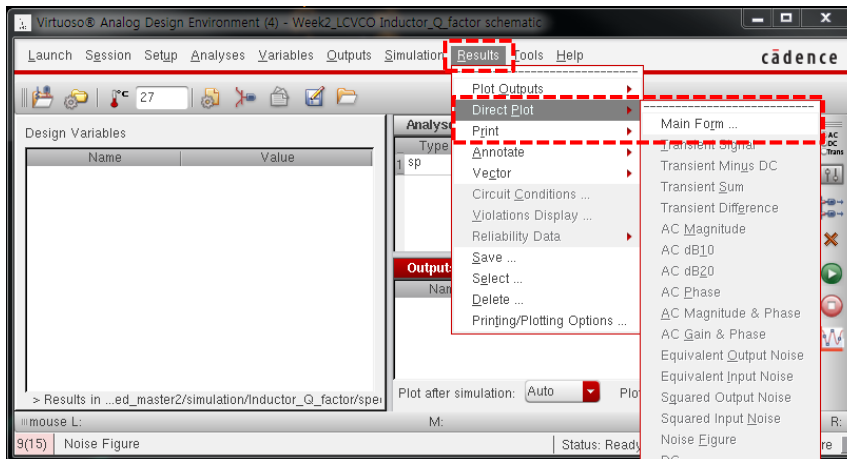- Simulation condition setting
 - Results → Direct Plot → Main Form
 - Function : YP
 - Add To Outputs choice
 - Modifier : Real → Y11 and Imaginary → Y11
 - OK



Y- Parameter

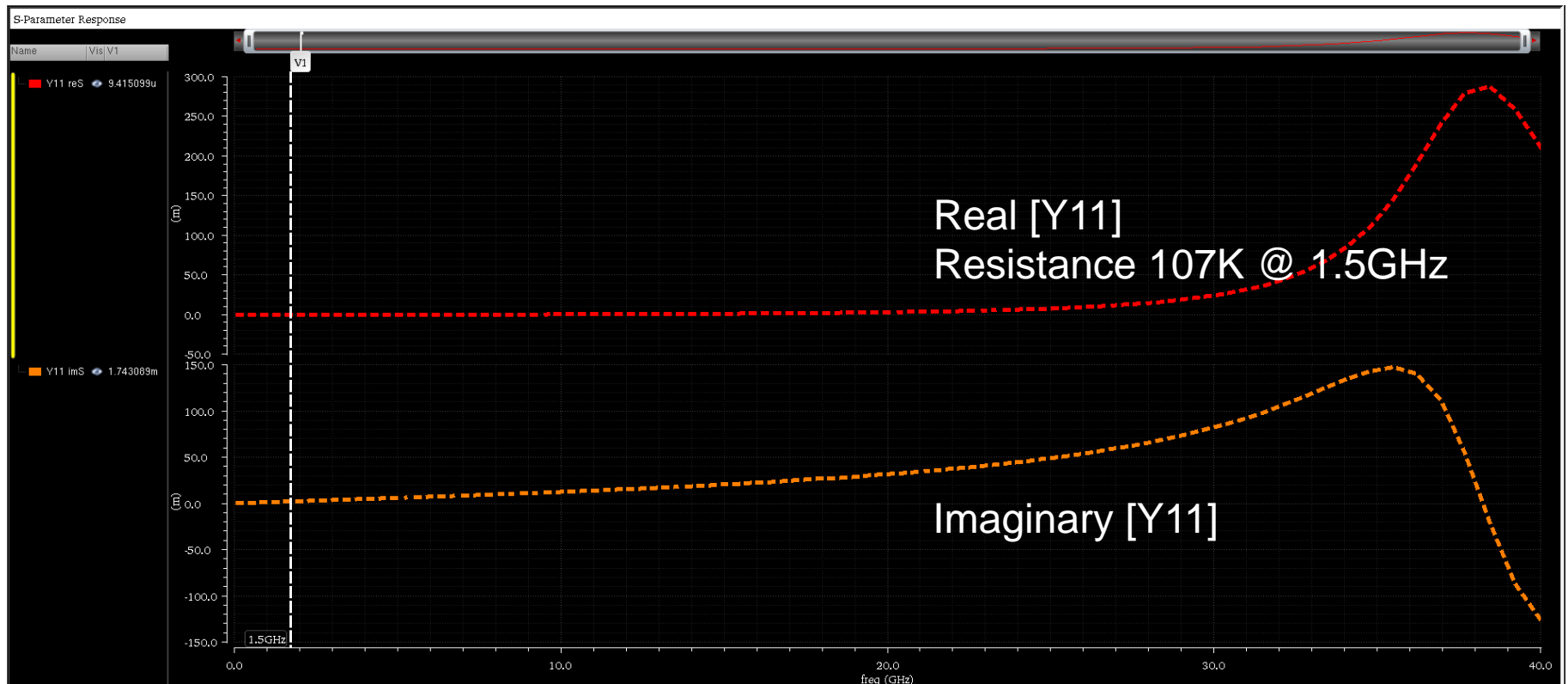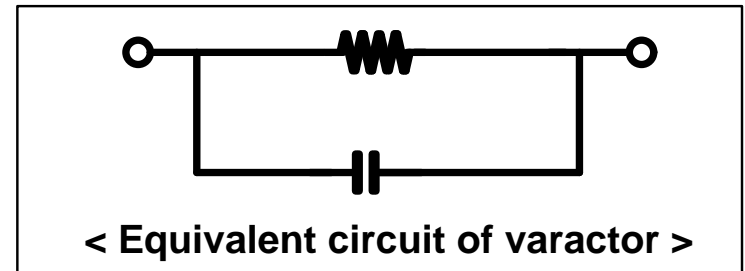- $Y = 1/R + j\omega C$
 - Resistance = $1 / \text{Real} [Y_{11}]$
 - Capacitance = $\text{Imaginary} [Y_{11}] / \omega$



Capacitance


- Simulation condition setting

- $C = \frac{\omega C}{\omega} = \frac{\text{Imag}[Y_{11}]}{\omega}$
- Calculator (Visualization & Analysis XL)
- Wave choice → `imag(yp(1 1 ?result "sp")) / (2*pi*xval(yp(1 1 ?result "sp")))`



Capacitance

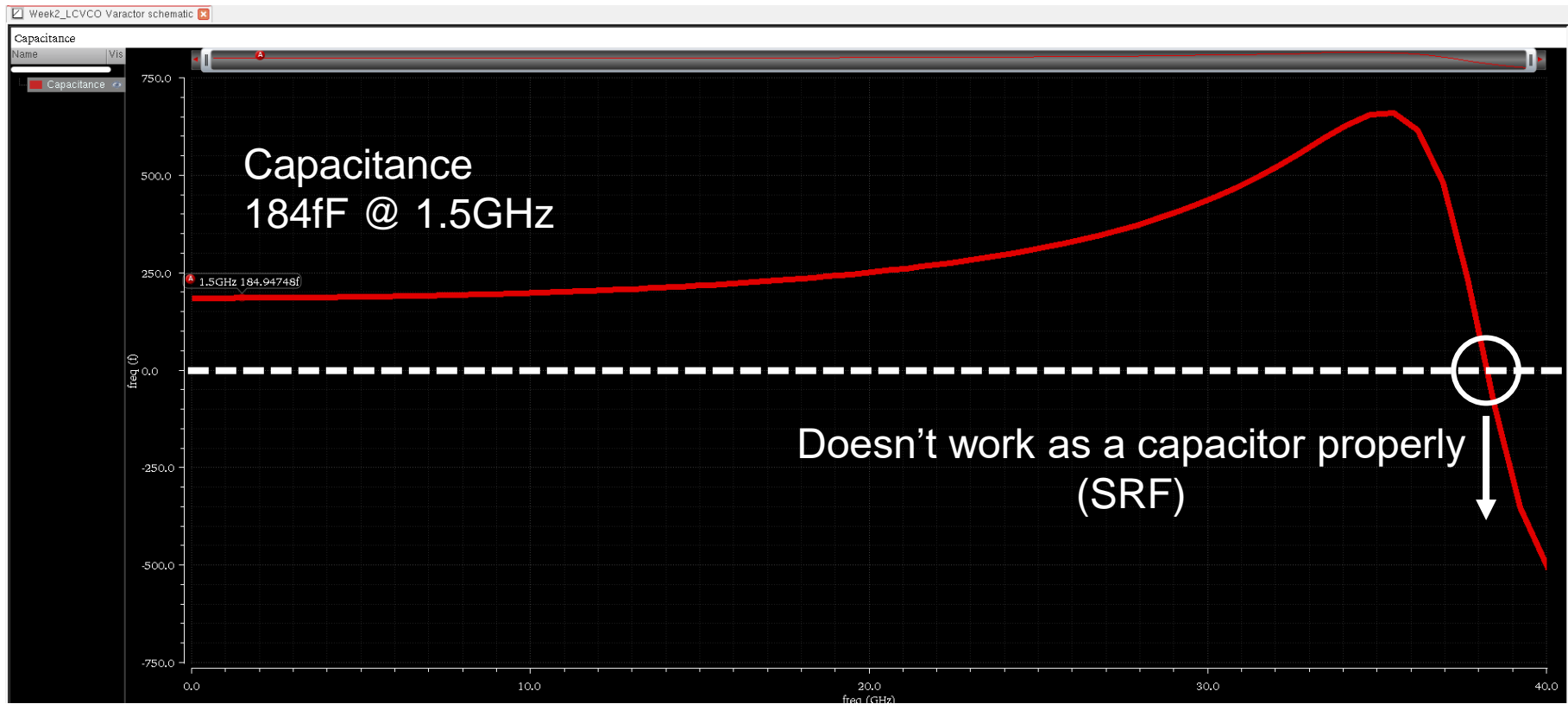- Capacitance simulation
 - Capacitance : 184fF @ 1.50GHz



Q-factor

- In an parallel RC circuit..


$$Q = \omega \frac{\text{energy stored}}{\text{energy loss}} = \omega CR = \frac{\text{imag}(Y11)}{\text{real}(Y11)}$$

- Calculator (Visualization & Analysis XL)
- Wave choice → `imag(yprm('sp 1 1))/real(yprm('sp 1 1))`




Q-factor Results

- Varactor Q-factor simulation

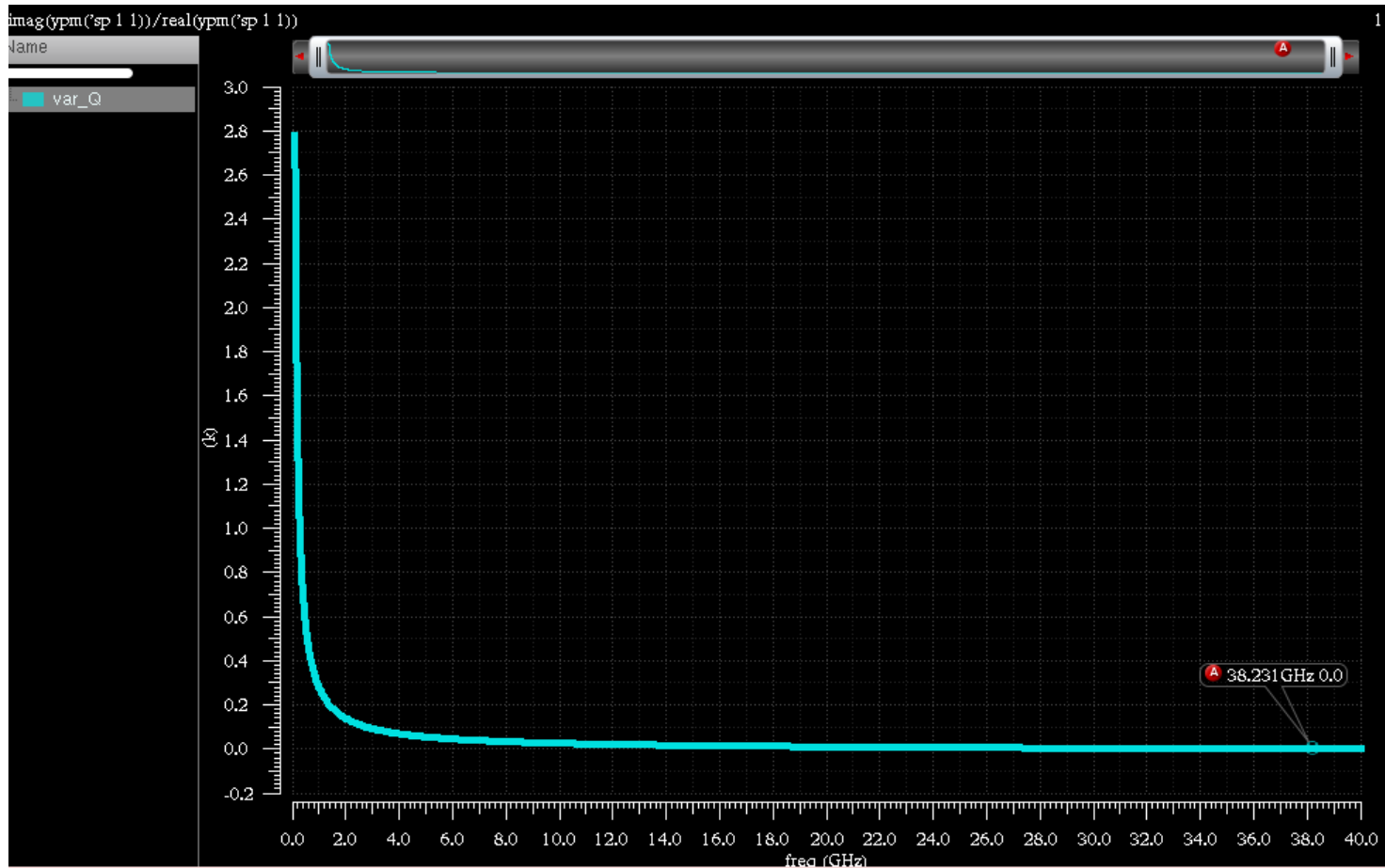


Capacitance

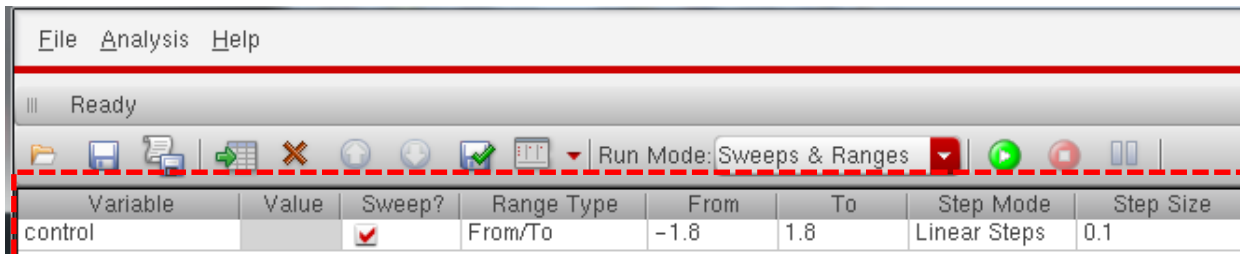- Control voltage sweep
 - Tools → Parametric Analysis
 - Voltage : -1.8V ~ 1.8V




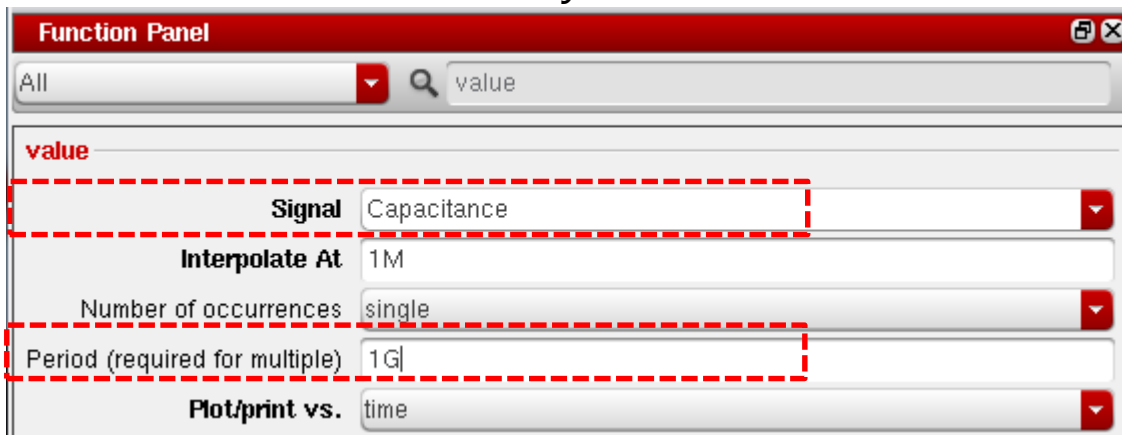- Calculator → Family → value → 파형 선택 (Capacitance) → Plot




Capacitance


- V_{SG} VS Capacitance

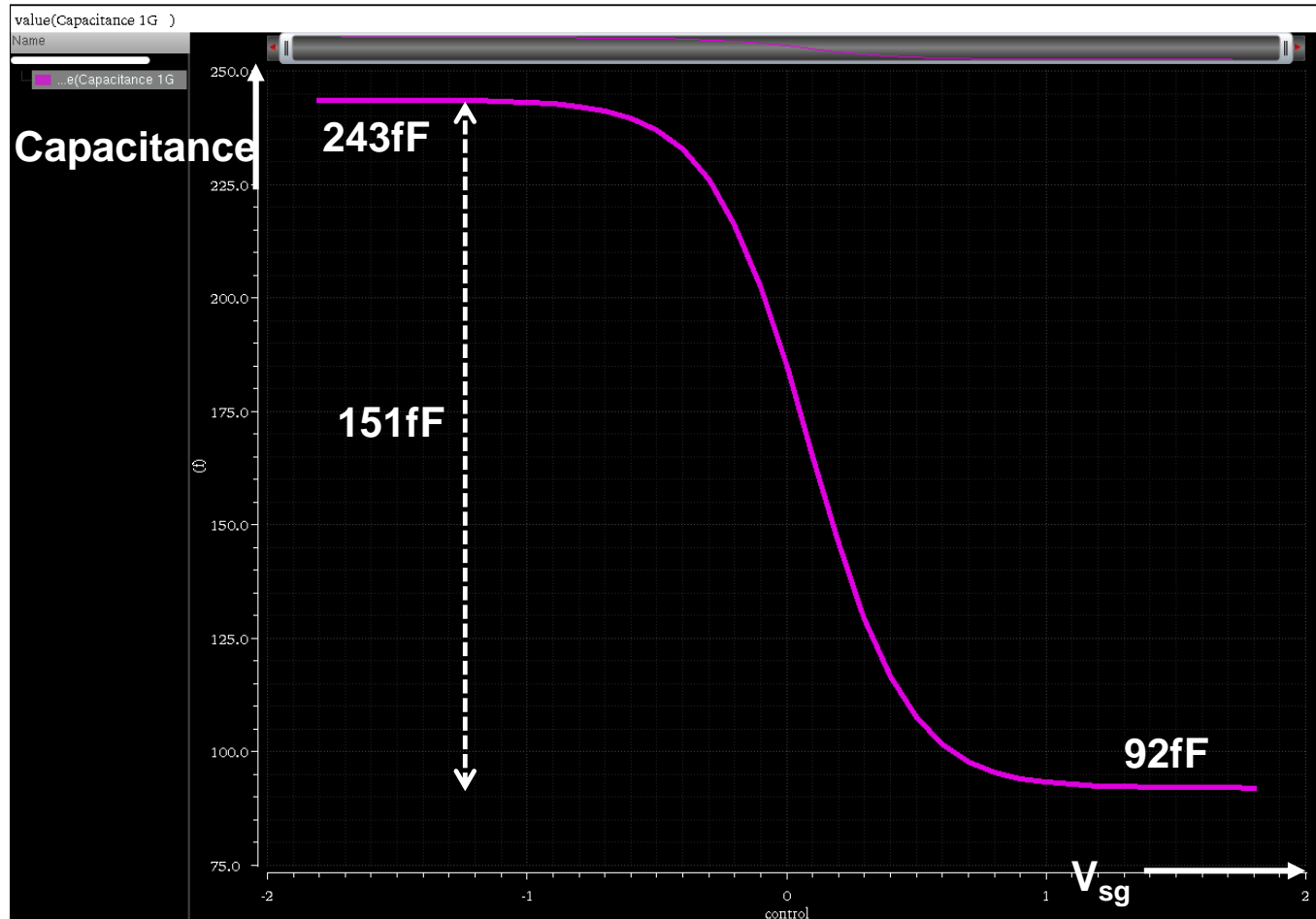

LC VCO Schematic




- Simulation LC VCO schematic

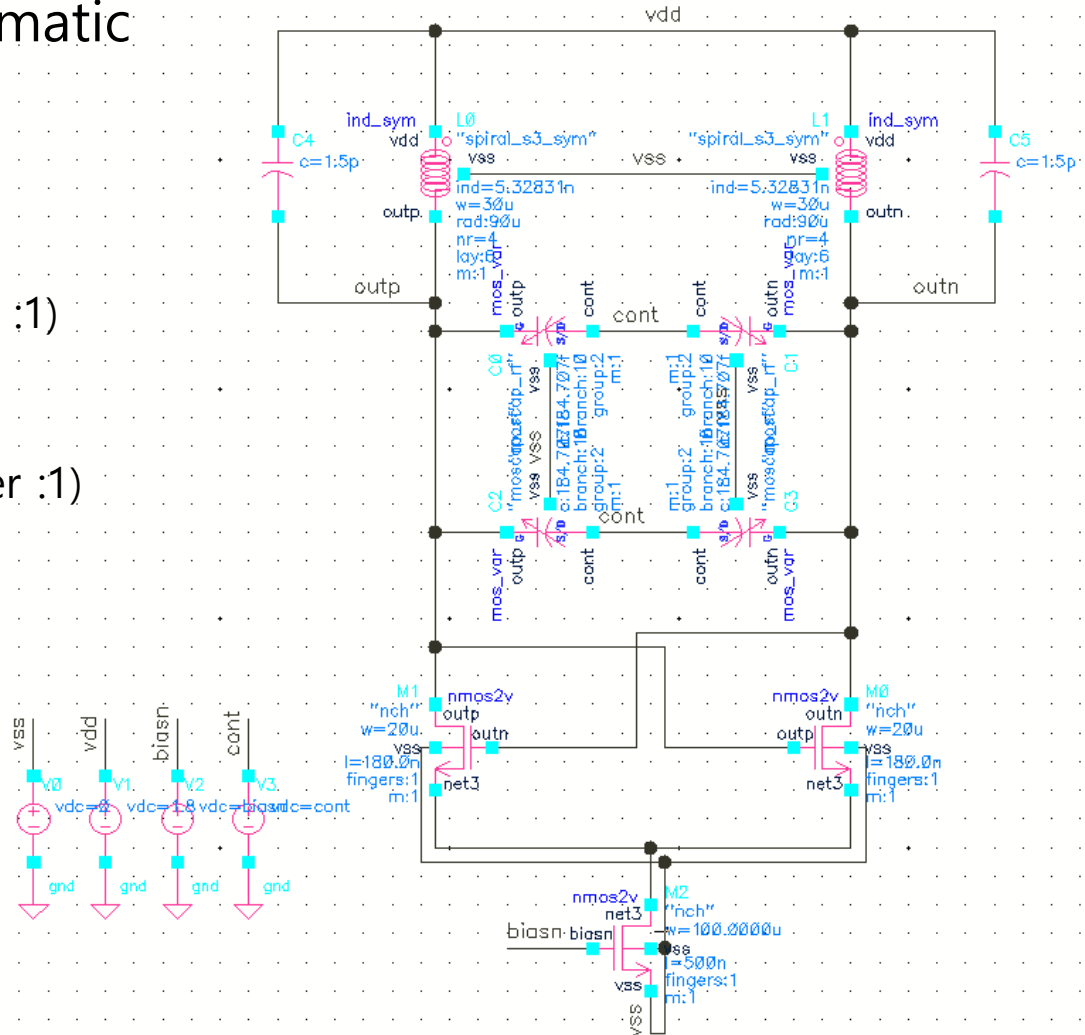- Inductor : 5.54nH
 - Capacitor : 1.5pF
 - Input NMOS
 - Length : 180n
 - Total Width : 20u (finger :1)
 - Source NMOS
 - Length : 500n
 - Total Width : 100u (finger :1)
 - Varactor
 - vdd : 1.8V
 - biasn : 0.8V
 - cont : 변수 지정 (cont)
 - Initial condition
outp & outn
:1.8V, 1.85V
- 






OSC Frequency ($V_{cont} = 0V$)

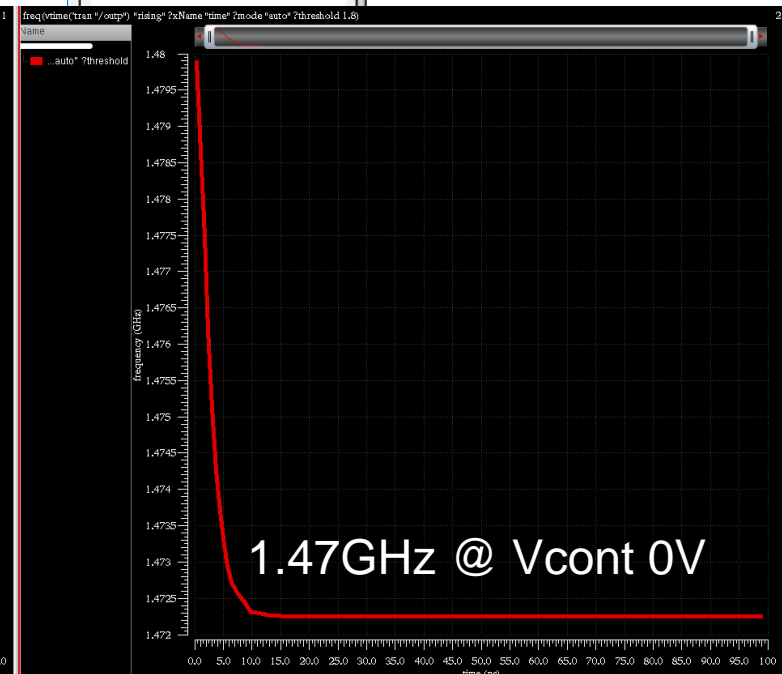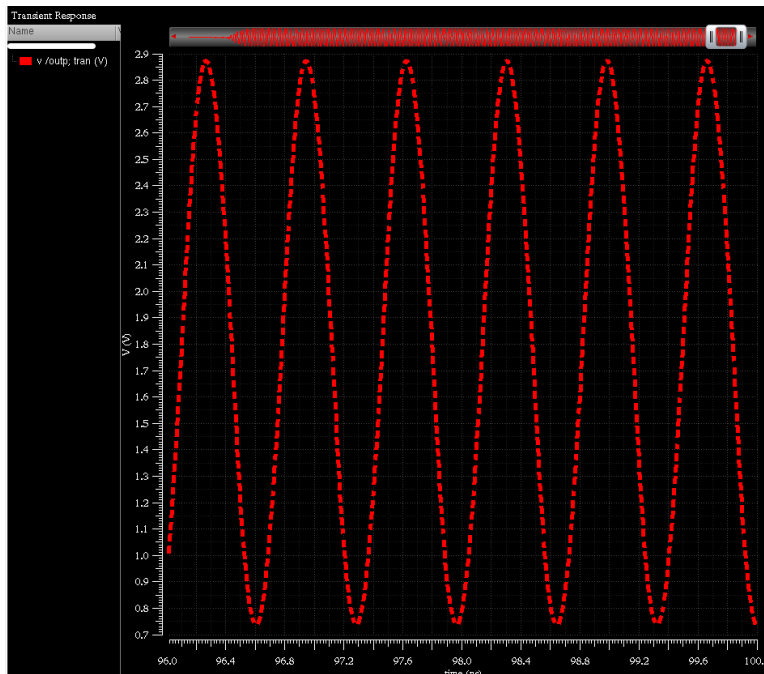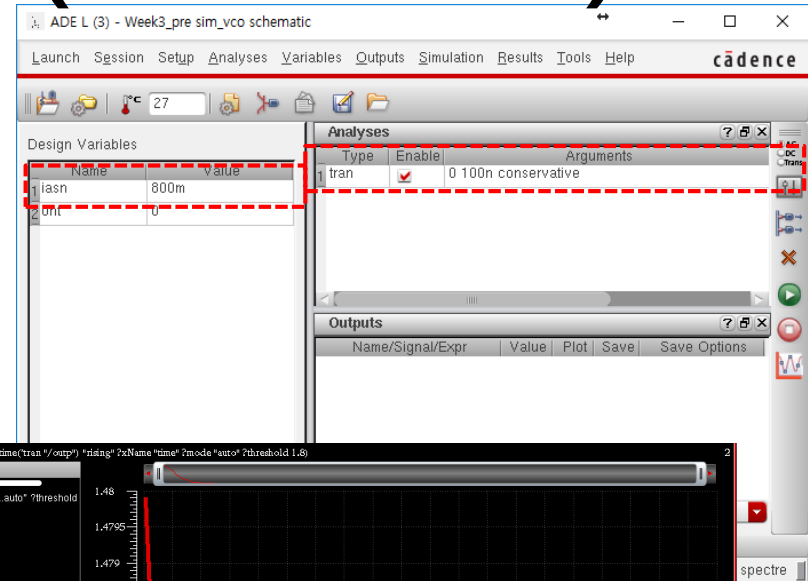- Control Voltage 0V
 - OSC frequency : 1.47GHz
 - Transient simulation (100ns)
 - Output 파형 및 Frequency 측정





OSC Frequency (Vcont = 1.8V)

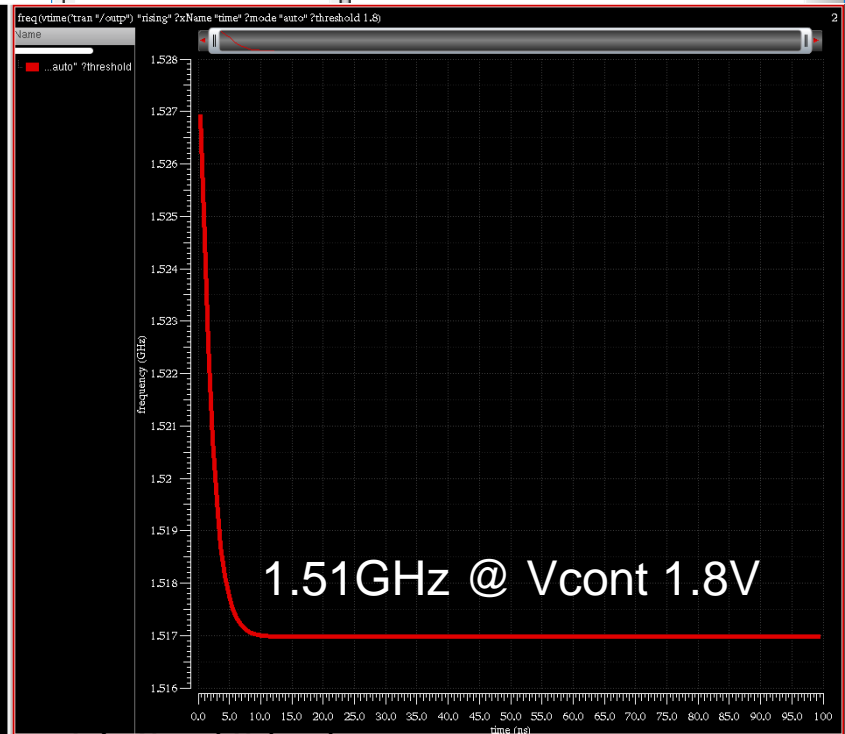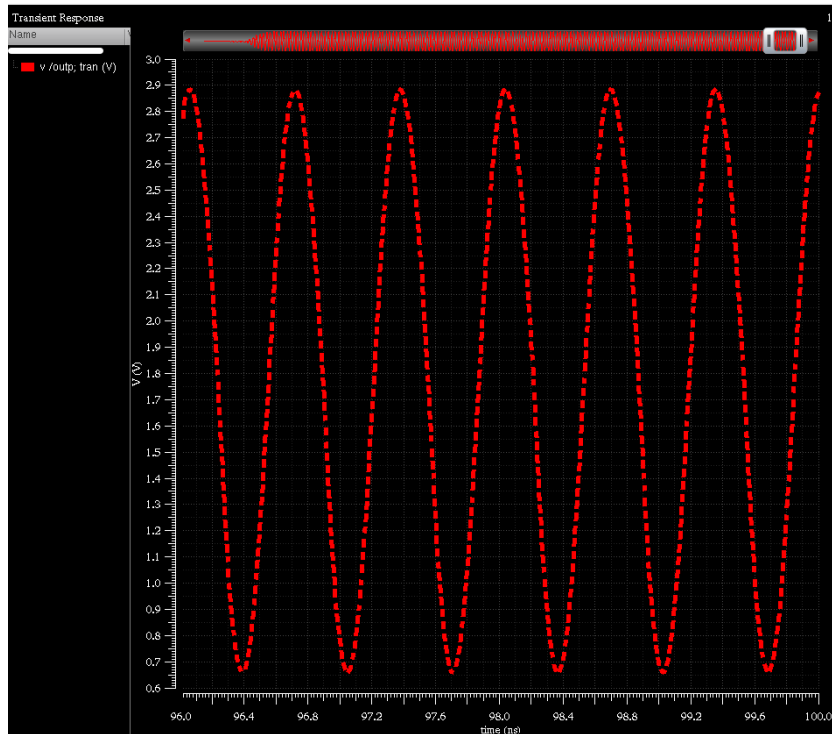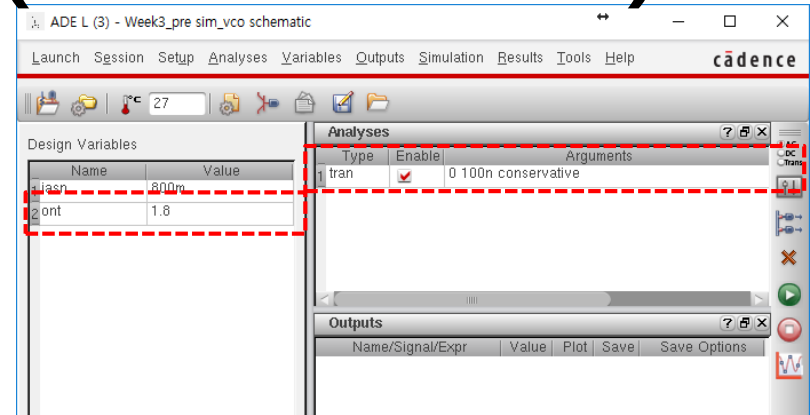- Control Voltage 1.8V
 - OSC frequency : 1.51GHz
 - Transient simulation (100ns)
 - Output 파형 및 Frequency 측정





Phase Noise (PSS)

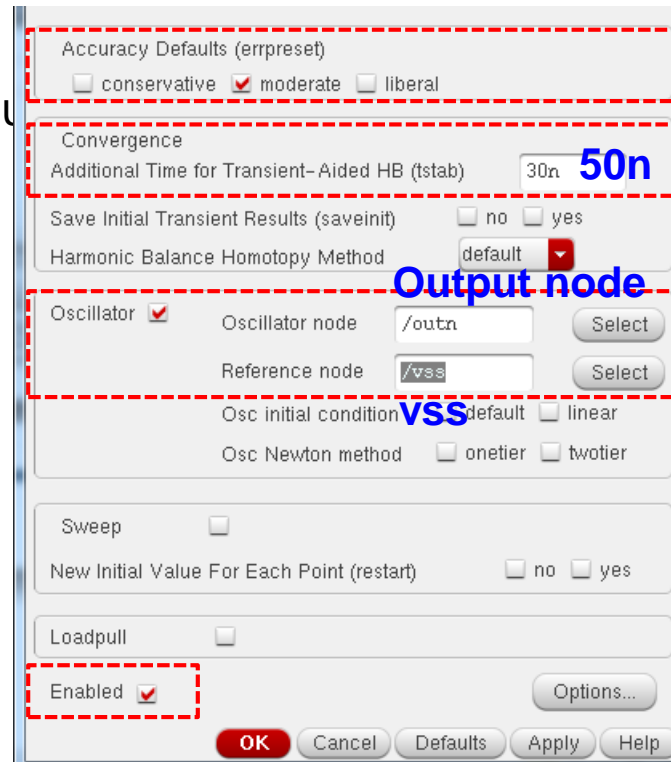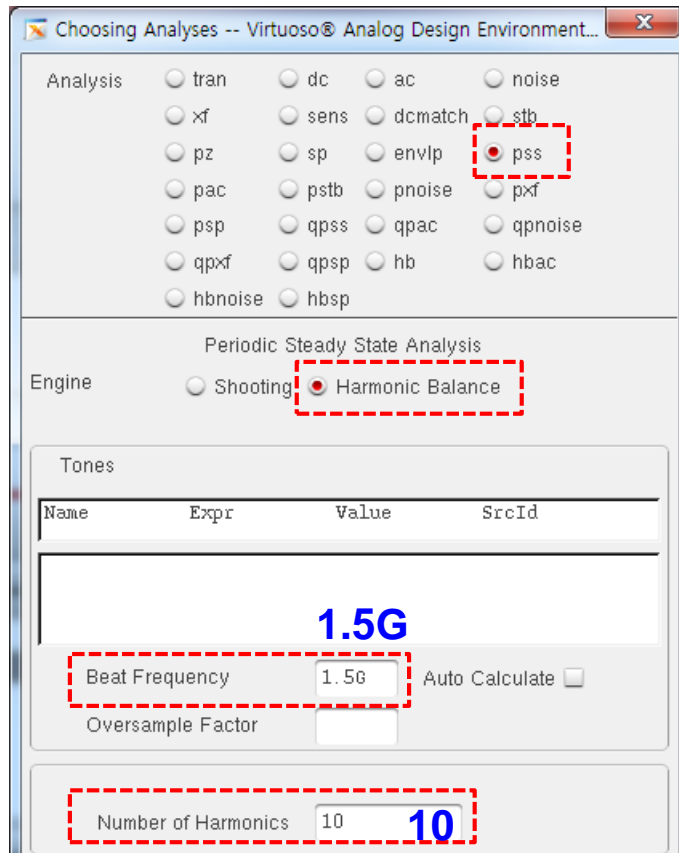

tstab : Oscillation
안정 구간 설정

Phase Noise (Pnoise)


- Pnoise
 - Setup PSS first, then Pnoise

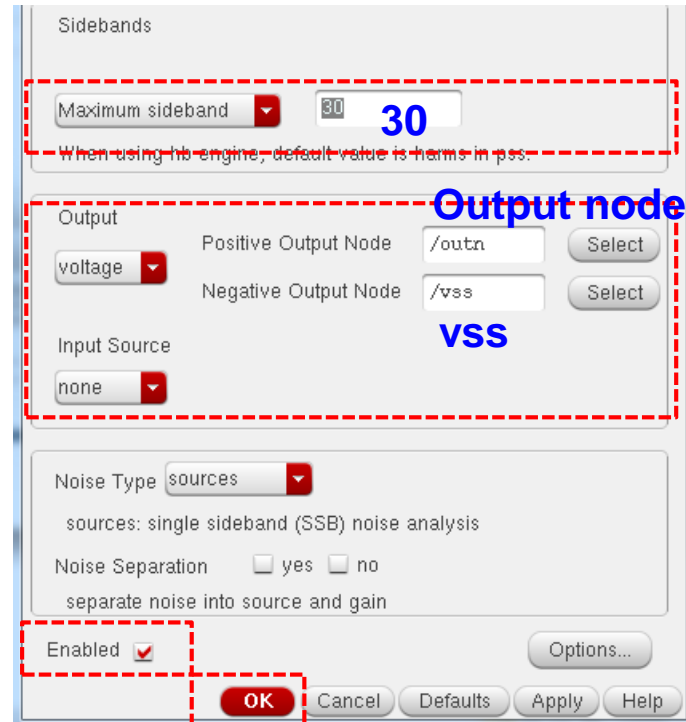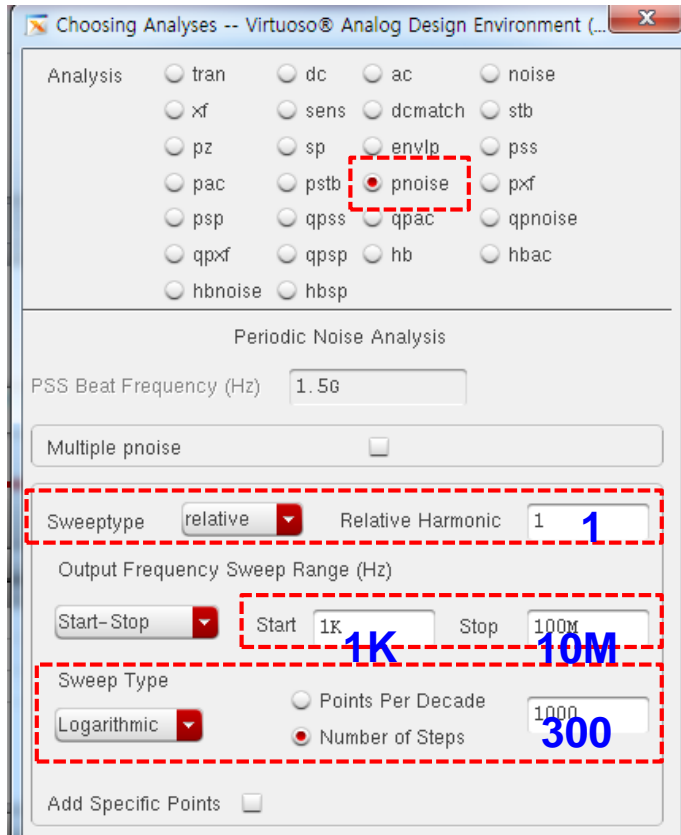

Output : Voltage 설정
Output Node 설정
Input : none


Phase Noise

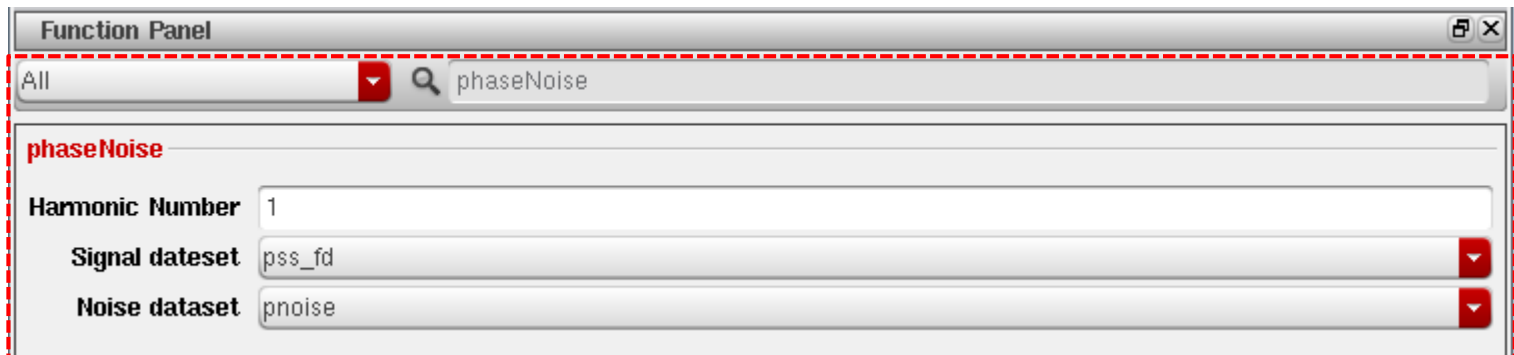- Phase noise
 - Calculator (Visualization & Analysis XL)
 - Function Panel (phaseNoise 입력)
 - Harmonic Number : 1
 - Signal dataset : pss_fd
 - Noise dataset : pnoise
 - Apply





Phase Noise

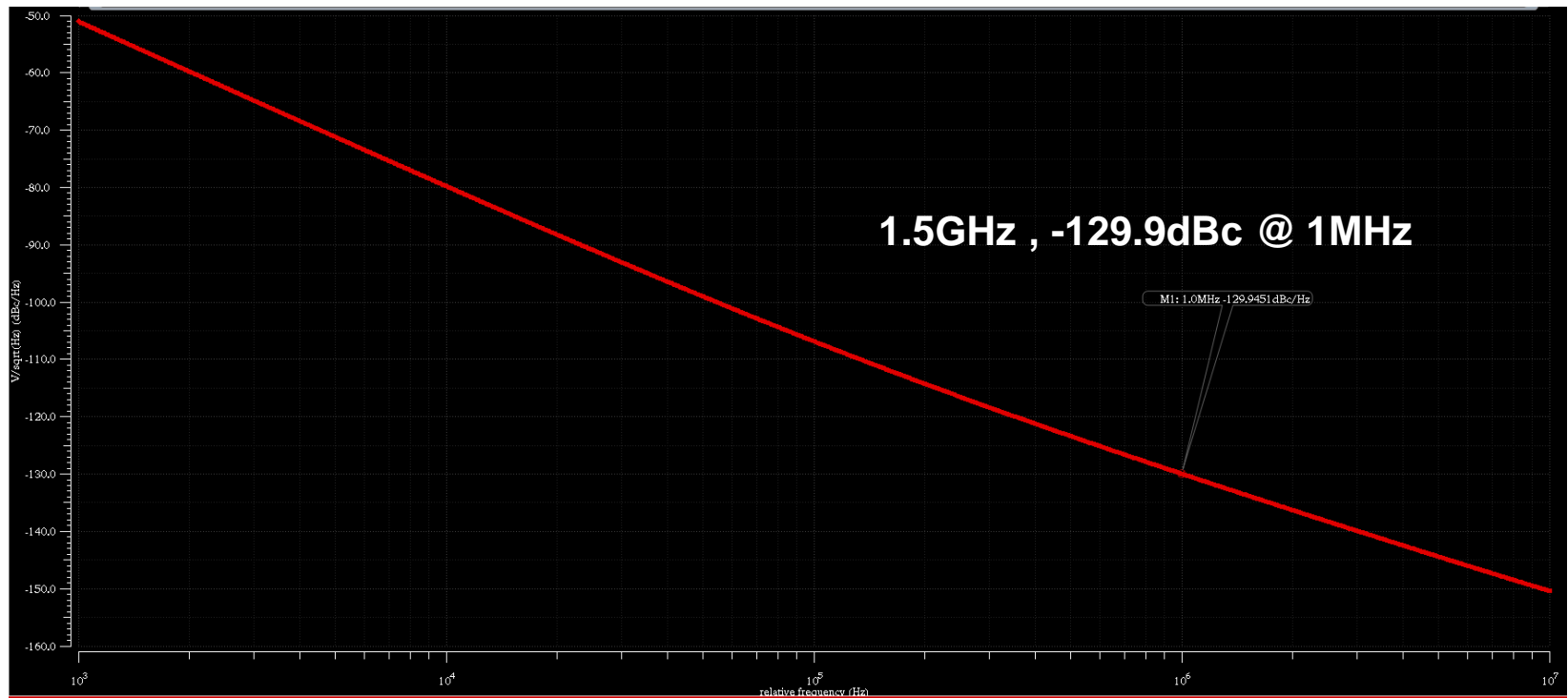- Phase noise
 - $V_{\text{cont}} = 1.48\text{V}$
 - 1.5GHz, -129.9dBc @ 1MHz





VCO Comparison

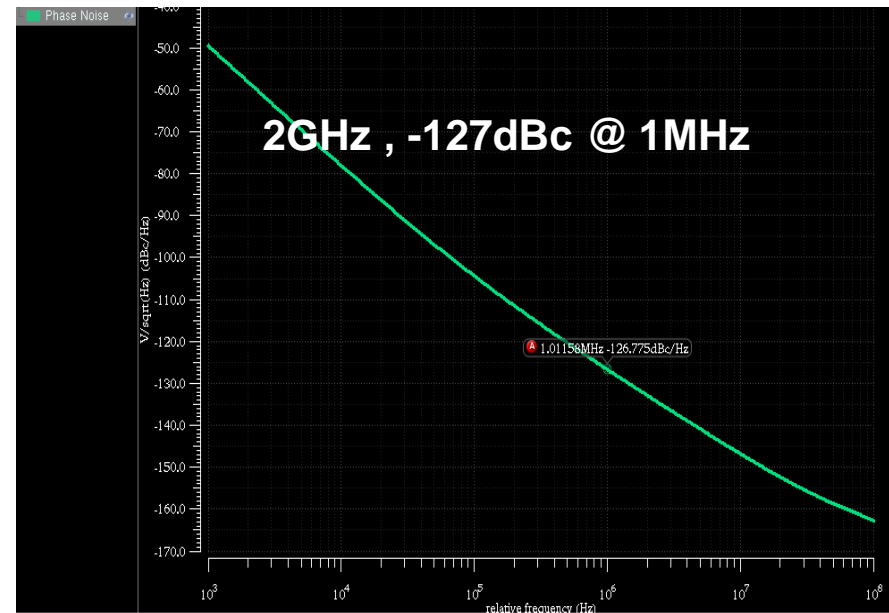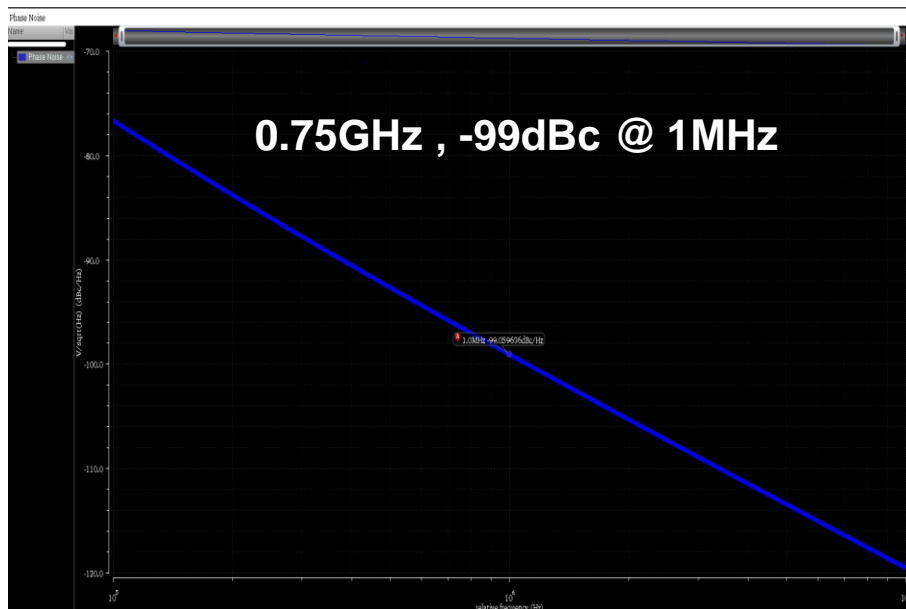- Phase noise
 - Ring VCO : -99dBc @ 0.75GHz 1MHz offset
 - LC VCO : -132dBc @ 1.17GHz 1MHz offset
 - **LC VCO is better for phase noise.**



VCO Comparison

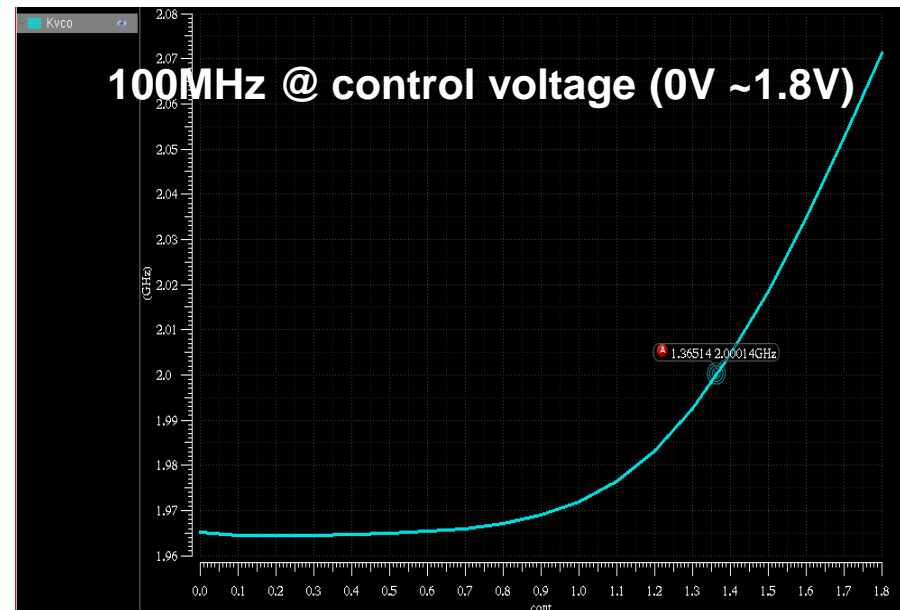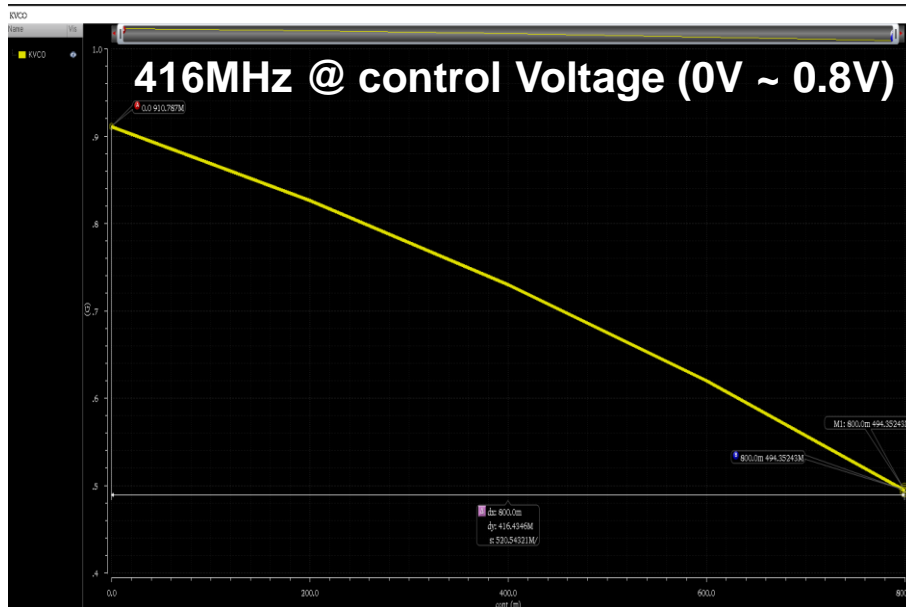- Frequency tuning range
 - Ring VCO : 416MHz @ control voltage (0V ~ 0.8V)
 - LC VCO : 100MHz @ control voltage (0V ~ 1.8V)
 - **Ring VCO is better for frequency tuning range.**



Homework

- ✓ Design 2-GHz ($\pm 100\text{MHz}$) LC VCO with tuning range larger than 100MHz
- ✓ Verify and plot output waveforms and K_{VCO} . (Use plot method of DE2)
- ✓ Verify and plot phase noise with control voltage(0V, 0.9V, 1.8V) generating 2-GHz clock.
- ✓ Indicate LC VCO schematic, inductor value, and using varactor count in the report.
- ✓ LC VCO specification
 - Supply voltage : 1.8V
 - Load capacitance: 1.5 pF
 - Phase noise : Min -115dBc/Hz
 - Frequency tuning range : Min 100MHz
- ✓ Deadline : 09/24(Thu) 19:00
 - Upload pdf file to YSCEC